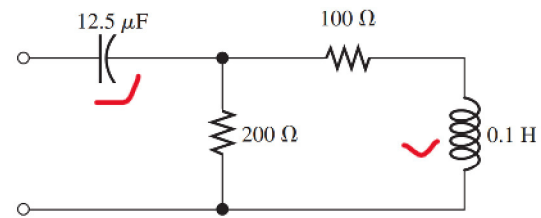


Example 1

Sunday, 16 August, 2020 9:49 AM

Determine the complex impedance between terminals shown in Figure for $\omega = 1000 \text{ rad/s}$





$$Z_L = j\omega L$$

$$Z_C = 1/(j \cdot 1000 \cdot 12.5 \cdot 10^{-6})$$

$$Z_C = 1/(j\omega C)$$
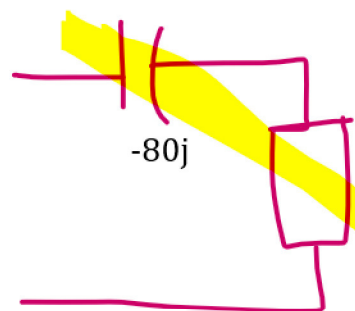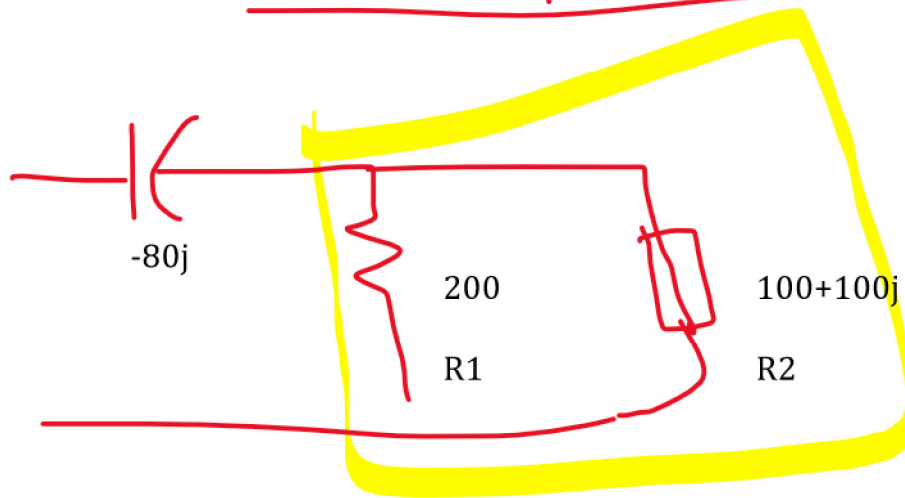
$$80 \cdot j / j \cdot j = 80j / (-1) = -80j$$



$$1/(1/R_1 + 1/R_2)$$

$$1/(1/200 + 1/(100+100j))$$

$$80+40j$$

$$1/(1/200 + 1/(100+100j)) = 80+40j$$

$$(80+40j) + (-80j) = 80-40j$$



Example 2

Sunday, 16 August, 2020 10:07 AM

$$V = V_m \cos(\omega t + \theta)$$

$$V_m \angle \theta$$

- A voltage $v_L(t) = 100 \cos(200t)$ is applied to a 0.25-H inductance. (Notice that $\omega = 200$.)
- a. Find the impedance of the inductance, the phasor current, and the phasor voltage.
- b. Draw the phasor diagram.

$$\text{Phasor Voltage (V}_L\text{)} = 100 \angle 0 = 100 (\cos(0) + j \sin(0)) = 100 (1 + j0) = 100$$

$$\text{Impedance of the inductance (Z}_L\text{)} = j\omega L = j*200*0.25 = 50j$$

$$\text{Phasor Current (I}_L\text{)} = V_L / Z_L = 100 / 50j = 2/j = -2j$$

Complex to Phasor

$$A + Bj \rightarrow \sqrt{A^2 + B^2} \angle \tan^{-1} \left(\frac{b}{a} \right)$$

$$\sqrt{0^2 + (-2)^2} \angle \tan^{-1} \left(-\frac{2}{0} \right) = 2 \angle 90$$

Example 3

Sunday, 16 August, 2020 10:08 AM

- A voltage $v_C(t) = 100 \cos(200t)$ is applied to a $100\mu\text{F}$ capacitance.
- a. Find the impedance of the capacitance, the phasor current, and the phasor voltage.
- b. Draw the phasor diagram.

$$Z_C = 1/(j\omega C)$$

$$V_C = Z_C * I_C$$

Example 4

Sunday, 16 August, 2020 10:19 AM

- Find the steady-state current for the circuit shown in Figure. Also, find the phasor voltage across each element and construct a phasor diagram.

Step 1: Convert the values to Complex Impedances

$$R = 100$$

$$L = 0.3 \text{ H} \rightarrow Z_L = j\omega L = j500 \cdot 0.3 = 150j$$

$$C = 40 \cdot 10^{-6} \text{ F} \rightarrow Z_C = 1/(j\omega C) = 1/(j500 \cdot 40 \cdot 10^{-6}) = -50j$$

Loop

$$-v_s + 100i + (150j \cdot i) + (-50j \cdot i) = 0$$


$$V_s = I(100 + 150j - 50j)$$

$$I =$$

$$V_r = R \cdot I$$

$$V_L = Z_L \cdot I$$

$$V_C = Z_C \cdot I$$

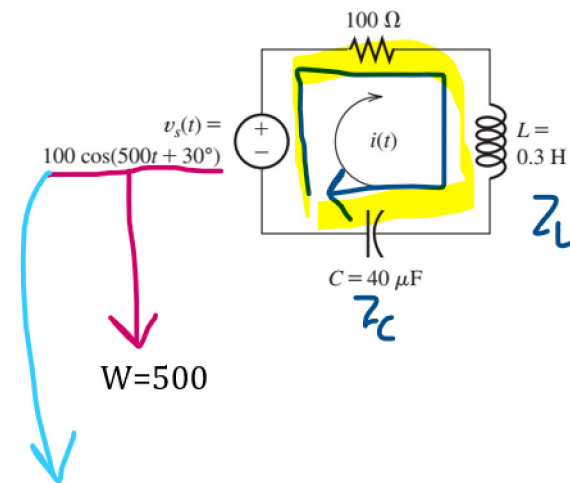

100∠30 Phasor Form

Complex Form

$$100 (\cos(30) + j \sin(30))$$