



Fall Semester 2020-2021

Continuous Assessment Test –II

Programme Name & Branch: MIC & SCOPE

Class Number: VL2020210105232

Course Code: EEE1024

Course Title: Fundamentals of Electrical and Electronics Engineering

Exam Mode: Online


Exam Duration: 45 mins

Maximum Marks: 30


Faculty Name: Prof. Sanchit Khataavkar

General instruction(s):

Refer MS Forms and Teams

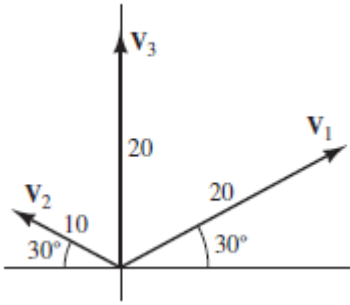(Marks distribution 5 x 6 = 30 Marks)		
S. N o.	Question	Course Outcome (CO)
1.	<p>Prove the associative law for OR operation of 3 logical inputs A, B and C using truth tables.</p> <p>(Law statement – 2marks, Intermediate steps – 2marks, Final – 2marks)</p>	CO_03
2.	<p>Consider the phasors shown in the figure below. The frequency of each signal is $f = 500\text{Hz}$.</p> <p>a) Write a time domain expression for each voltage in the form $V_m \cos(\omega t + \theta^\circ)$ (3 marks)</p> <p>b) Reduce the sum $v_z(t) = v_1(t) + v_2(t)$ to a single term of the form $V_m \cos(\omega t + \theta^\circ)$ using phasors. (3 marks)</p> 	CO_02
3.	<p>Convert the following- (Each sub-question: 3 marks – 2 marks for working, Final - 1 mark)</p> <p>a) 412.65_{10} to binary</p> <p>b) $D93.8_{16}$ to binary</p>	CO_03

4. Find the mesh currents I_1 and I_2 in the circuit given below.
(Mesh current equations – 3 marks, Final – 3marks)

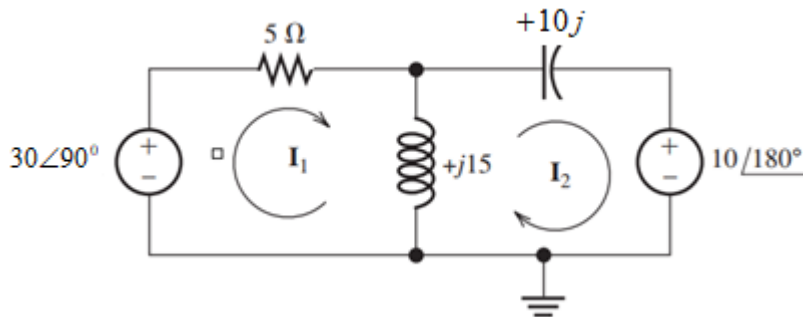

CO_02

5. Explain briefly (in 1-2 sentences only) the relation between input lines and select lines in a multiplexer and write the types of multiplexers (3 marks)

CO_03

Draw the output waveform (Y) for the input data and select lines waveforms of a 4:1 multiplexer, given below. (Note: Draw only the waveform of output by looking at the inputs and select lines from the question paper) (3 marks)

