

BASIC CIRCUIT ELEMENTS AND SOURCES, OHMS LAW

Module 1: Fundamentals of DC Circuits

EEE 1024 Fundamentals of Electrical and Electronics Engineering



1



BIOGRAPHY

- Dr. Kishore Bingi
- Assistant Professor Senior Grade 1
- School of Electrical Engineering
- PhD from Universiti Teknologi PETRONAS, Malaysia
- <https://www.kishorebingi.co.in/>
- kishore.bingi@vit.ac.in



Team Name: EEE1024 A1 Slot Monday & Wednesday Morning



Syllabus: Teams - General - Files



Material: Teams - Module - Files



Attendance: Teams - Time in & Time Out - VTOP



Questions during Presentation: Raise Hand



Queries in General: Teams - Channel - Chat



Assignments - End of each module through Moodle



MICROSOFT TEAMS & OTHERS

TOPICS



- Electrical Circuit
- Circuit Elements
- Charge
- Electrical Current
- Electrical Voltage
- Power & Energy
- Resistors and Ohm's Law
- Ohm's Law Triangle
- Power Triangle
- Ohm's Law Pie Chart

ELECTRICAL CIRCUIT

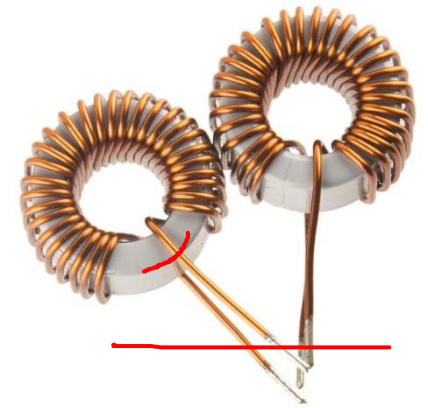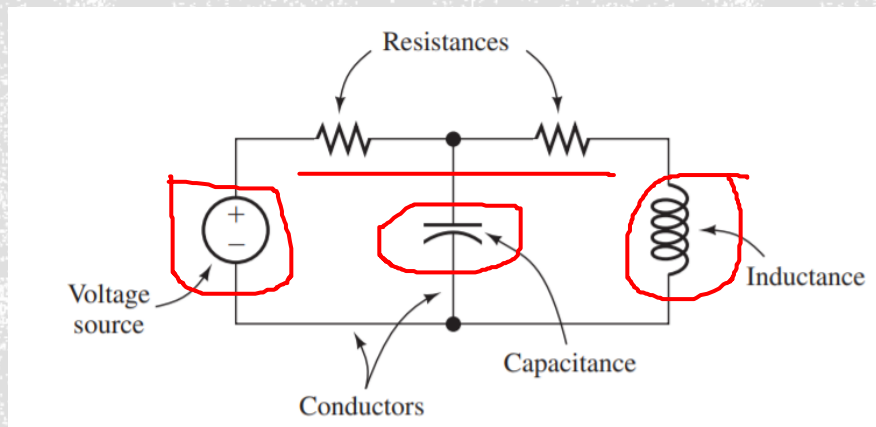
- An **electrical circuit** consists of various types of circuit elements connected in closed paths by conductors.
- The circuit elements can be resistances, inductances, capacitances, and voltage sources, among others



R L C

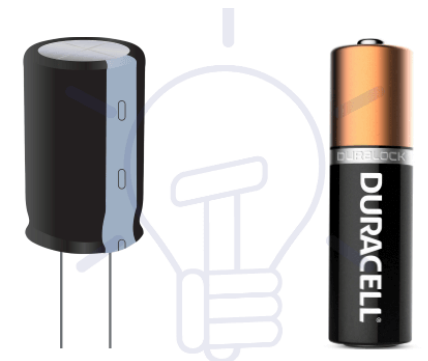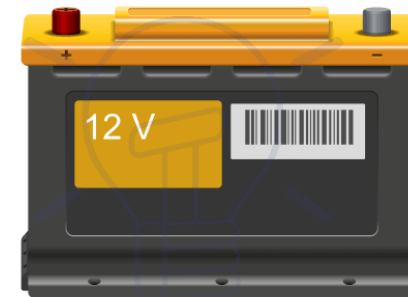

CHARGE

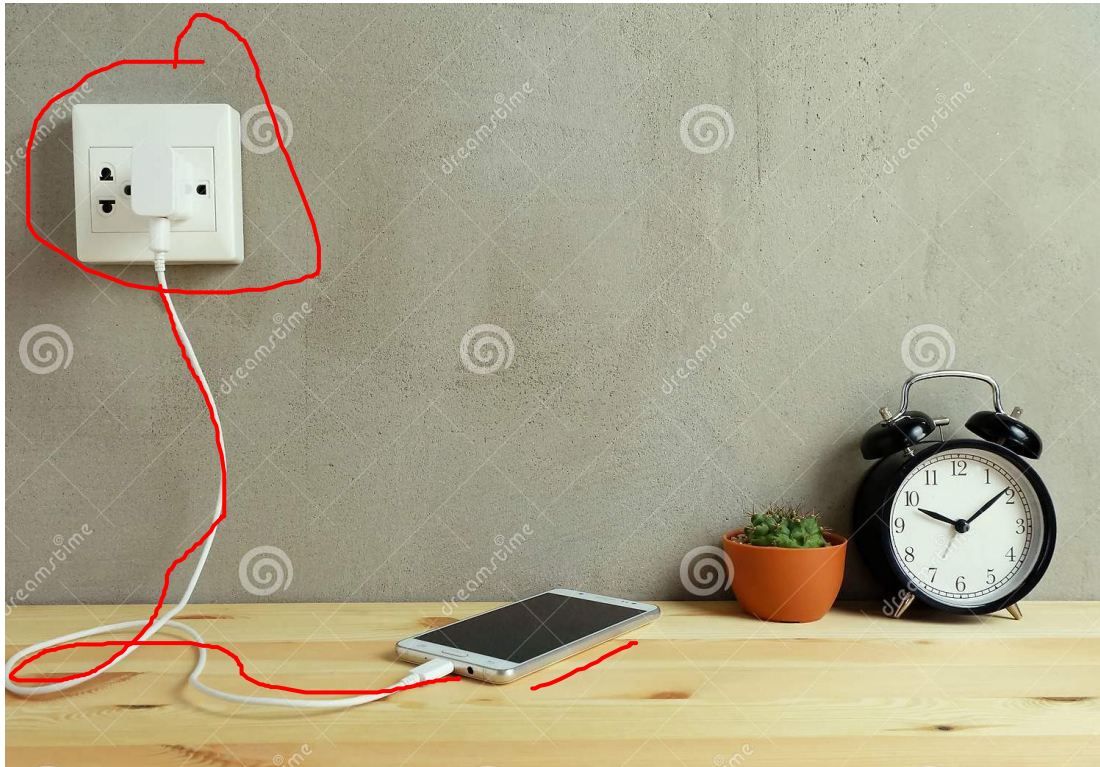

- Charge flows easily through conductors, which are represented by lines connecting circuit elements.
- Voltage sources create forces that cause charge to flow through the conductors and other circuit elements.
- As a result, energy is transferred between the circuit elements, resulting in a useful function.

ELECTRICAL CURRENT

- Electrical current is the time rate of flow of electrical charge ($q(t)$) through a conductor or circuit element.

$$\underline{i(t) = \frac{dq(t)}{dt}}$$

- The units are amperes (A), which are equivalent to coulombs per second (C/s).
- The charge on an electron is $-1.602 \times 10^{-19}\text{C}$.
- To find charge given current, we must integrate.

$$\underline{q(t) = \int_{t_0}^t i(t)dt + q(t_0)}$$

- t_0 is some initial time at which the charge is known.

EXAMPLE 1: DETERMINING CURRENT GIVEN CHARGE

- Suppose that charge versus time for a circuit element is given by

$$q(t) = \begin{cases} 0 & \text{for } t < 0 \\ 2 - 2e^{-100t} \text{ C} & \text{for } t > 0 \end{cases}$$

- Calculate $i(t)$ and Plot $i(t)$ and $q(t)$
- Solution:

$$i(t) = \frac{dq(t)}{dt}$$

$$\text{For } t < 0 \rightarrow i(t) = \frac{dq(t)}{dt} \rightarrow 0$$

$$\text{For } t > 0 \rightarrow i(t) = \frac{dq(t)}{dt} \rightarrow \frac{d}{dt}(2 - 2e^{-100t}) \rightarrow 200e^{-100t} \text{ A}$$

EXAMPLE 2: DETERMINING CURRENT GIVEN CHARGE

- The charge that passes through a circuit element is given by



$$q(t) = 0.01 \sin(200t) \text{ C}$$

- Find the current as a function of time.





DIRECT CURRENT (DC) AND ALTERNATING CURRENT (AC)

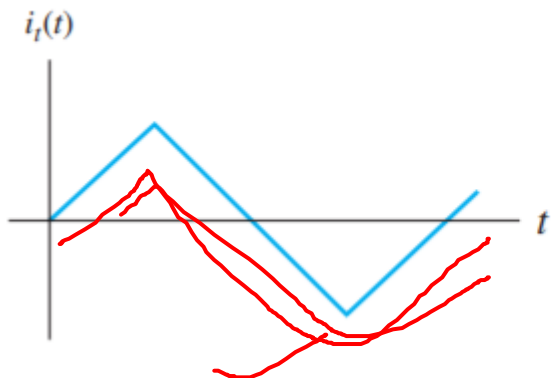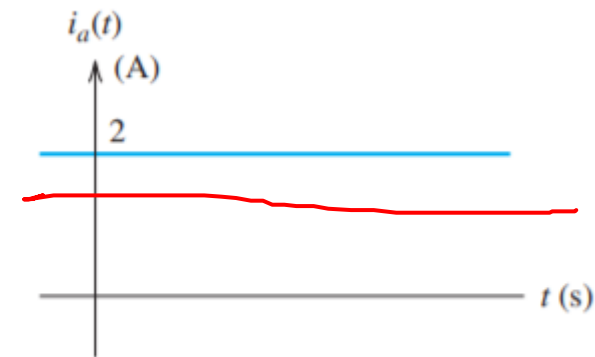- When a **current is constant with time**, we say that we have **direct current**, abbreviated as **dc**
- When current that varies with time, reversing direction periodically, is called alternating current, abbreviated as **ac**.





?

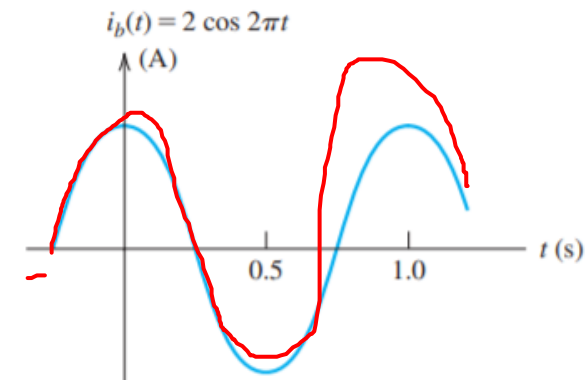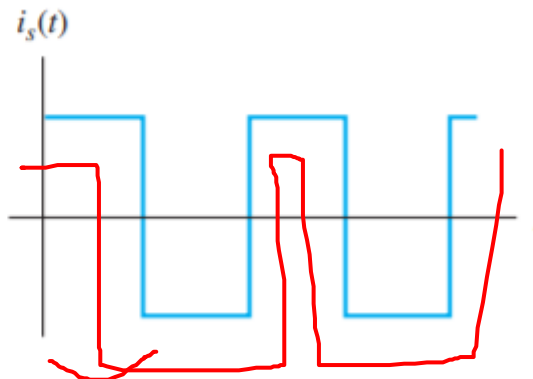

DIRECT VOLTAGE (DC) AND ALTERNATING VOLTAGE (AC)

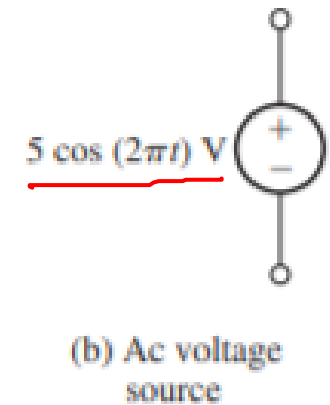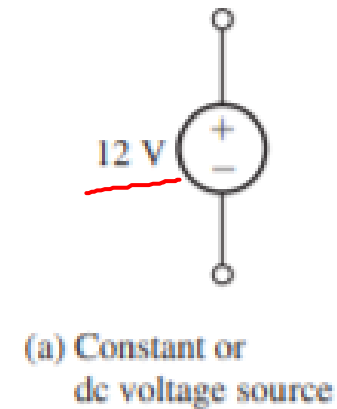- The **voltage** associated with a circuit element is the energy transferred per unit of charge that flows through the element.
- The units of voltage are volts (V), which are equivalent to joules per coulomb (J/C).
- Voltage constant with time is called **dc voltage**.
- Voltage that change in magnitude and alternate in polarity with time is called **ac voltage**.




BASIC CIRCUIT ELEMENTS

- Resistance ✓
- Inductance ✓
- Capacitor ✓

SOURCES

- Voltage (V or J/C) – dc & ac ✓
- Current (A or C/s) – dc & ac ✓
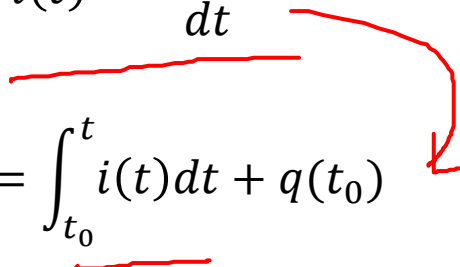
$$i(t) = \frac{dq(t)}{dt}$$
$$q(t) = \int_{t_0}^t i(t) dt + q(t_0)$$


POWER & ENERGY

- The current i is the rate of flow of charge and the voltage v is a measure of the energy transferred per unit of charge, the product of the current and the voltage is the rate of energy transfer.

- Thus, the product of current and voltage is power.

$$p = v * i$$

- Volts * Amperes = (joules/coulomb) * (coulombs/second) = joules/second = watts

POWER & ENERGY

- To calculate the energy w delivered to a circuit element between time instants t_1 and t_2 , we integrate power

$$\mathcal{E} \quad \underline{w} = \int_{\underline{t_1}}^{\underline{t_2}} p(t) dt$$

- The units of energy is joules (J)

EXAMPLE 3 & 4: ENERGY & POWER

- Voltage is 12V and Current is 2 A.
Calculate the power

$$p = v * i$$

$$p = 24 \text{ W}$$

$$E = \int_{t_1}^{t_2} 24 dt$$
$$= 24(t_2 - t_1)$$

- Voltage is 12V and Current is $2e^{-t}$.
Calculate the power and energy for the intervals from $t_1 = 0$ to $t_2 = \infty$

$$p = 12 * 2e^{-t}$$

$$p = 24e^{-t} \text{ W}$$

- Energy:


$$w = \int_0^{\infty} 24e^{-t} dt$$
$$w = 24 \text{ J}$$



RESISTORS AND OHM'S LAW

- The relationship between Voltage, Current and Resistance in any DC electrical circuit was firstly discovered by the German physicist Georg Ohm.
- The voltage ***V*** across an ideal resistor is proportional to the current ***I*** through the resistor ***R***.


$$\underline{V = I * R}$$

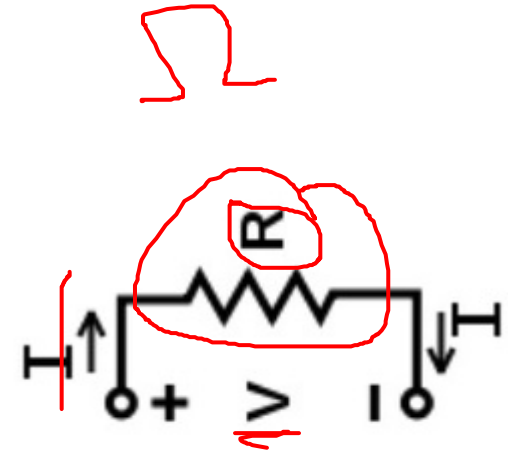- The units of resistance are V/A, which are called ohms. The uppercase Greek letter omega (Ω) represents ohms.




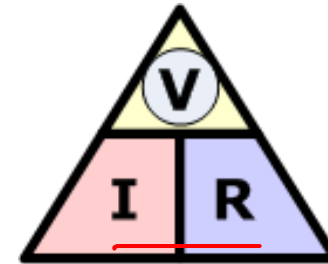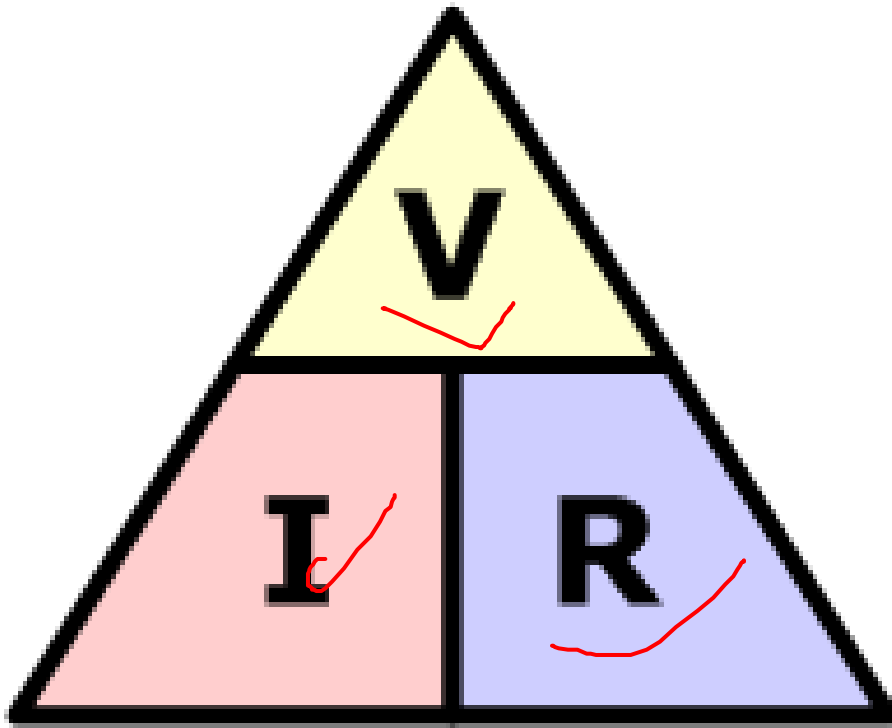

$$\textcircled{V} = I \times R$$


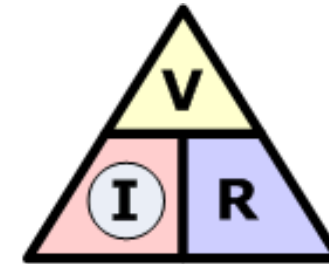


$$\textcircled{I} = \frac{V}{R}$$

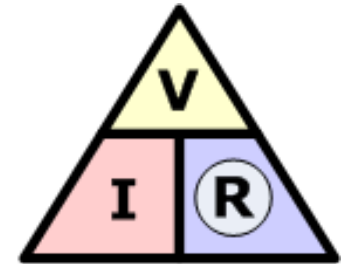


$$\textcircled{R} = \frac{V}{I}$$


OHMS LAW TRIANGLE

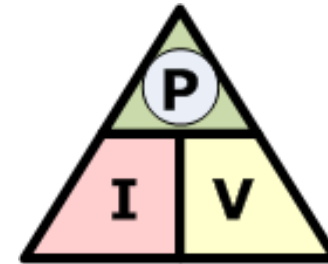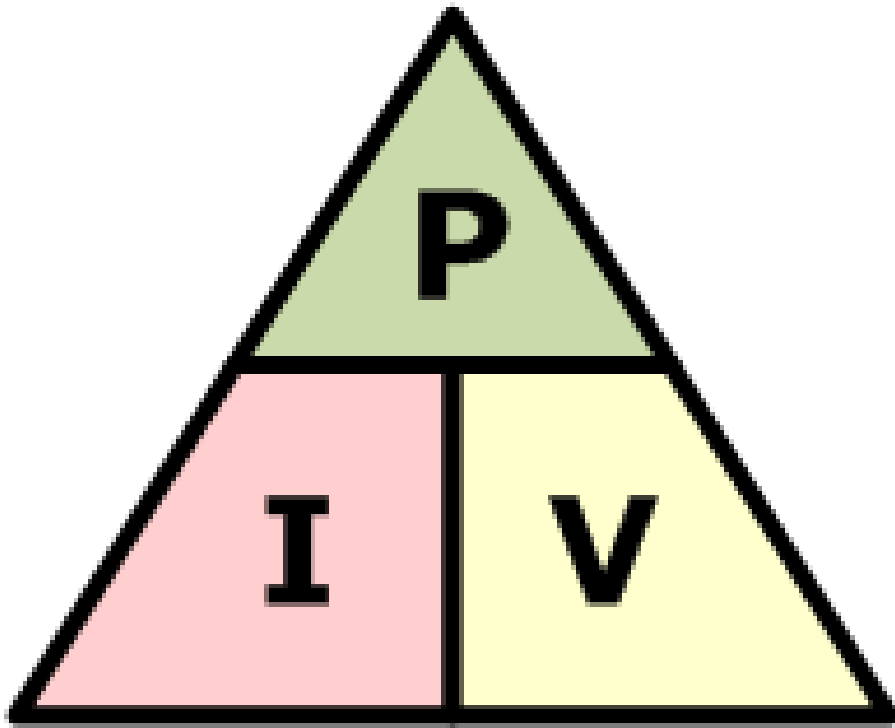

$$\textcircled{P} = I \times V$$

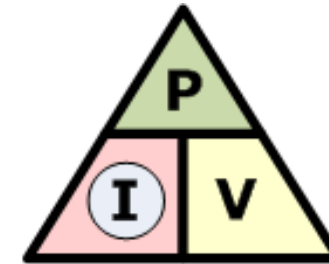

$$\textcircled{I} = \frac{P}{V}$$

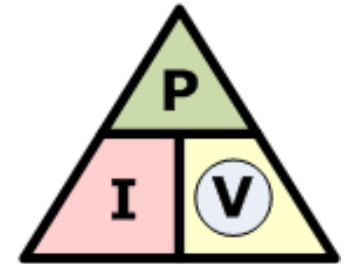


$$\textcircled{V} = \frac{P}{I}$$

POWER TRIANGLE

I = Amps

V = Volts

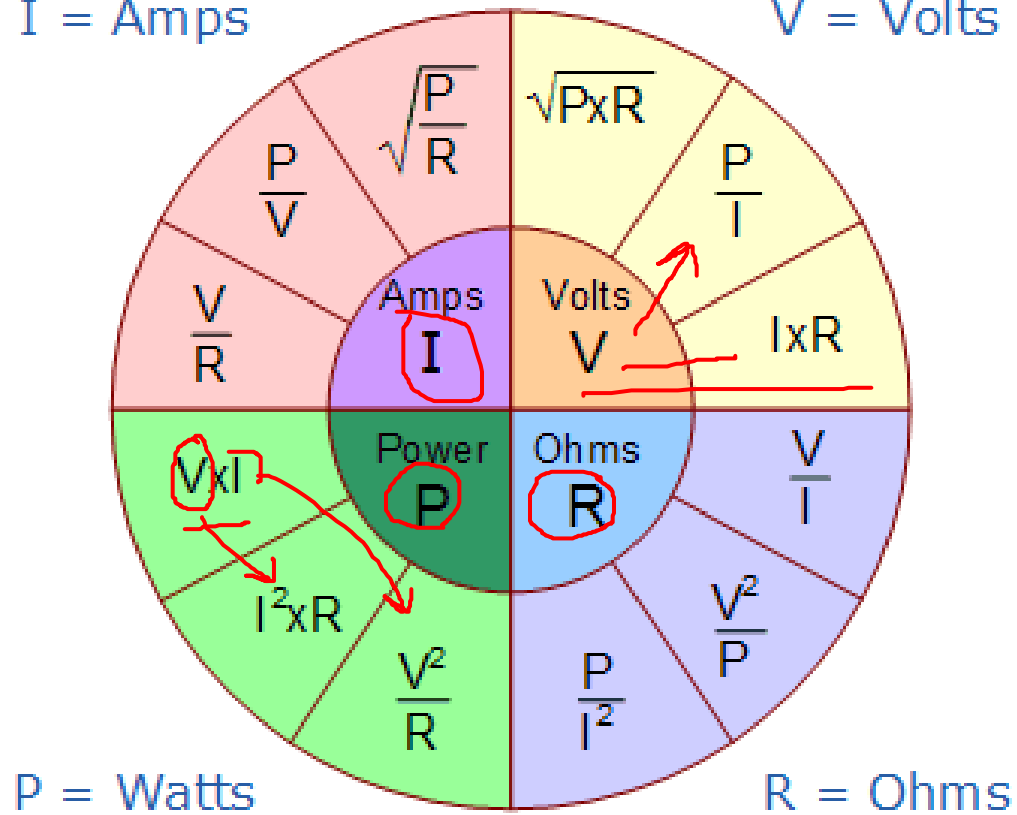

OHMS LAW PIE CHART



CONDUCTANCE

- Solving Ohm's law for current, we have


$$i = \frac{1}{R} v$$

- We call the quantity $\frac{1}{R}$ a conductance.
- It is customary to denote conductance with the letter G.

$$G = \frac{1}{R}$$

- Conductance's have the units of inverse ohms (Ω^{-1}), which are called siemens (abbreviated S). Thus, we can write Ohm's law as

$$i = G * v$$

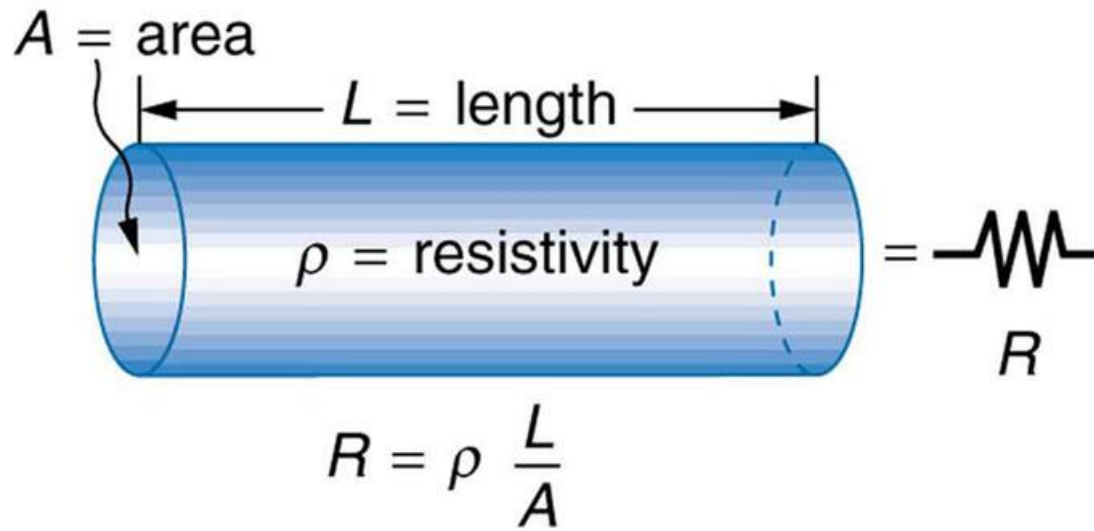

- The cross-sectional area A is constant along the length of the cylinder or bar. If the length L of the resistor is much greater than the dimensions of its cross section, the resistance is approximately given by

$$R = \frac{\rho L}{A}$$

- ρ is the resistivity of the material used to construct the resistor.
- The units of resistivity are ohm meters (Ωm)

RESISTANCE RELATED TO PHYSICAL PARAMETERS

RESISTANCE RELATED TO PHYSICAL PARAMETERS

- Materials can be classified as **conductors**, **semiconductors**, or **insulators**, depending on their resistivity.
- **Conductors** have the **lowest resistivity** and **easily conduct electrical current**.
- **Insulators** have **very high resistivity** and **conduct very little current** (at least for moderate voltages).
- **Semiconductors** fall between conductors and insulators.



- Insulator
- conductors
- semiconductors



ASSIGNMENT 1: RESISTANCE CALCULATION

Compute the resistance of a copper wire having a diameter of 2.05 mm and a length of 10 m. Note the resistivity of a copper is given as $1.72 \times 10^{-8} \Omega\text{m}$.

ASSIGNMENT 2: MATCH THE FOLLOWING

- | | |
|--------------------------------|----------------------|
| 1. Units of Voltage | a. Watt |
| 2. Units of Current | b. $V=I*R$ |
| 3. Units of Power | c. Ohm (Ω) |
| 4. Units of Resistance | d. Ampere (A or C/s) |
| 5. Units of Charge | e. Volt (V or J/C) |
| 6. Units of Energy | f. $P=V*I$ |
| 7. Units of <u>Conductance</u> | g. Siemens (S) |
| 8. Ohm's law | h. $(R*A)/L$ |
| 9. Power | i. Joules (J) |
| 10. Resistivity | j. C |