




# **EEE1024: Fundamentals of Electrical and Electronics Engineering**

**Dr. Sanchit Khataavkar**

# **NODE VOLTAGE ANALYSIS**

# Node Voltage Analysis


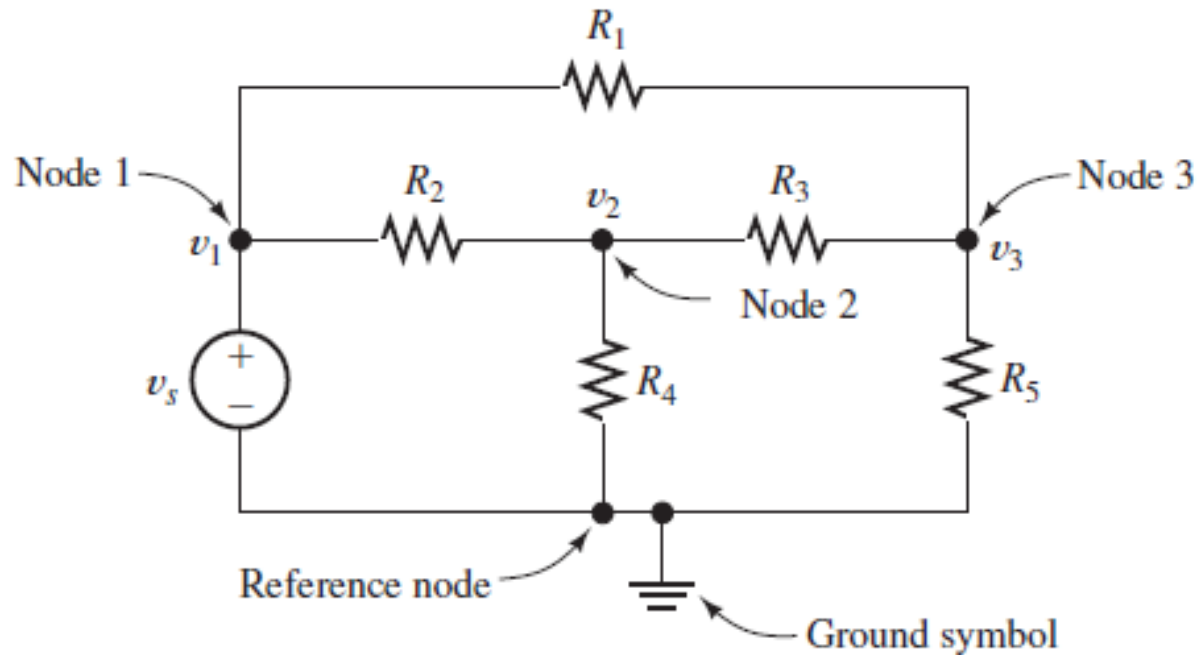


Series or parallel combinations – no use for this circuit!

# Node Voltage Analysis

Example 1:

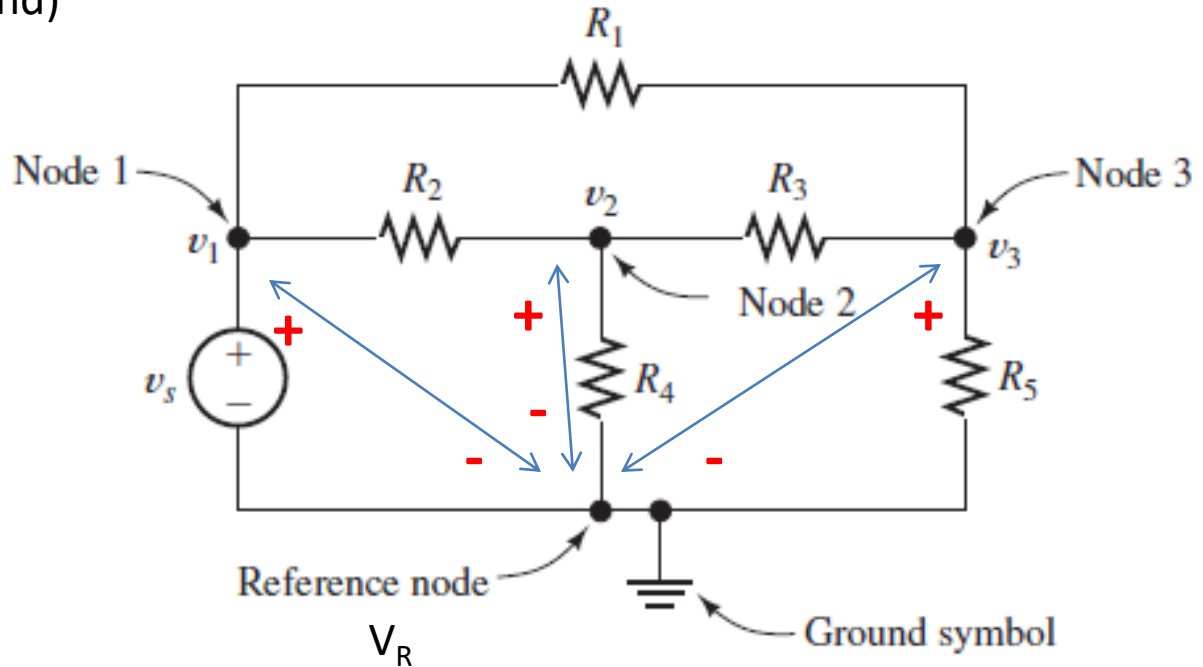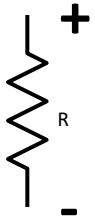1. Assign a **Reference Node** (Ground)
2. Assign **node voltage** names to remaining nodes.



3. Solve **easy nodes first** (which have a source connected to ref. node)
4. Write **KCL for each node** (ohm's law in mind)
5. Solve for all node voltages

# Node Voltage Analysis - 1

Example 1:

@ Node 1,  $v_1 = v_s$

KCL @ Node 3

$$\frac{(v_3 - v_1)}{R_1} + \frac{(v_3 - v_2)}{R_3} + \frac{(v_3 - 0)}{R_4} = 0$$


KCL @ Node 1

$$\frac{(v_1 - v_3)}{R_1} + \frac{(v_1 - v_2)}{R_2} = 0$$

KCL @ Node 2

$$i_1 + i_2 + i_3 = 0$$
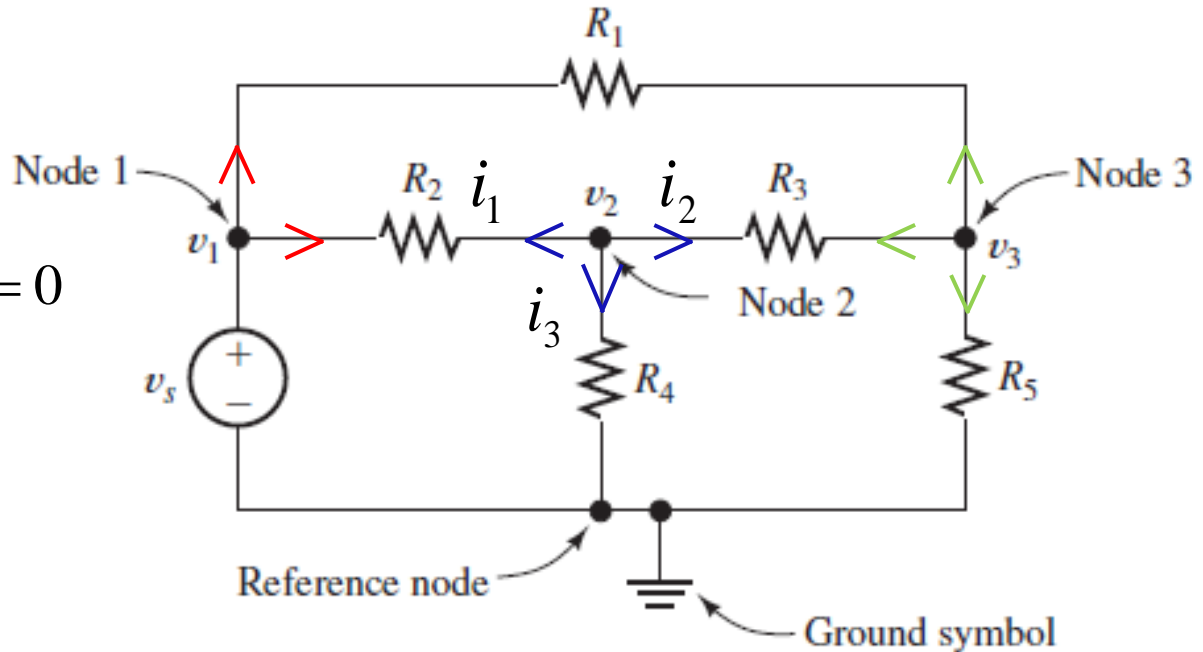
$$\frac{(v_2 - v_1)}{R_2} + \frac{(v_2 - v_3)}{R_3} + \frac{(v_2 - 0)}{R_4} = 0$$




Add all currents leaving the node and set the sum to zero

– if there is a current source ???

# Node Voltage Analysis - 2

Example 2:

Use KCL and find equations at each node

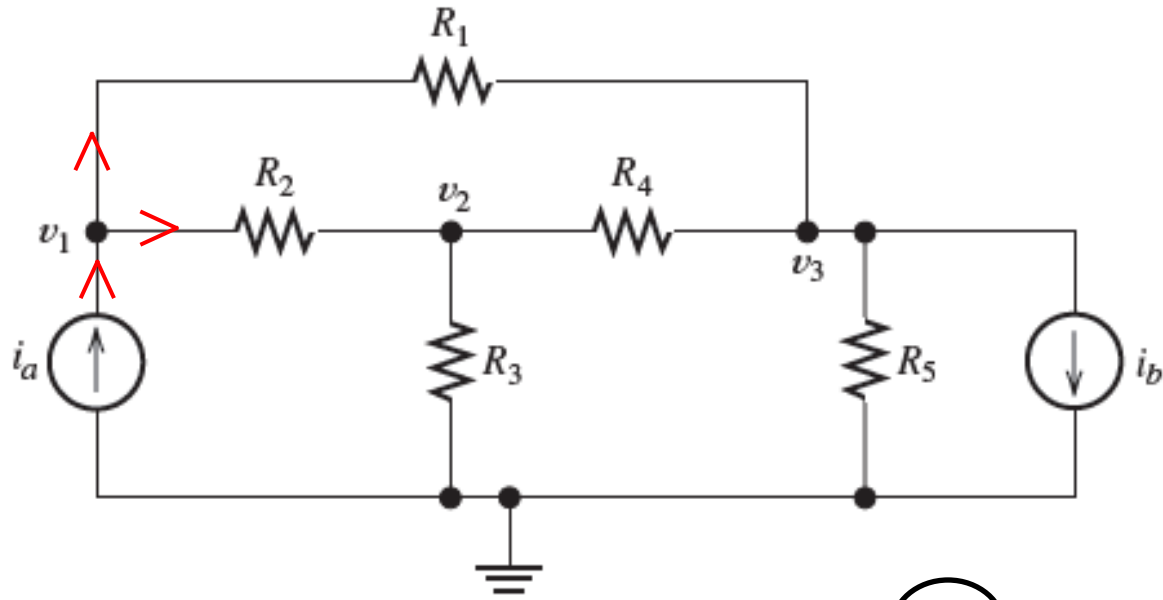


$$\frac{(v_1 - v_3)}{R_1} + \frac{(v_1 - v_2)}{R_2} = i_a \quad \text{--- (1)}$$

$$\frac{(v_2 - v_1)}{R_2} + \frac{(v_2 - v_3)}{R_4} + \frac{v_2}{R_3} = 0 \quad \text{--- (2)}$$

$$\frac{(v_3 - v_2)}{R_4} + \frac{(v_3 - v_1)}{R_1} + \frac{v_3}{R_5} + i_b = 0 \quad \text{--- (3)}$$

# Node Voltage Analysis - Practice


Q1:

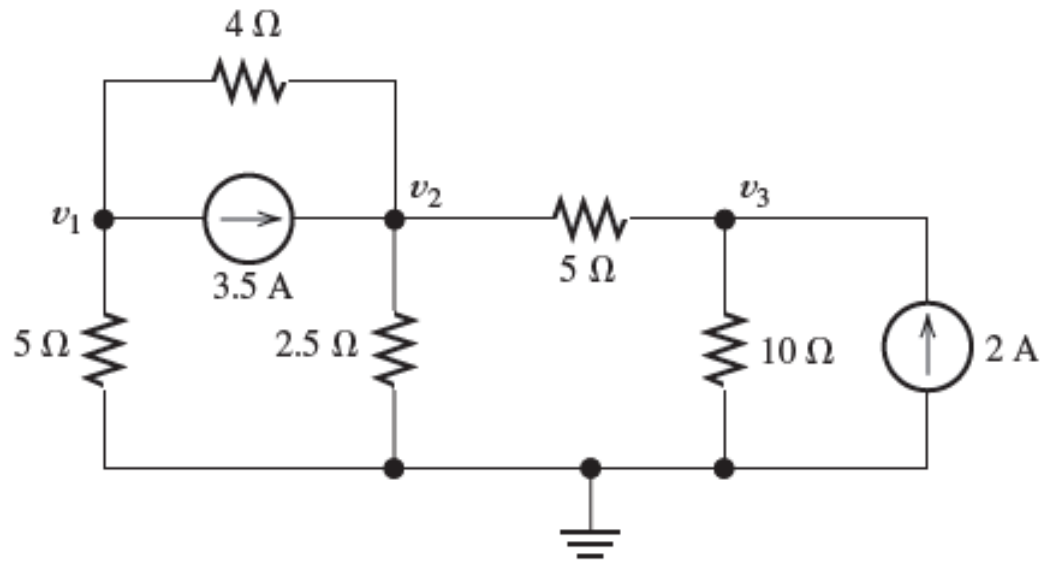

ASSIGNMENT – due 29<sup>th</sup> July 2020

# Node Voltage Analysis - Practice

Q 2:

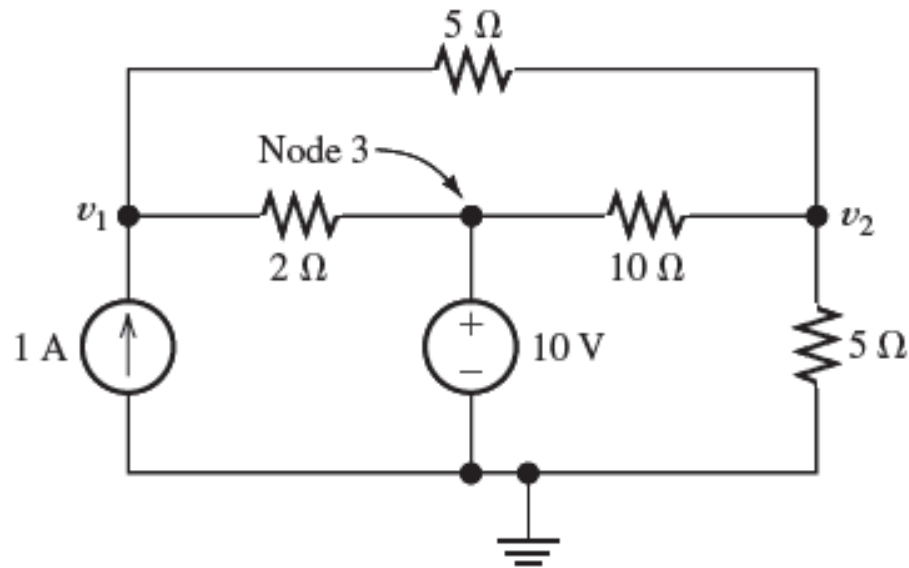


ASSIGNMENT – due 29<sup>th</sup> July 2020




# MESH CURRENT ANALYSIS

# Mesh Current Analysis

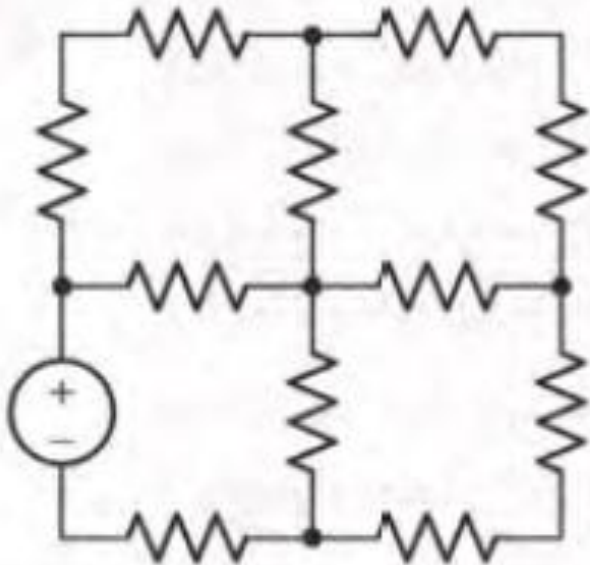


PLANAR Networks

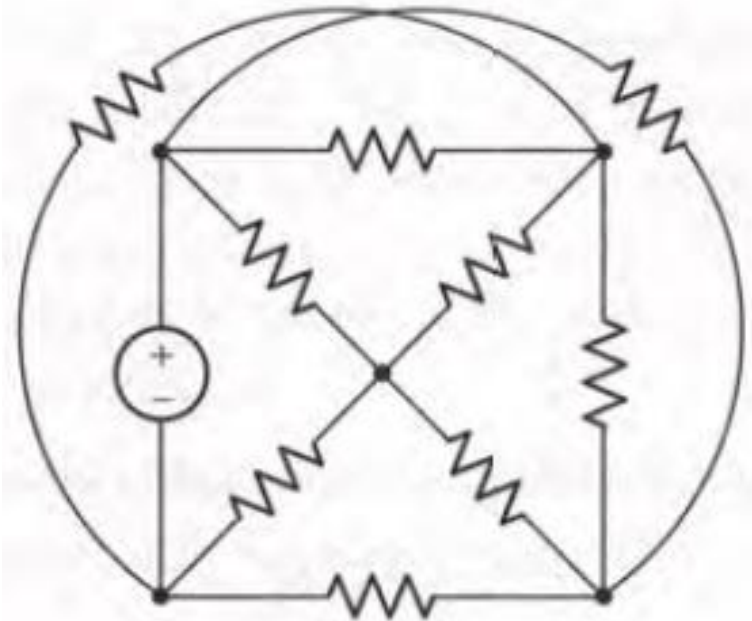

NON-PLANAR  
Networks

# Mesh Current / Loop Current



Branch current Vs Mesh current

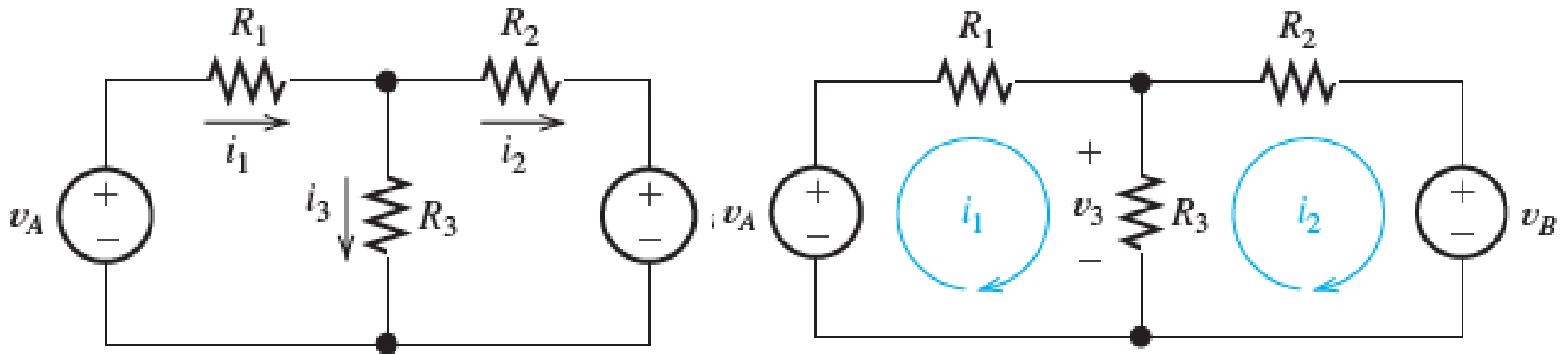

Branch currents –  
through elements

Mesh currents

# How to choose the mesh currents?

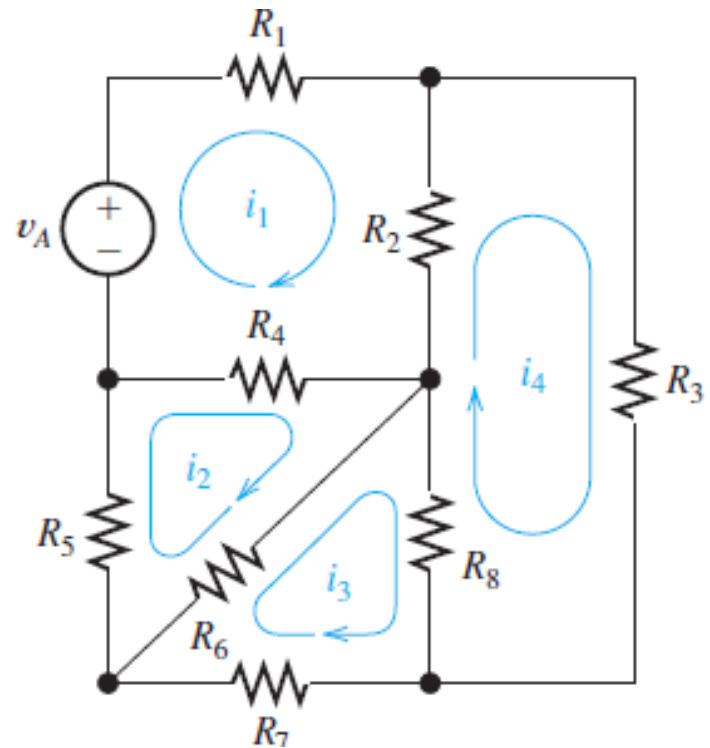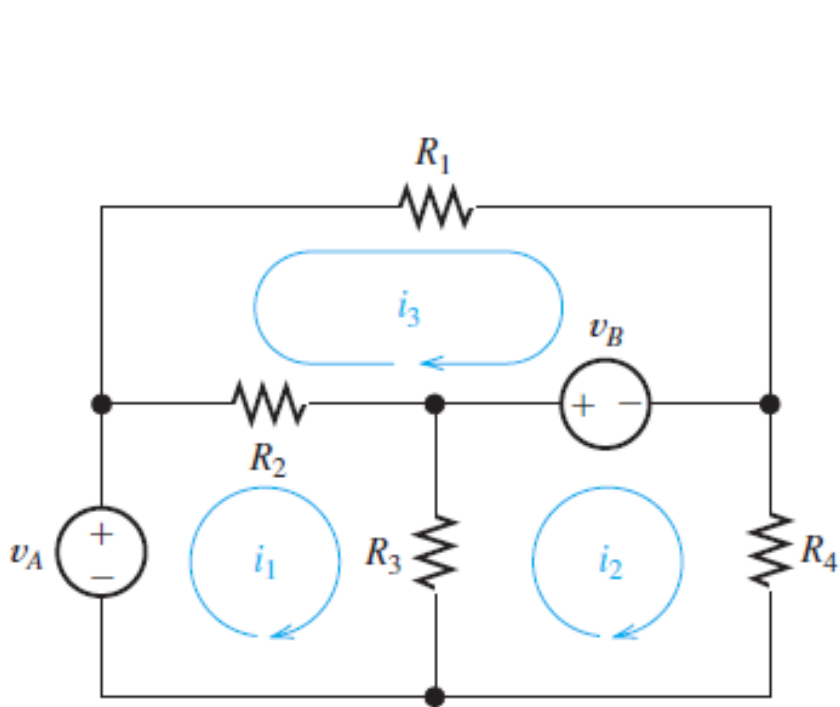

In complicated circuits, this method comes in handy!

# Acknowledgements

1. H. Hayt, J.E. Kemmerly and S. M. Durbin, 'Engineering Circuit Analysis', 6/e, Tata McGraw Hill, New Delhi, 2011
2. Allan R. Hambley, 'Electrical Engineering - Principles & Applications, Pearson Education, First Impression, 6/e, 2013