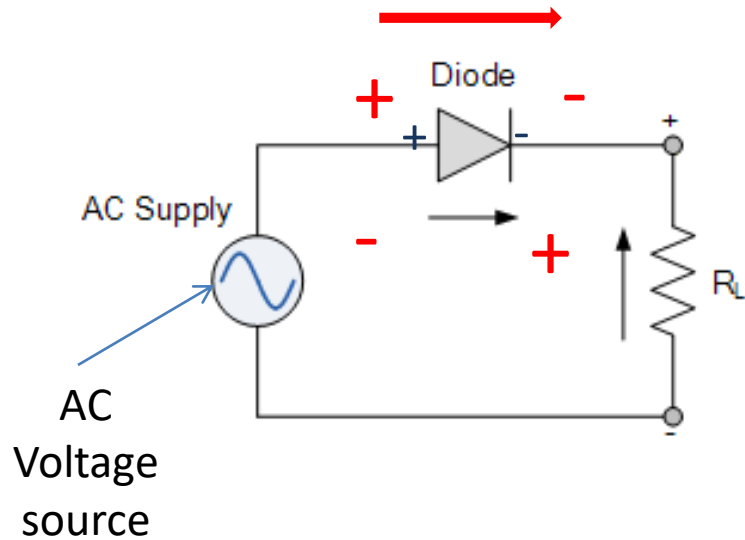





EEE1024: Fundamentals of Electrical and Electronics Engineering

Dr. Sanchit Khataavkar

Half wave Rectifier



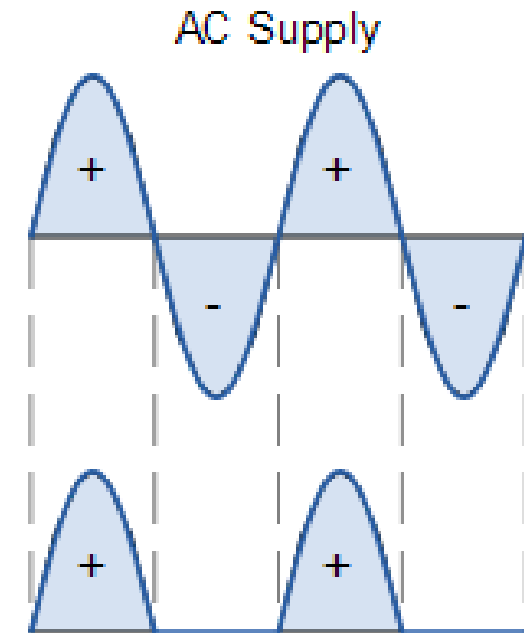
Unique feature of a pn-junction diode utilized to convert the *bi-directional* alternating supply into a *one-way unidirectional* current by eliminating one-half of the supply.




Rectified Output Waveform
No Negative Half-cycle

Half wave Rectifier

AC Sinusoidal Waveform

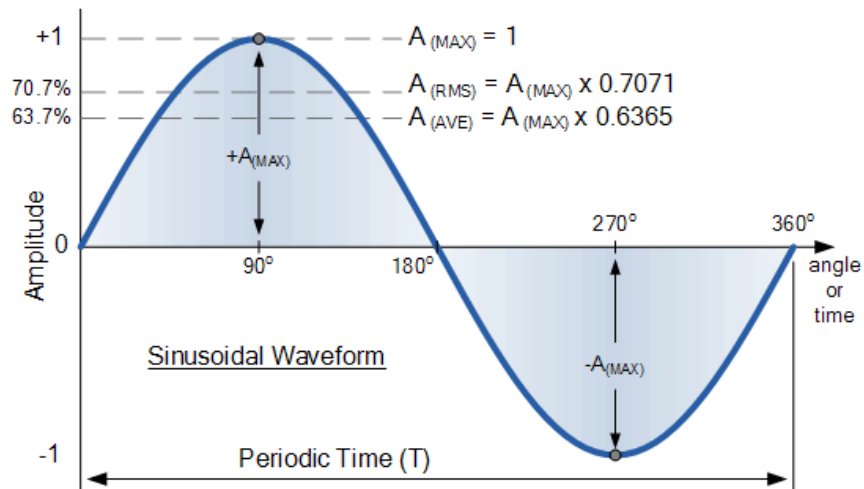
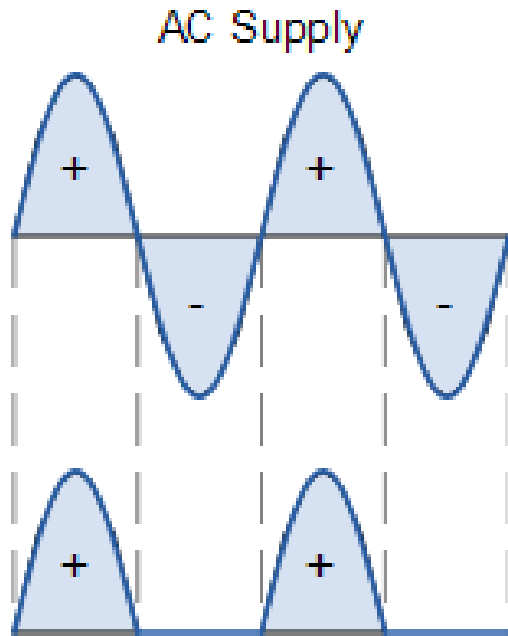
$$A_{AVG} = \frac{0.637}{2} \times A_{MAX} = \frac{A_{MAX}}{\pi} = 0.318 A_{MAX}$$



Rectified Output Waveform
No Negative Half-cycle

$$V_{AVG} = 0.318 \times V_{MAX}$$

$$I_{AVG} = 0.318 \times I_{MAX}$$


$$\frac{V_{AVG}}{V_{RMS}} = 0.9$$

$$V_{AVG} = 0.45 \times V_{RMS}$$

$$I_{AVG} = 0.45 \times I_{RMS}$$

Half wave Rectifier

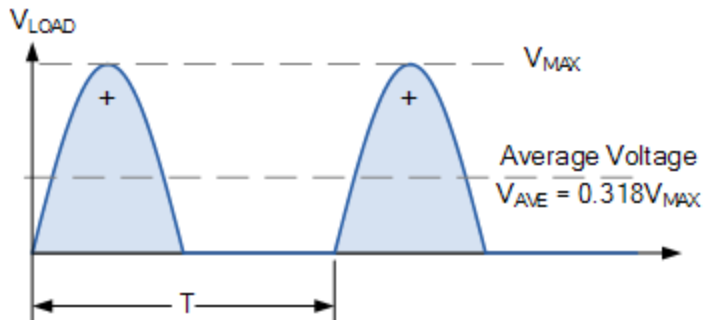Example A single phase half-wave rectifier is connected to a 50V RMS 50Hz AC supply. If the rectifier is used to supply a resistive load of 150 Ohms. Calculate the equivalent DC voltage developed across the load, the load current and power dissipated by the load. Assume ideal diode characteristics.



$$V_m = V_p = V_{PK} = V_{MAX}$$

$$V_{RMS} = 50 \text{ volts} \quad \text{—————} \quad \text{Given}$$

$$V_{max} = V_P = 1.414 \cdot V_{RMS} = 1.414 \cdot 50 = 70.7 \text{ volts}$$

$$V_{RMS} = V_{PK} \times 0.707 \quad \frac{V_{RMS}}{V_P} = 0.707 \quad \frac{V_P}{V_{RMS}} = \frac{1}{0.707} = 1.414$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\text{Equivalent DC voltage} = V_{AVG} = 0.318 \cdot V_P = 0.318 \cdot 70.7 = 22.5 \text{ volts}$$


$$\text{Load current } I_L = \frac{V_{AVG} \text{ or } V_{DC}}{R_L} = 22.5 / 150 = 0.15 \text{ A or } 150 \text{ mA}$$

$$\text{Power dissipated by load } P_L = V_{DC} \times I \text{ or } I^2 \cdot R_L = 22.5 \cdot 0.15 = 3.375 \text{ W} \cong 3.4 \text{ W}$$

Full wave Rectifier

Full wave BRIDGE Rectifier

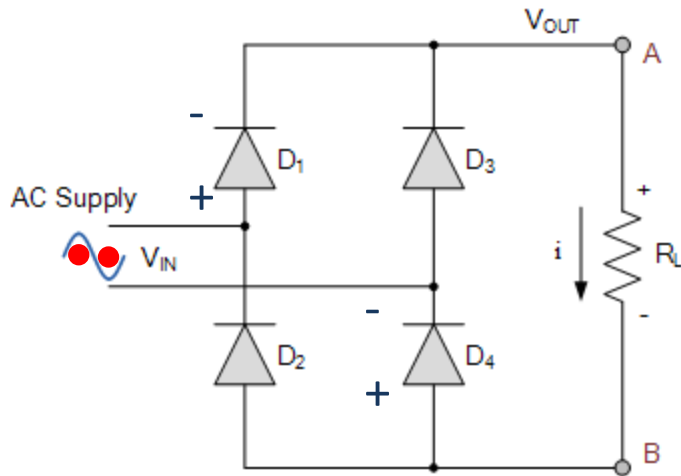This bridge configuration of diodes provides full-wave rectification because at any time two of the four diodes are forward biased while the other two are reverse biased.



During +ve half cycle of V_{IN} ,

D_1 and D_4 are forward biased, whereas,

D_2 and D_3 are reverse biased



During -ve half cycle of V_{IN} ,

D_2 and D_3 are forward biased, whereas,

D_1 and D_4 are reverse biased

Full wave Rectifier

Full wave BRIDGE Rectifier

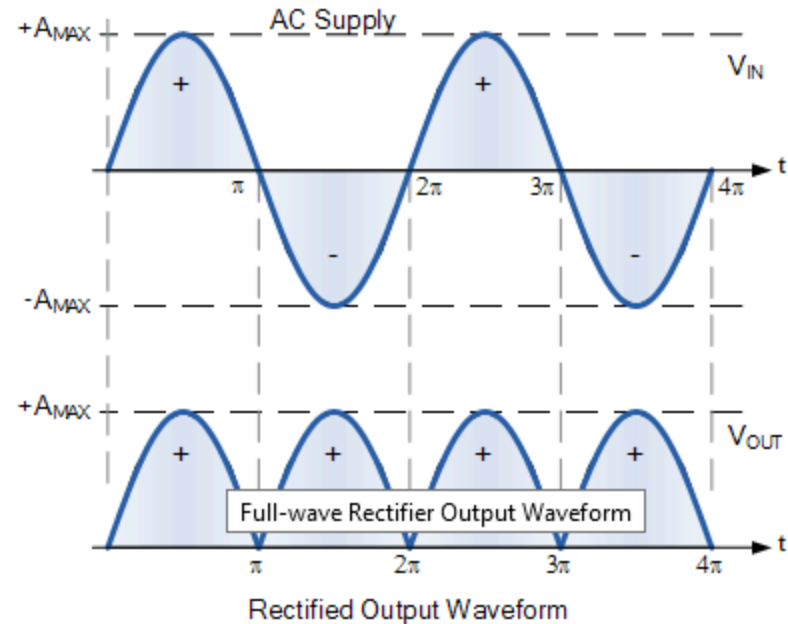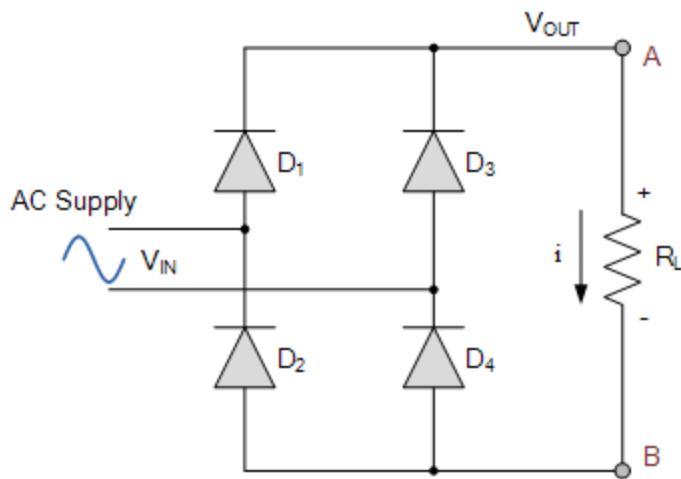

$$V_{AVG} = 0.637 * V_{MAX}$$



$$I_{AVG} = 0.637 * I_{MAX}$$

$$V_{AVG} = 0.9 * V_{RMS}$$

$$I_{AVG} = 0.9 * I_{RMS}$$


Ripple Factor

Half wave (HW) Rectifier

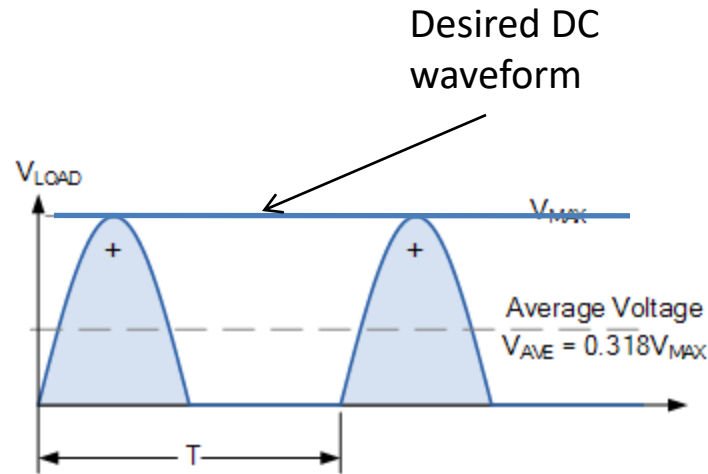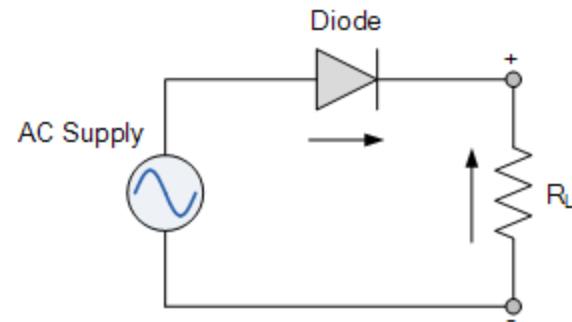

Actual o/p of a HW rectifier

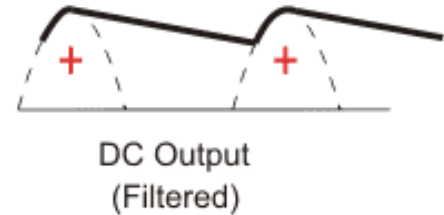O/p of HW rectifier which is filtered using a capacitor



DC Output (Filtered)

Ripple Factor γ – Unwanted AC component remaining while converting AC waveform into DC

$$\gamma = \sqrt{\left(\frac{V_{rms}}{V_{DC}}\right)^2 - 1}$$

$$= \frac{\sqrt{(V_{rms})^2 - (V_{dc})^2}}{V_{dc}}$$

$$= \frac{\sqrt{(0.5I_m)^2 - (0.318I_m)^2}}{0.318I_m}$$

$$= 1.21$$


For a half-wave rectifier

$$\gamma = \frac{\sqrt{(I_{rms})^2 - (I_{dc})^2}}{I_{dc}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{rms}^2 = \frac{V_m^2}{(\sqrt{2})^2} = \frac{V_m^2}{2}$$

“p-n” Junction Diode: *Breakdown*

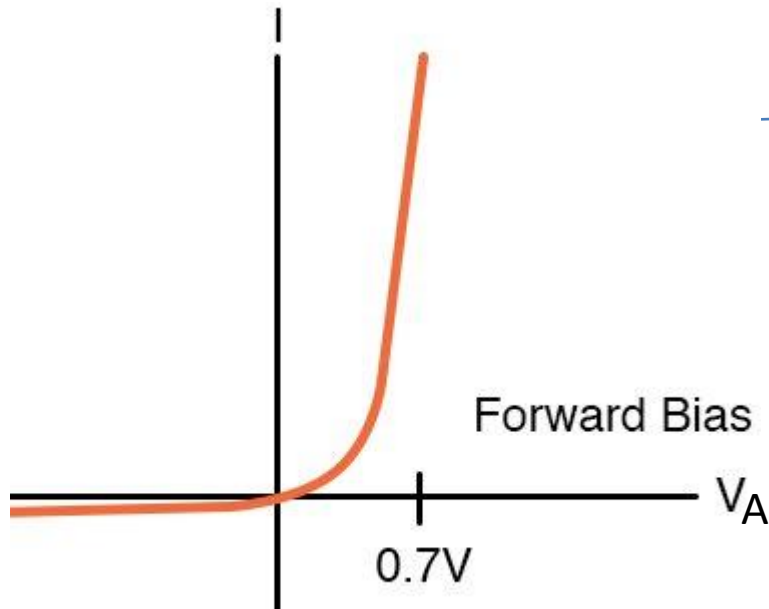


$$I = -I_o$$

Ideal diode equation for Reverse bias

$$I = I_o \left(e^{\frac{qV_A}{kT}} - 1 \right)$$

Ideal diode equation for Forward bias

$$\frac{kT}{q} = 0.026V$$

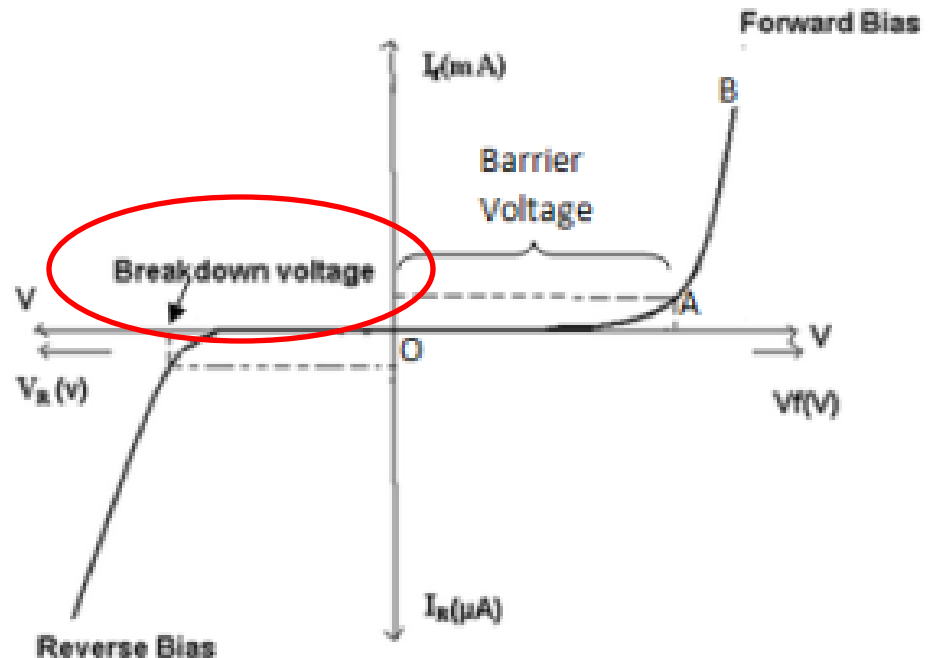

“p-n” Junction Diode: Breakdown

Causes of BREAKDOWN

Zener effect

Zener breakdown –

- If the doping of either p type or n-type is more, depletion region is thin
- Number of free electrons is more
- In reverse bias – these free electrons gain velocity and collide, breaking bonds and setting more electrons “free”



Avalanche effect

Avalanche breakdown –

- Reverse bias – Depletion region (Electric field) increases
- Velocity of the few electrons that cross the junction increases
- These electrons collide and break the covalent bonds
- Breaking of bonds sets electrons “free”

ZENER Diode

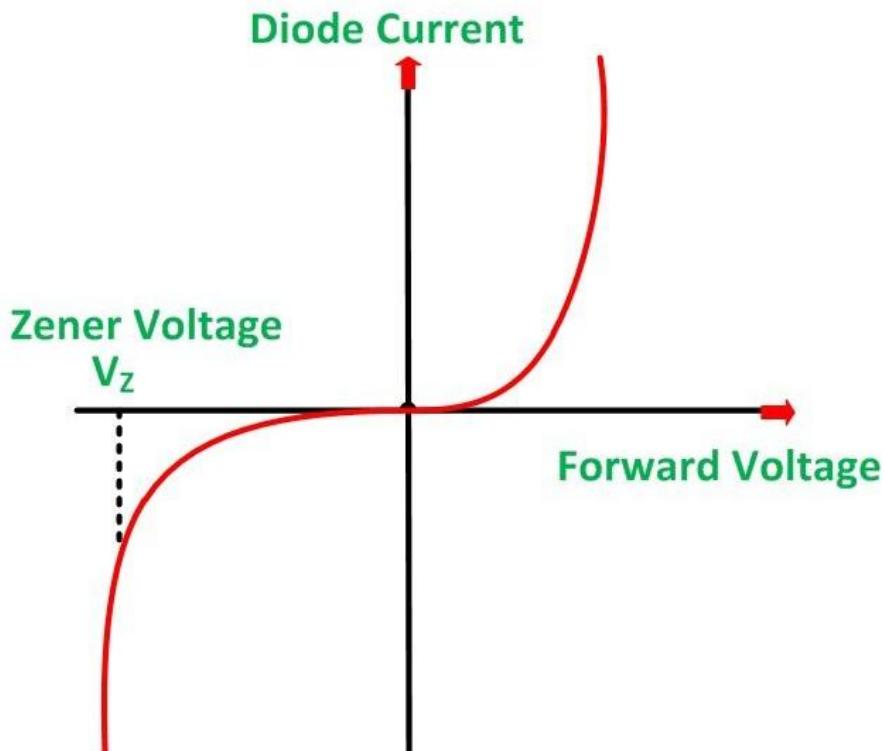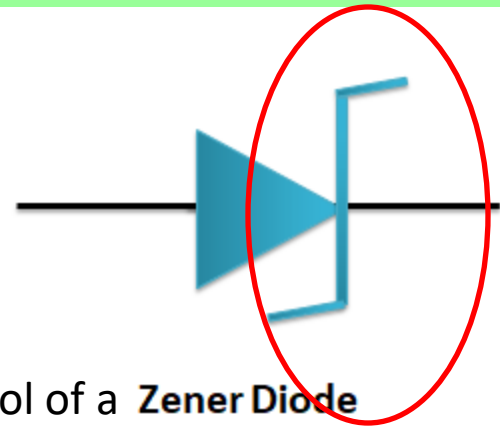- ✓ Zener diode is basically like an ordinary PN junction diode but normally operated only in reverse biased condition.
- ✓ It is a highly doped pn junction diode.




Normal diode – gets damaged at larger reverse biases, i.e. in breakdown

Zener diode – designed to sustain breakdown

Zener diode is **bi-directional device** as it can operate in forward bias as well as large reverse bias (breakdown)


ZENER Diode – *Interesting Application*

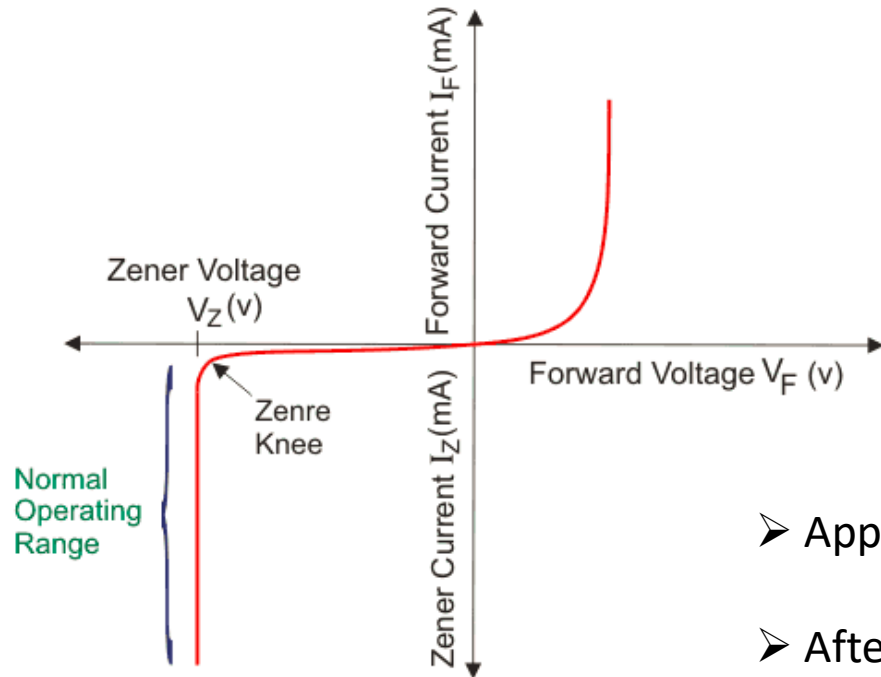

- Apply reverse voltage, negligible current flows till V_Z
- After V_Z , enormous amount of current flows in opposite direction.
- This current keeps on flowing even though there is any increase in voltage.
- Even if we increase the reverse voltage further, the voltage across the diode remains at the same value of Zener breakdown voltage!!!



ZENER Diode – *Voltage Regulation I*

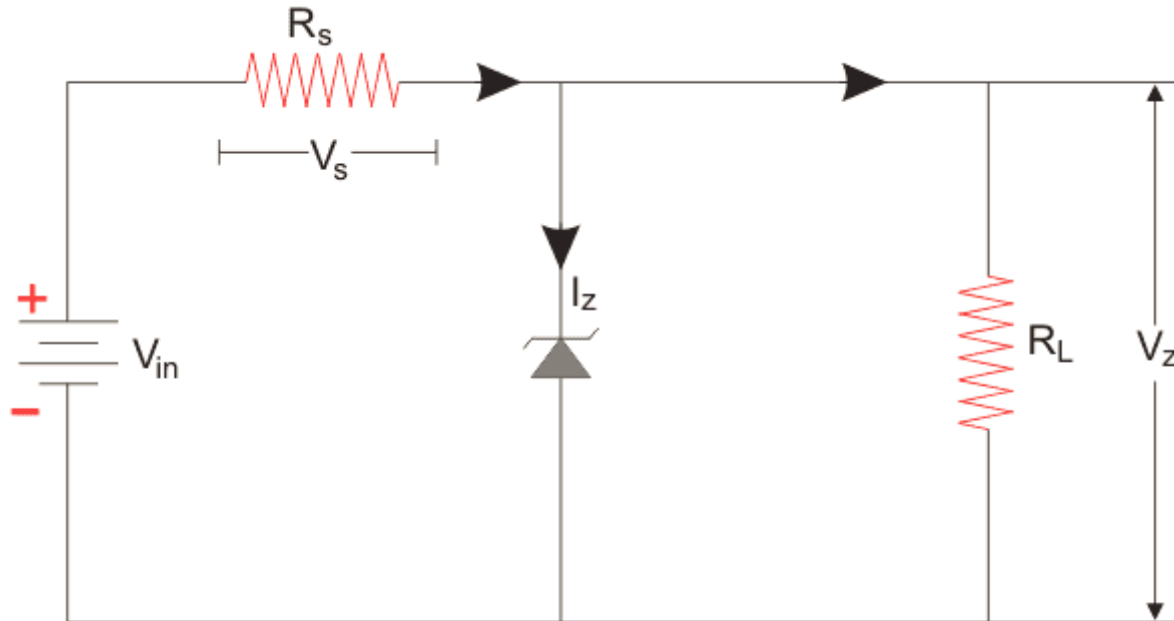- ✓ For example, we want that the voltage across a load in our circuit does not exceed, let's say, 12 volts.



- ✓ Select a Zener diode with a breakdown voltage of 12 volts and connect it across the load, ***in parallel!***
- ✓ Then even if the input voltage exceeds that value, the voltage across the load will never exceed 12 volts.

ZENER Diode – Voltage Regulation -II

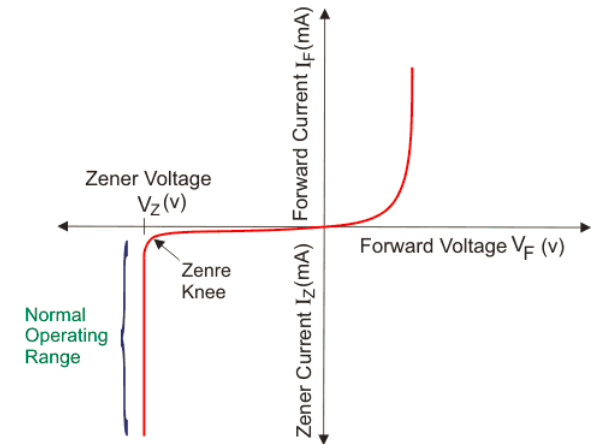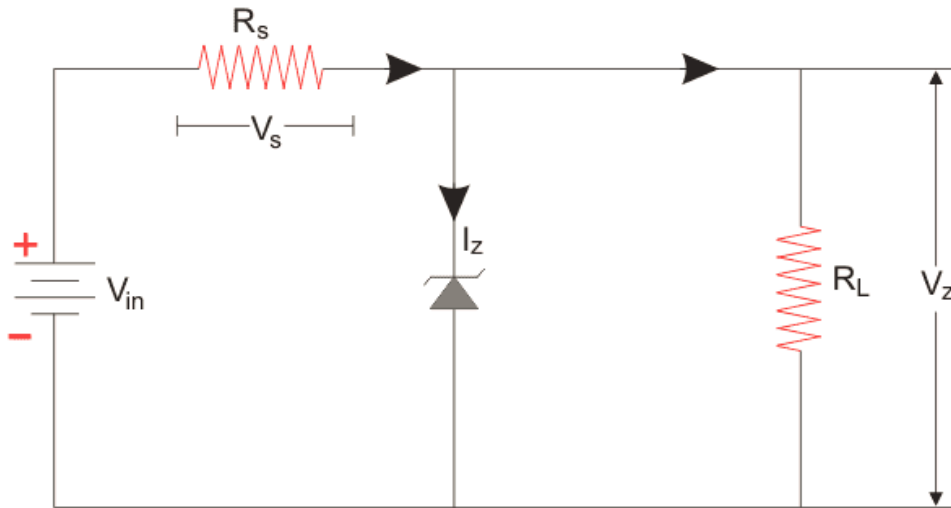

1. Zener diode – connected in **reverse bias**
2. Load and Zener diode – in parallel => voltage across both load and Zener – same
3. When the voltage across the diode exceeds the Zener breakdown voltage, a significant amount of current starts flowing through the diode.
4. The Zener diode provides a path for the current to flow and hence the load gets protected from excessive currents.

Zener diode, thus, provides two uses –

- a) Acts like a voltage regulator
- b) Prevents excessive currents from reaching the load

Acknowledgements

1. <https://electricalbaba.com/ripple-factor-half-wave-rectifier/>
2. <https://electronicspost.com/v-i-characteristics-of-p-n-junction-diode/>
3. <https://www.electrical4u.com/what-is-zener-diode/>
4. <https://www.electrical4u.com/zener-diode-as-voltage-regulator/>
5. <https://circuitglobe.com/zener-breakdown-and-avalanche-breakdown.html>
6. <https://www.electronics-tutorials.ws/power/single-phase-rectification.html>