




EEE1024: Fundamentals of Electrical and Electronics Engineering

Dr. Sanchit Khataavkar


SR FLIP FLOP

SET (S) RESET (R) flipflop

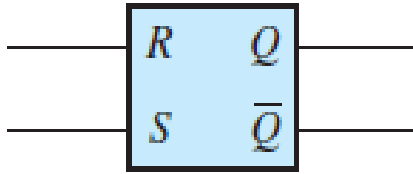

Circuit symbol

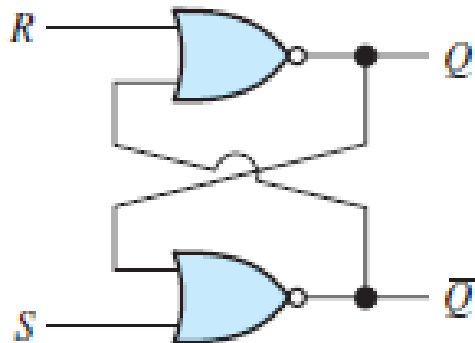- Inverter replaced by **NOR gate**
- **Latch: Unclocked flip-flop**



SR flipflop implementation

- ❖ When S is HIGH and R is LOW, \overline{Q} is forced to LOW and Q to HIGH (1)*
- ❖ When S returns to LOW, Q stays HIGH: FF remains in SET state
- ❖ Now, S is LOW and if R becomes HIGH, Q is forced to LOW
- ❖ When R returns LOW, Q stays LOW: FF remains in the RESET state
- ❖ Both R and S not allowed to remain HIGH at the same time
- ❖ With both R and S LOW, FF remembers PREVIOUS STATE

A	B	$C = A+B$	$C = \overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Truth table of NOR gate:


* When any of the i/p is 1, o/p is 0

R	S	Q_n	Normal Operation
0	0	Q_{n-1}	
0	1	1	
1	0	0	
1	1	Not allowed	


Truth table of SR flipflop

SR flipflop - Application

Eliminate effects of a switch bounce

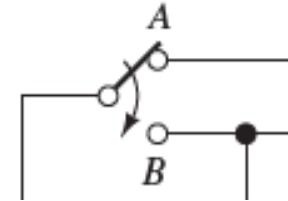

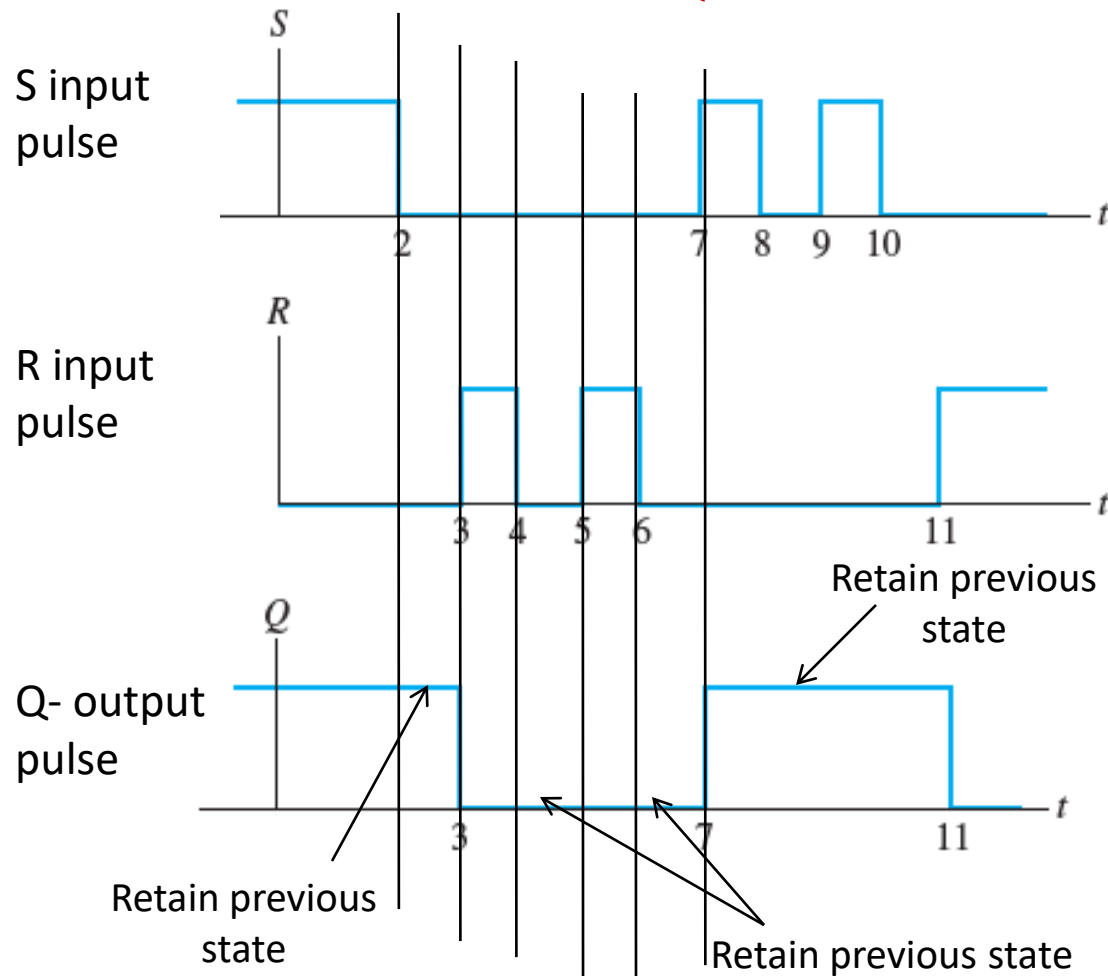Q) The waveforms present at the input terminals of a SR flip flop are shown. Sketch the waveforms for Q versus time




R	S	Q_n
0	0	Q_{n-1}
0	1	1
1	0	0
1	1	Not allowed

Edge-triggered FLIP FLOPs

SR flipflop – Un-Clocked – Latch :

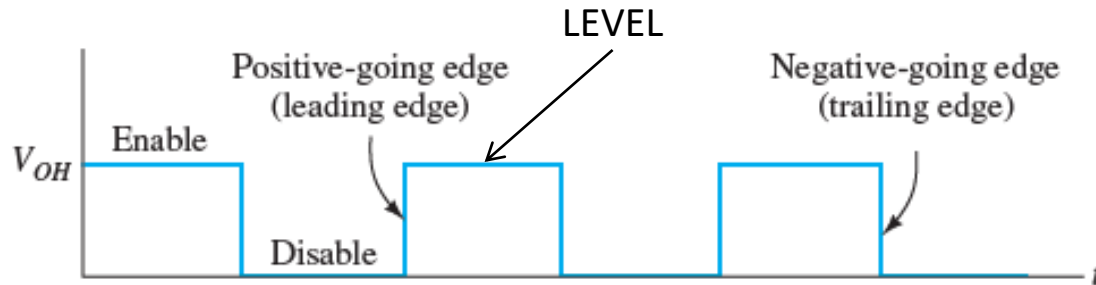Level triggered – *High clock level enables the inputs & low clock level disables it*



- Edge triggered circuits – Respond to the inputs only on the *transition* of the *clock signal*
- If clock signal is steady, i.e. either a HIGH or a LOW, inputs are disabled.
- At the clock transition, the flip-flop responds to just prior to the transition

Edge-triggered circuits

Positive Edge triggered:


Respond on **leading edge**- when clock goes from **LOW to HIGH**

Negative Edge triggered:

Respond on **trailing edge**- when clock goes from **HIGH to LOW**

D FLIP FLOP


D flip flop or Delay flip flop :

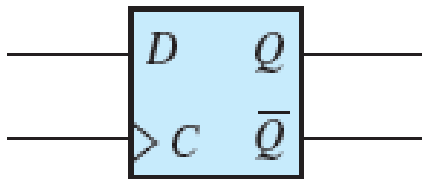

Circuit symbol

C	D	Q_n
0	\times	Q_{n-1}
1	\times	Q_{n-1}
\uparrow	0	0
\uparrow	1	1

Truth table of D flip flop

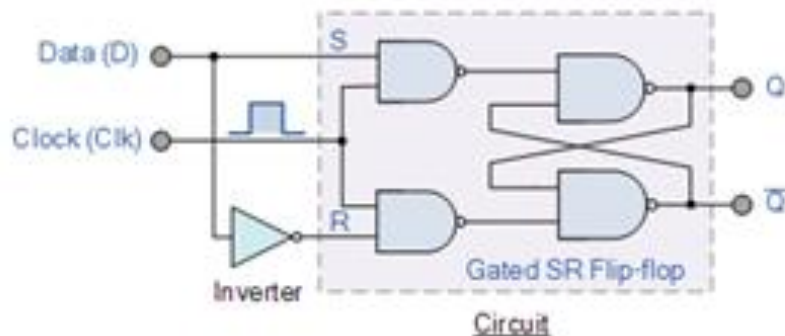

Logical Circuit implementation

➤ Output takes the value of input that was present just prior to the triggering clock transition


➤ Up arrow in truth table – indicates – positive edge of the clock signal

D FLIP FLOP - Operation


Q) The input signal to a positive edge triggered flip flop is shown.
Sketch the output Q versus time t

C	D	Q_n
0	×	Q_{n-1}
1	×	Q_{n-1}
↑	0	0
↑	1	1

Clock signal

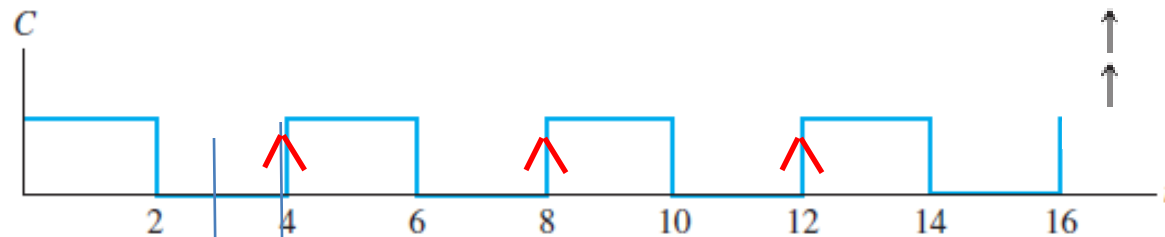


D input pulse

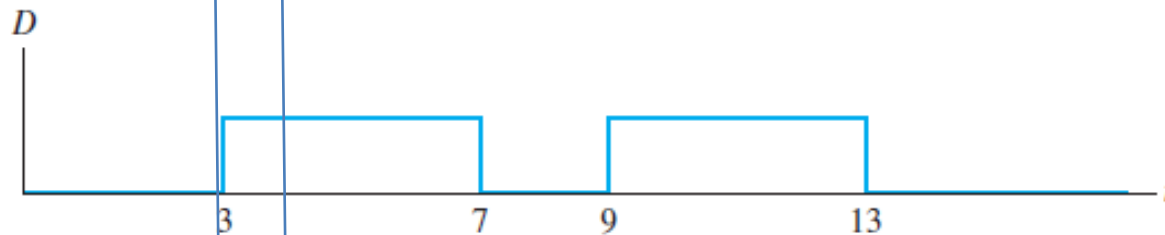


JK FLIP FLOP

JK flip flop : Most widely used!

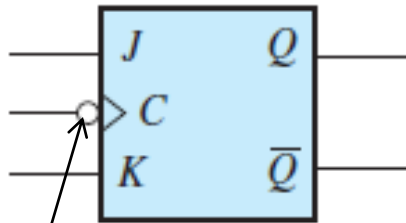

Circuit symbol

Negative edge
triggered symbol

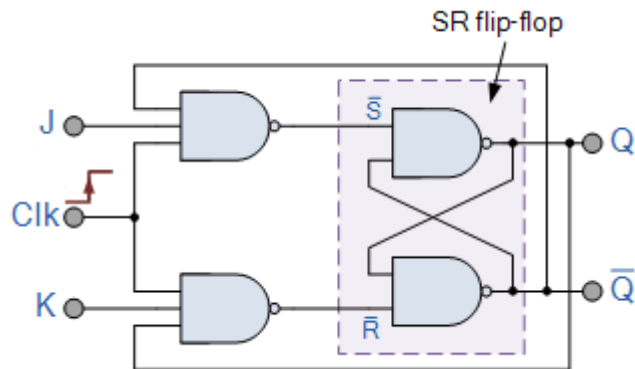

Logical Circuit implementation

C	J	K	Q_n	Comment
0	\times	\times	Q_{n-1}	Memory
1	\times	\times	Q_{n-1}	Memory
\downarrow	0	0	Q_{n-1}	Memory
\downarrow	0	1	0	Reset
\downarrow	1	0	1	Set
\downarrow	1	1	\bar{Q}_{n-1}	Toggle

Truth table of JK flip flop


➤ Operation similar to an SR flipflop except that when both inputs J & K are HIGH, state changes on the next negative going clock pulse

➤ When both J & K are HIGH, output of JK flipflop **toggles** on each cycle of clock – Low to High on one –ve edge transition and again High to Low on the next.

JK FLIP FLOP – Application - COUNTER


Counters – used to count the pulses of the input signal – IMP part of the ALU

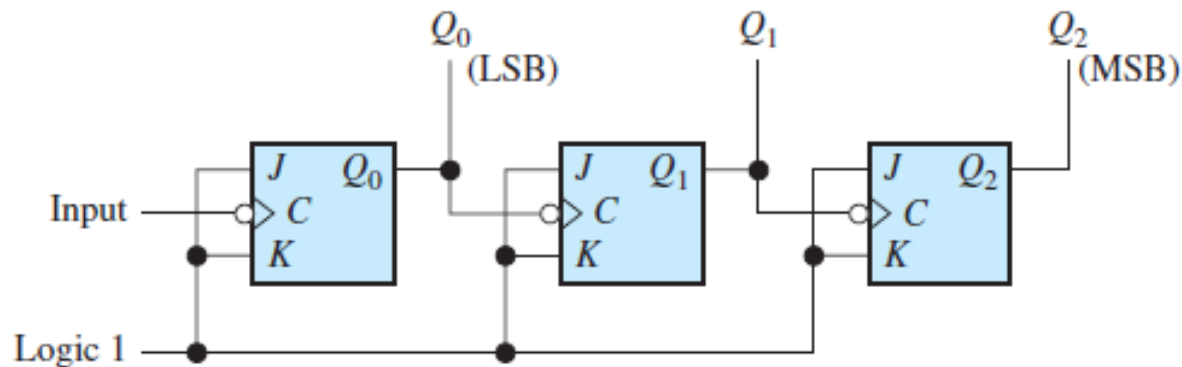RIPPLE COUNTER: Cascade of J-K flip flops



- When both inputs are HIGH, Q output toggles, in a J-K flip flop (FF)
- Input pulses to be counted are connected to input of the 1st JK FF and output of the 1st JK FF is connected to the input of the 2nd JK FF - *Cascading*

RIPPLE COUNTER Waveforms

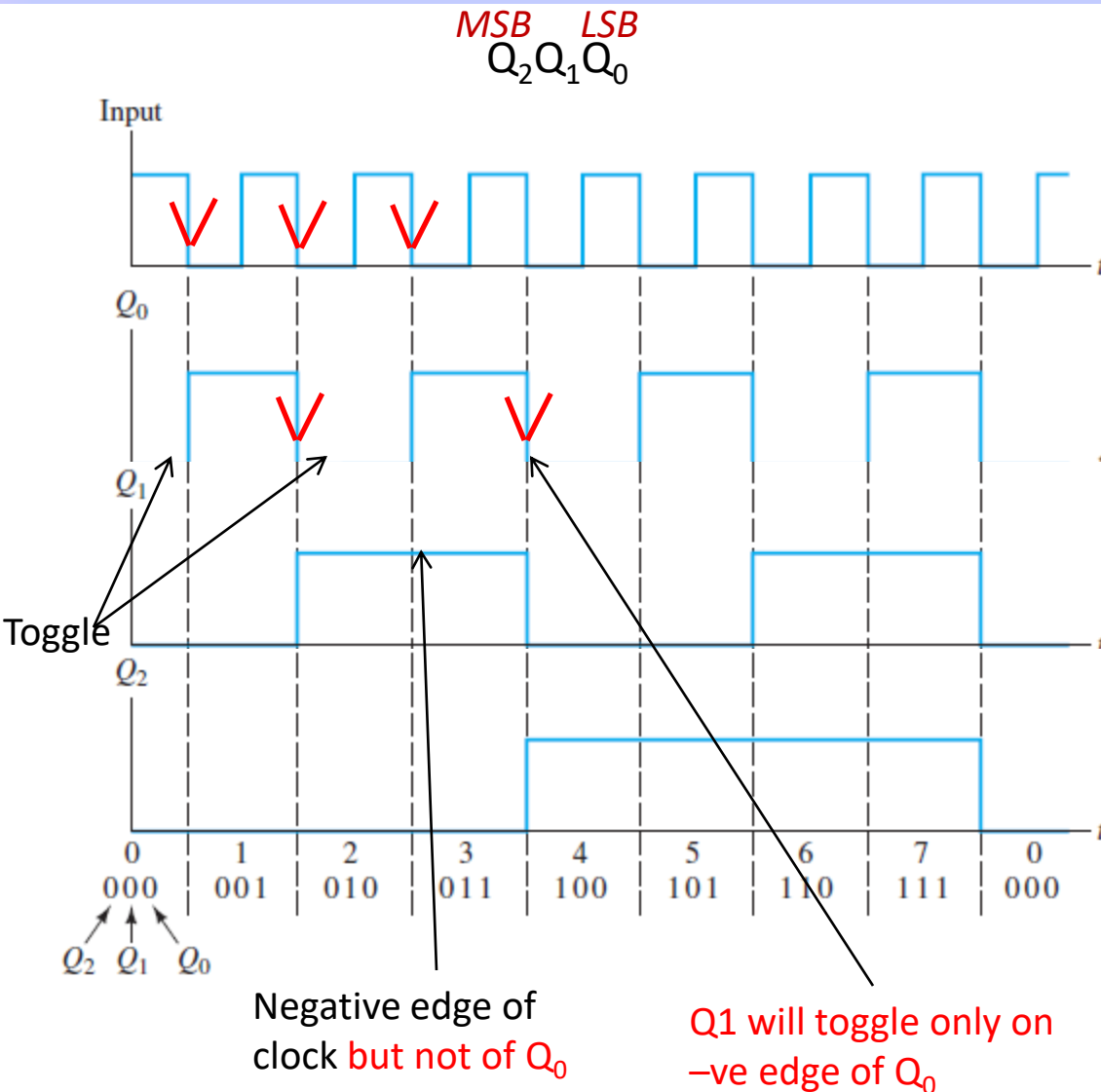

▪ Assume – all FF's in the Reset state ($Q=0$)

▪ When the falling edge of the 1st i/p pulse occurs, Q_0 changes to o/p - **1**

▪ On the falling edge of the 2nd i/p pulse, Q_0 toggles back to **0**

▪ Falling input to 2nd stage, makes Q_1 go HIGH (**1**)

• After 7 pulses, the counter is in 111 state & on the 8th pulse, counter returns to **0**.

Why doesn't Q_1 toggle here ?


Sinusoidal Voltage and current

Phasors

Complex Impedances

Steady state analysis

A.C. Power Calc.

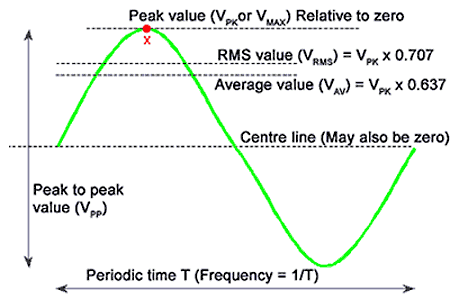

*Peak,
Average,
RMS
For V, I*

*Definition,
Addition*

Z_C and Z_L

*KCL, KVL,
Node,
Mesh*

*Power
Triangle
and its
terms*

MODULE - 2

Number Systems

Conversions

Logic gates Boolean algebra

*Boolean
expressions +
LAWS*

Special Combi circuits

*Half adder
Full adder*

Special Combi circuits

*MUX,
DEMUX*

Seq. circuits

*Flip flops-
SR FF,
D FF,
JK FF,
& its
applications*

Acknowledgements

1. Allan R. Hambley, 'Electrical Engineering - Principles & Applications, Pearson Education, First Impression, 6/e, 2013
2. https://www.electronics-tutorials.ws/sequential/seq_4.html