




EEE1024: Fundamentals of Electrical and Electronics Engineering

Dr. Sanchit Khataavkar

Mesh current method - 1

Example 1

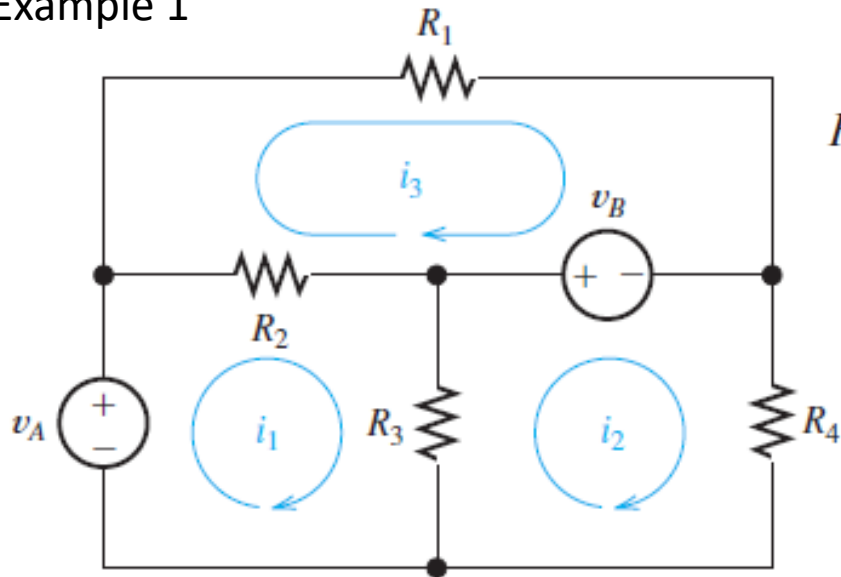

$$R_2(i_1 - i_3) + R_3(i_1 - i_2) - v_A = 0 \quad \text{KVL @ Mesh 1}$$

$$R_3(i_2 - i_1) + R_4 i_2 + v_B = 0 \quad \text{KVL @ Mesh 2}$$

$$R_2(i_3 - i_1) + R_1 i_3 - v_B = 0 \quad \text{KVL @ Mesh 3}$$


Matrix form

$$\begin{aligned}(R_2 + R_3)i_1 - R_3i_2 - R_2i_3 &= v_A \\ -R_3i_1 + (R_3 + R_4)i_2 &= -v_B \\ -R_2i_1 + (R_1 + R_2)i_3 &= v_B\end{aligned}$$

$$\begin{bmatrix} (R_2 + R_3) & -R_3 & -R_2 \\ -R_3 & (R_3 + R_4) & 0 \\ -R_2 & 0 & (R_1 + R_2) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} v_A \\ -v_B \\ v_B \end{bmatrix}$$

Mesh current method - 2

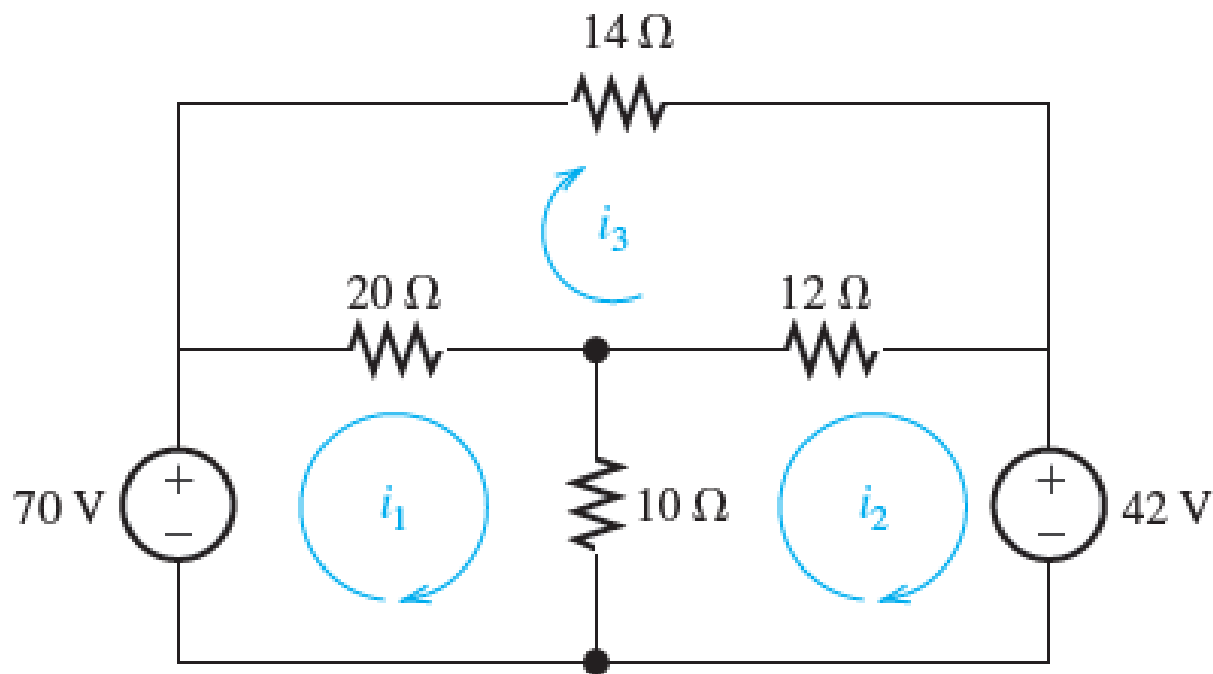Example 2: Solve for currents in each element of this circuit



KVL @ Mesh 1: $20(i_1 - i_3) + 10(i_1 - i_2) - 70 = 0 \rightarrow 30i_1 - 10i_2 - 20i_3 = 70$

KVL @ Mesh 2: $10(i_2 - i_1) + 12(i_2 - i_3) + 42 = 0 \rightarrow -10i_1 + 22i_2 - 12i_3 = -42$

KVL @ Mesh 3: $20(i_3 - i_1) + 14i_3 + 12(i_3 - i_2) = 0 \rightarrow -20i_1 - 12i_2 + 46i_3 = 0$

Mesh current method - 3

Example 2 continued

$$30i_1 - 10i_2 - 20i_3 = 70$$

$$-10i_1 + 22i_2 - 12i_3 = -42$$

$$-20i_1 - 12i_2 + 46i_3 = 0$$

$$\begin{bmatrix} 30 & -10 & -20 \\ -10 & 22 & -12 \\ -20 & -12 & 46 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 70 \\ -42 \\ 0 \end{bmatrix}$$

Method 1: Calculator

Method 2: Manual calculations

Method 3: MATLAB!

```
>> R = [30 -10 -20; -10 22 -12; -20 -12 46];
```

```
>> V = [70; -42; 0];
```

```
>> I = R\V
```

```
I =  
 4.0000  
 1.0000  
 2.0000
```


$$i_1 = 4A$$

$$i_2 = 1A$$

$$i_3 = 2A$$

Current through $10\Omega = i_{10}$

$$i_2 - i_1 = 1 - 4 = -3A$$

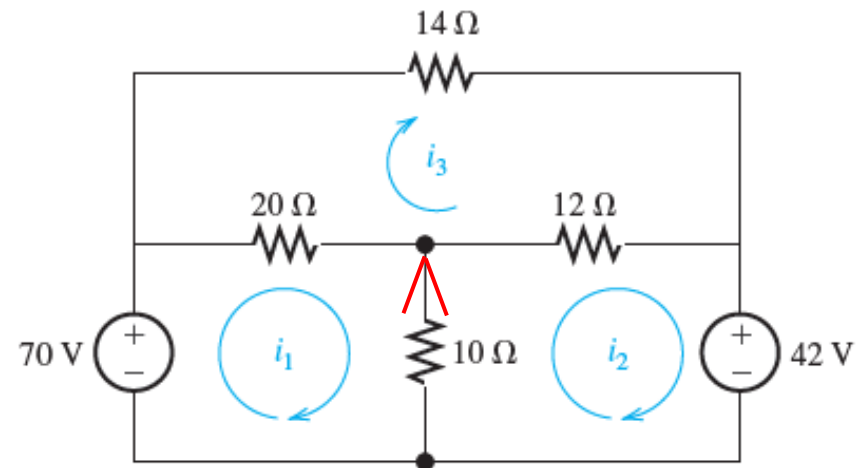

Mesh current method - 2

Example 2: a) Find the current through the $10\ \Omega$ resistor of the given circuit.

b) Find the power supplied by 42V voltage source


c) Find the power delivered to the $10\ \Omega$ resistor using mesh currents analysis in the figure shown

$$i_1 = 4\text{ A}$$

$$i_2 = 1\text{ A} \quad i_2 - i_1 = 1 - 4 = -3\text{ A}$$

$$i_3 = 2\text{ A}$$
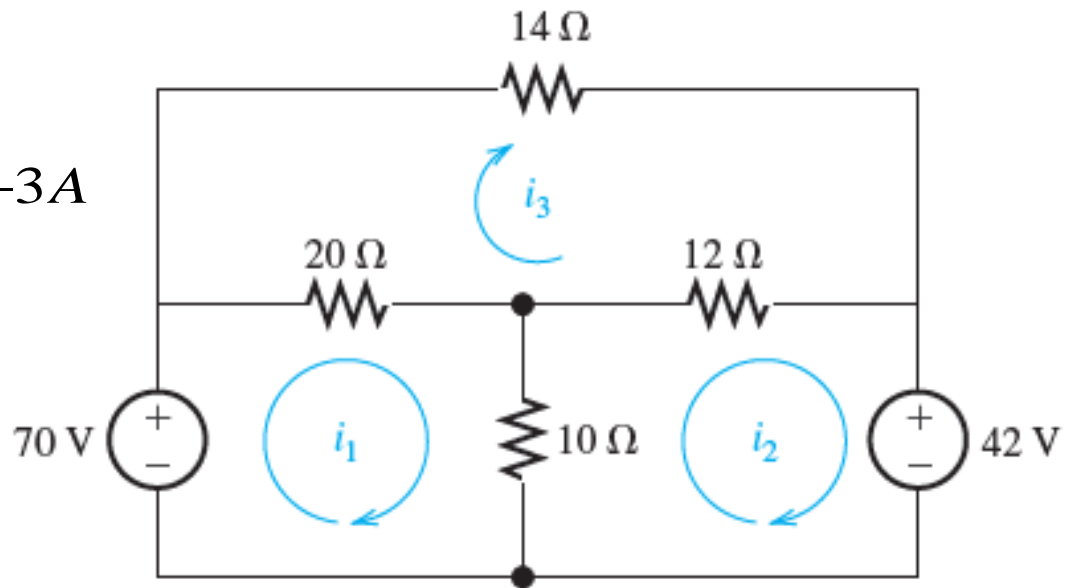
$$\begin{aligned} \text{b) } P &= V * i_2 \\ &= 42\text{ W} \end{aligned}$$




c) Either mesh 1 or mesh 2 can be used.

$$P = V(i_1 - i_2) \quad P = (i_1 - i_2)^2 R$$

$$\begin{aligned} P_{10} &= (4 - 1)^2 \times 10 \\ &= 90\text{ W} \end{aligned}$$

Mesh current method – *Current Sources*

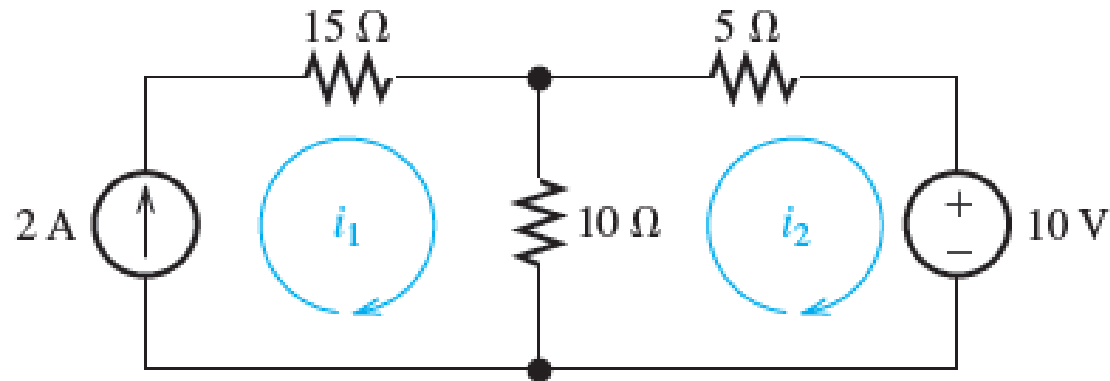

@ Mesh 1,

$$i_1 = 2 \text{ A}$$

@ Mesh 2,


$$10(i_2 - i_1) + 5i_2 + 10 = 0$$

$$10i_2 - 20 + 5i_2 = -10$$

$$15i_2 = 10 \quad \text{or} \quad i_2 = 0.67 \text{ A}$$


DO NOT APPLY KVL to LOOP/MESH having a CURRENT SOURCE!

THEVENIN'S Theorem

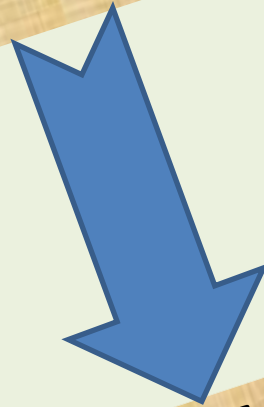

**MAXIMUM POWER TRANSFER
Theorem -**

Need for Thevenin's Theorem

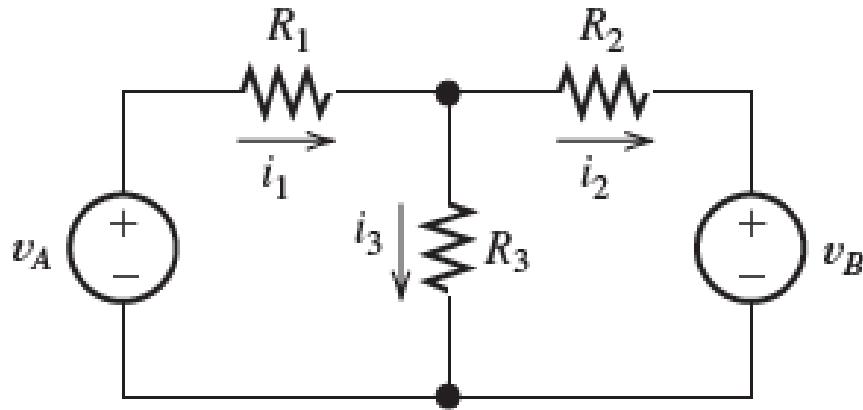

➤ Find V across R_3

➤ Find V across terminal A and B and current through R_3 for 50 values of R_3

??

Thevenin's Theorem

Léon Charles Thévenin

Complicated circuit – segregated into fixed part and variable part

Entire fixed part of a network is replaced by -
an **equivalent voltage source** and a **series resistor**,
called as *Thevenin Equivalent Circuit*



“ A linear bi-directional two terminal network can be replaced by an equivalent network consisting of a voltage source V_{th} (or V_t) connected in series with a resistor R_{th} (or R_t)”


Thevenin Equivalent Circuit

Network can be replaced by an equivalent network consisting of a voltage source V_t connected in series with a resistor R_t

What is V_t and R_t ?


V_t – Open Circuit voltage at the terminals

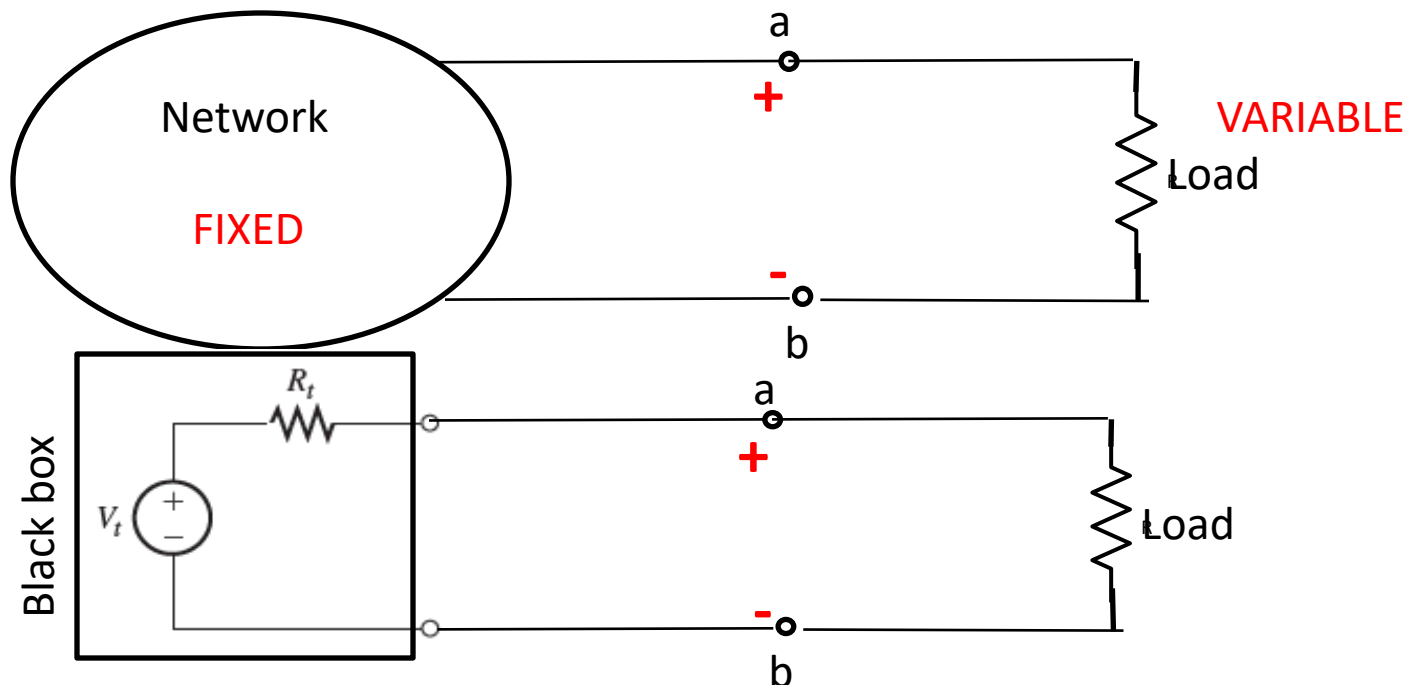R_t – Input/ equivalent resistance at the terminals
when sources (independent) are turned off



Thevenin Equivalent Circuit


Open-Circuit terminals

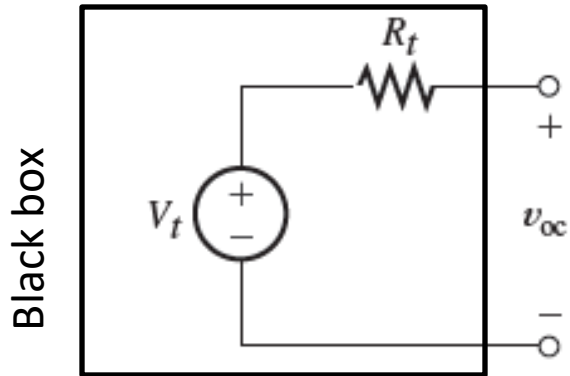

No current flows through this circuit

$$V_t = V_{oc}$$

Short-Circuit terminals

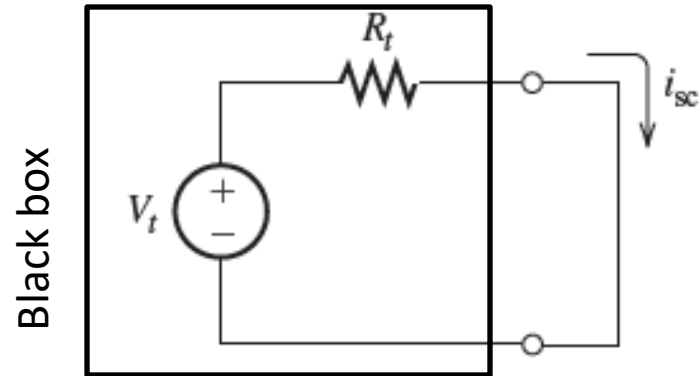

Current flows through this circuit & voltage across terminals is zero


$$R_t = \frac{V_t}{i_{sc}}$$

$$R_t = \frac{V_{oc}}{I_{sc}}$$

Finding Thevenin Resistance Directly

Zeroing method!

Zeroing a voltage source

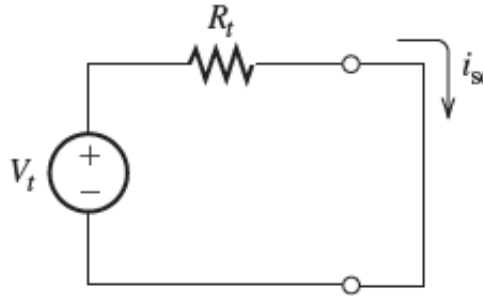


Reduce voltage to zero




SHORT-CIRCUIT

Zeroing a current source

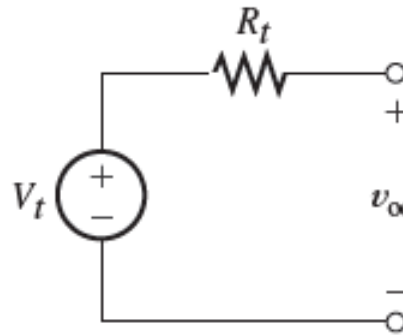


Reduce current to zero

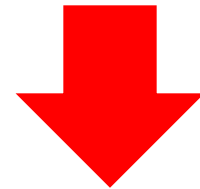


OPEN-CIRCUIT

Finding Thevenin Resistance Directly

Thevenin equivalent:
Original network

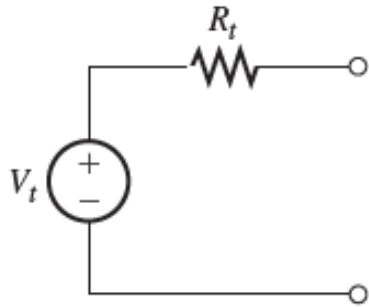


After Zeroing

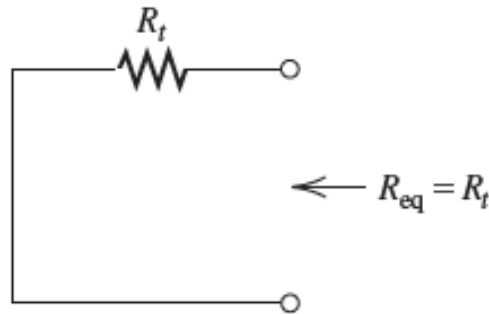

To find R_t ;


1. Zero sources in original
2. Compute R between terminals

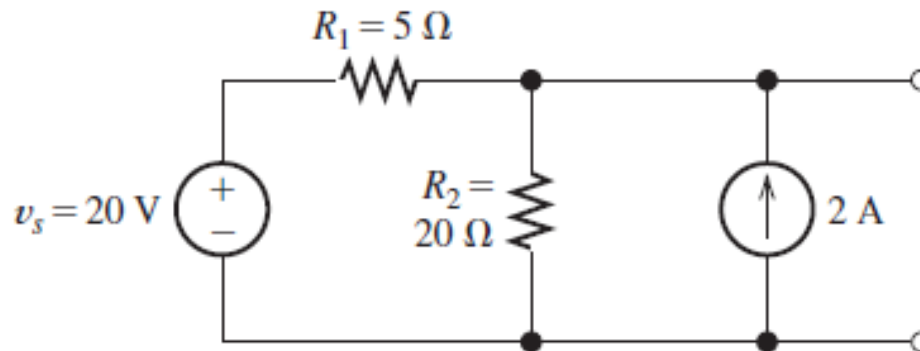Example 1: Find Thevenin resistance, short circuit current and Thevenin equivalent circuit for the circuit shown below




Thevenin Resistance - Example

Original circuit

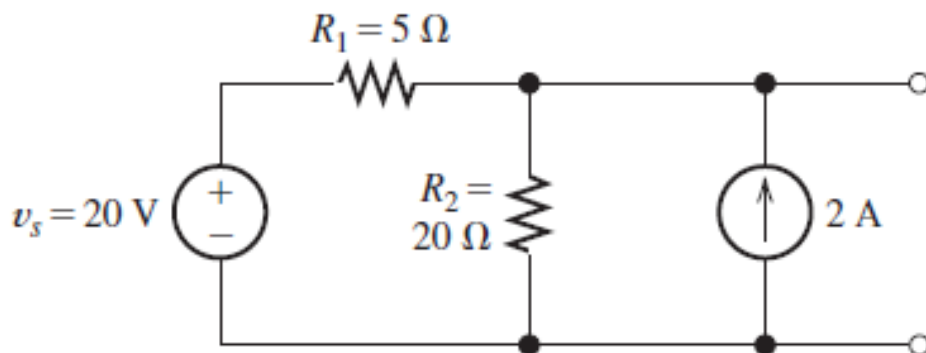


Circuit with
sources zeroed

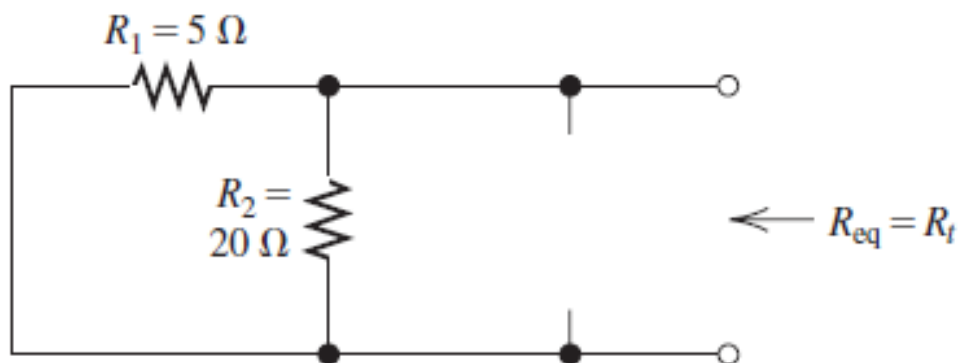

$$R_t = R_{eq} = \frac{1}{1/R_1 + 1/R_2} = \frac{1}{1/5 + 1/20} = 4\ \Omega$$

Thevenin Equivalent Circuit - Example

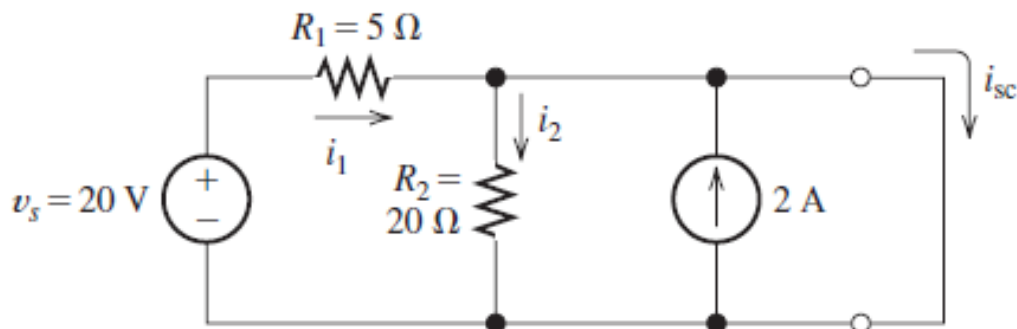

KCL @ Node joining top ends of R_2 and 2A source

$$i_1 + 2 = i_2 + i_{sc}$$

$$i_{sc} = 6 \text{ A.}$$


$$R_t = \frac{V_{oc}}{I_{sc}} \quad V_t = R_t i_{sc} = 4 \times 6 = 24 \text{ V}$$

In short circuit,
V across $R_2 = 0 \Rightarrow$
I through $R_2 = 0$

$$i_2 = 0$$

$$V_{R1} = 20 \text{ V}$$
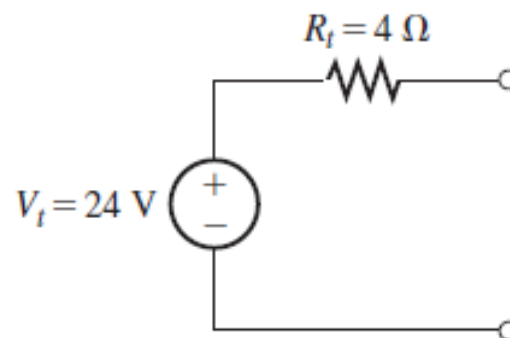
$$i_1 = \frac{v_s}{R_1} = \frac{20}{5} = 4 \text{ A}$$



Acknowledgements

1. H. Hayt, J.E. Kemmerly and S. M. Durbin, 'Engineering Circuit Analysis', 6/e, Tata McGraw Hill, New Delhi, 2011
2. Allan R. Hambley, 'Electrical Engineering - Principles & Applications, Pearson Education, First Impression, 6/e, 2013