




EEE1024: Fundamentals of Electrical and Electronics Engineering

Dr. Sanchit Khataavkar

Module 3

 1. Number Systems - Conversions
2. Logic Gates
3. Boolean Algebra
4. Computer Organization (Memory)
5. HA, FA, Mux, Demux
6. Sequential - Flip flops, Counters

SPECIAL Circuits – Half Adder & Full Adder



Performs
addition of
2 bits



Performs
addition of
3 bits

Digital Circuits –
Addition of 2 **binary** digits



A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

1
0 1 0 0 0 0 0 1
0 1 0 0 1 0 1 1

1 0 0 0 1 1 0 0


HALF ADDER

Binary Addition

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Truth table of XOR gate

A	B	$C = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

 


Truth table of AND gate

A	B	$C = AB$
0	0	0
0	1	0
1	0	0
1	1	1

HALF ADDER(2 bits)

Logic Circuit: Realization of Half Adder

 

Truth table

Inputs		Outputs	
A	B	Sum ($A \oplus B$)	Carry (AB)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- Binary addition: If there is any **Carry** in the input?
- Half adder cannot do the addition then !!!
- Which is why it is called HALF adder as only half of the binary addition is done

FULL ADDER (3 bits)


- The additional 3rd bit – Carry from previous operation - C_{IN}
- Two outputs – Sum – S (final) and Carry - C_{OUT}

Inputs			Outputs	
A	B	C_{IN}	S	C_{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Realize a logic circuit?

- 1 XOR, 3 AND, 1 OR
- 2 Half-adders and an OR gate

FULL ADDER (3 bits)

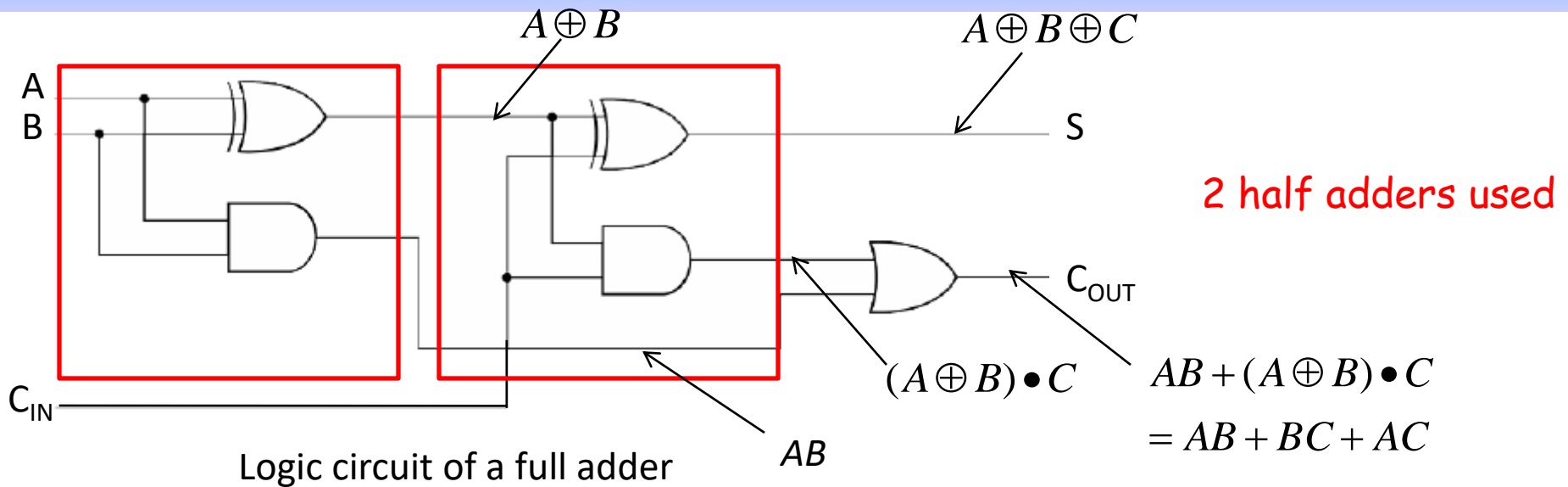

- First half adder produces a partial sum
- This sum is connected as input to 2nd half adder along with C_{IN} which produces final sum S
- Carry outputs of the 2 half adders connected to an OR gate which produces final carry C_{OUT}


Multiplexer and De-multiplexer

Multiplexer (MUX) - “Many-to-one” digital switch

- A combinational logic circuit has **multiple inputs** (sources) and a **single output** (destination).
- **Only one input is allowed at a particular time** to be connected to the output.
- **SELECT Lines** control which line (signal) is connected to the output


MUX Types

 - 2-to-1 (1 select line)
- 4-to-1 (2 select lines)
- 8-to-1 (3 select lines)
- 16-to-1 (4 select lines)




Block diagram

A typical application of MUX

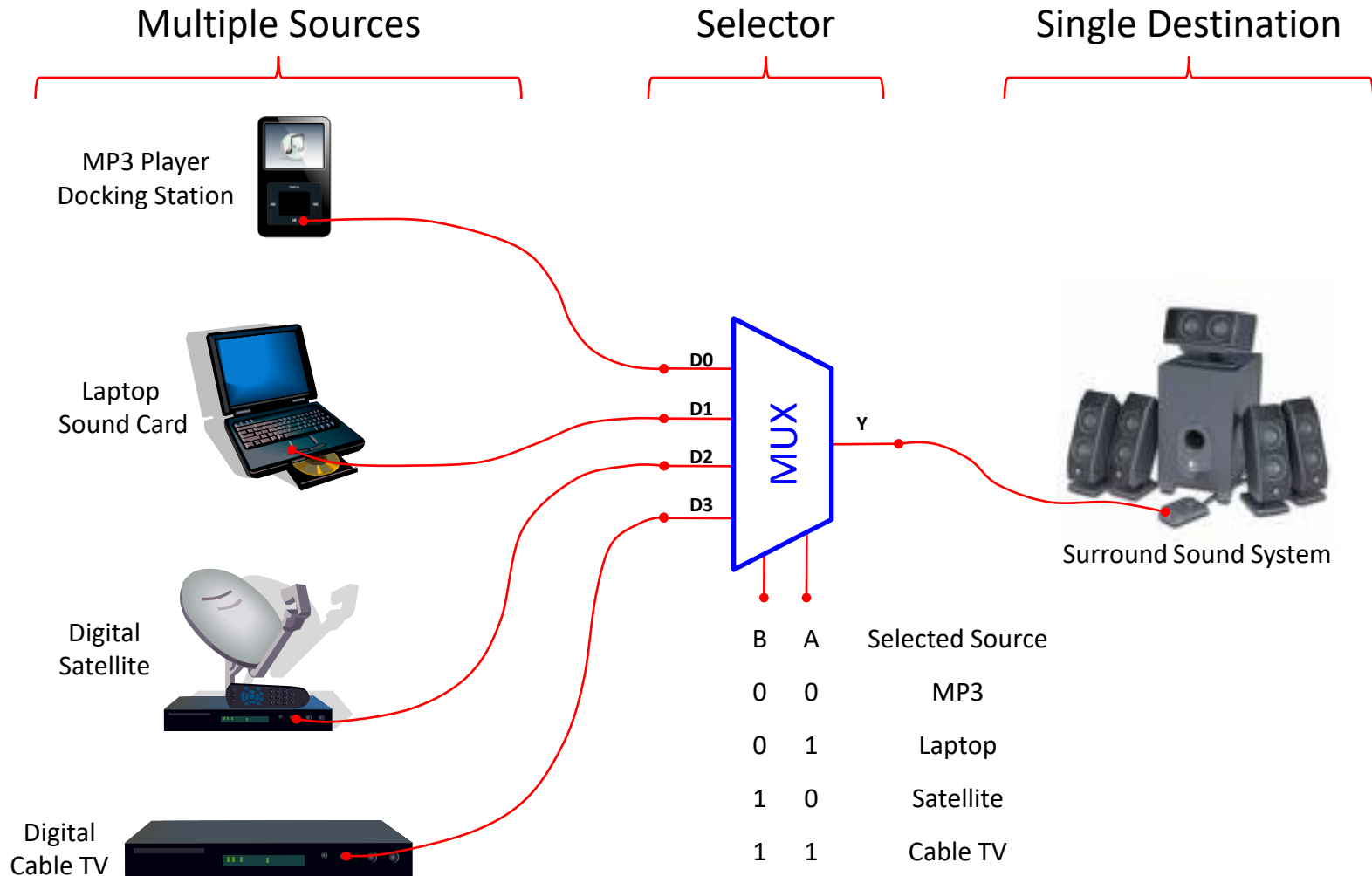

2:1 Multiplexer (MUX)


Block diagram

 

Truth table

S0	D0	D1	Out
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Logical circuit

 


➤ When S0 is 0, output reflects values of D0

➤ When S0 is 1, output reflects values of D1

4:1 Multiplexer (MUX)


Block diagram

 


Truth table

B	A	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

Logical circuit

 

4:1 Multiplexer waveforms

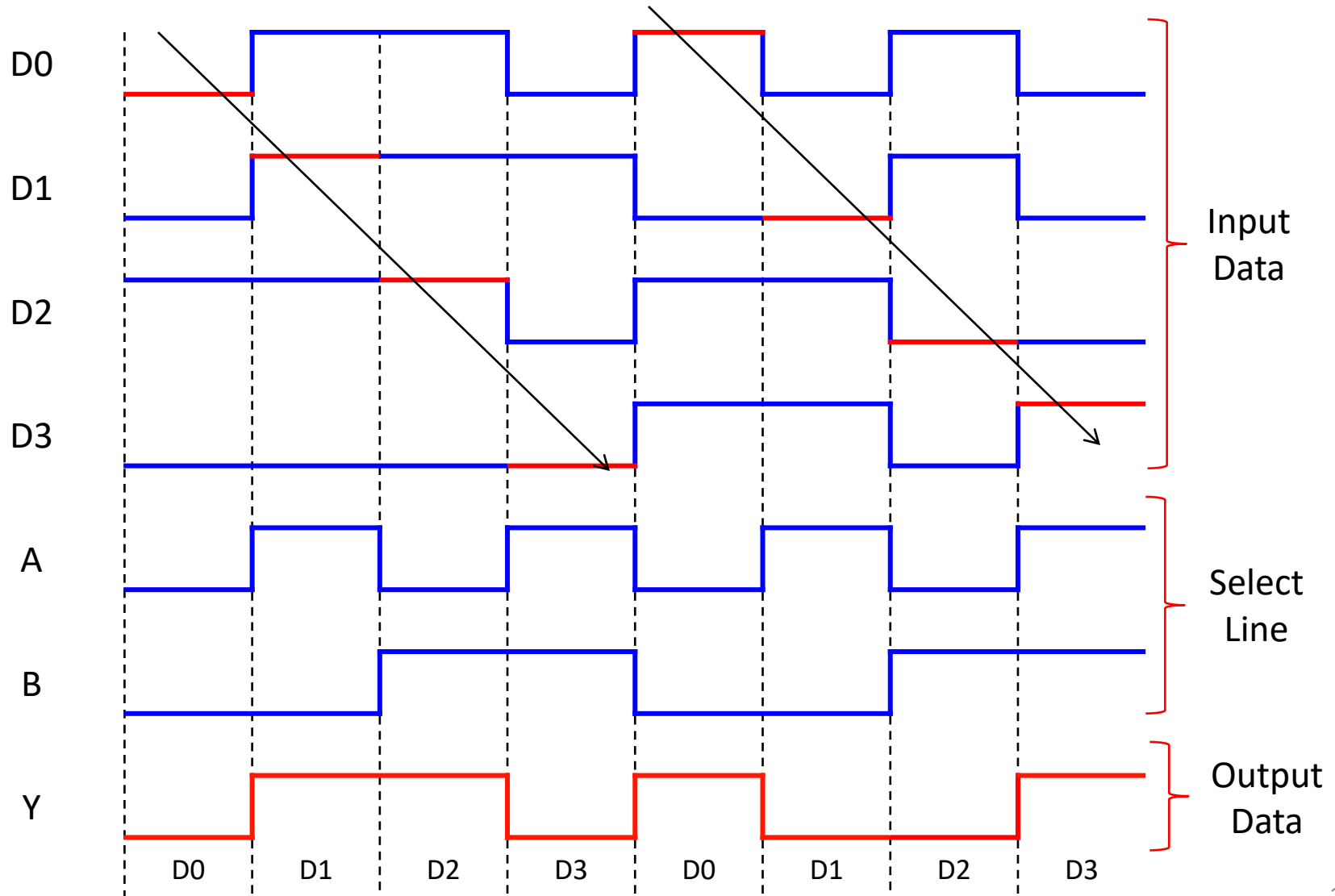


De-multiplexer

De-multiplexer (DEMUX) - “One-to-many” digital switch


- A combinational logic circuit which has a **single input** (source) and a **multiple outputs** (destinations)
- **SELECT Lines** control which line (signal) is connected to the output

DEMUX Types

 - 1-to-2 (1 select line)
- 1-to-4 (2 select lines)
- 1-to-8 (3 select lines)
- 1-to-16 (4 select lines)




A typical application of DEMUX

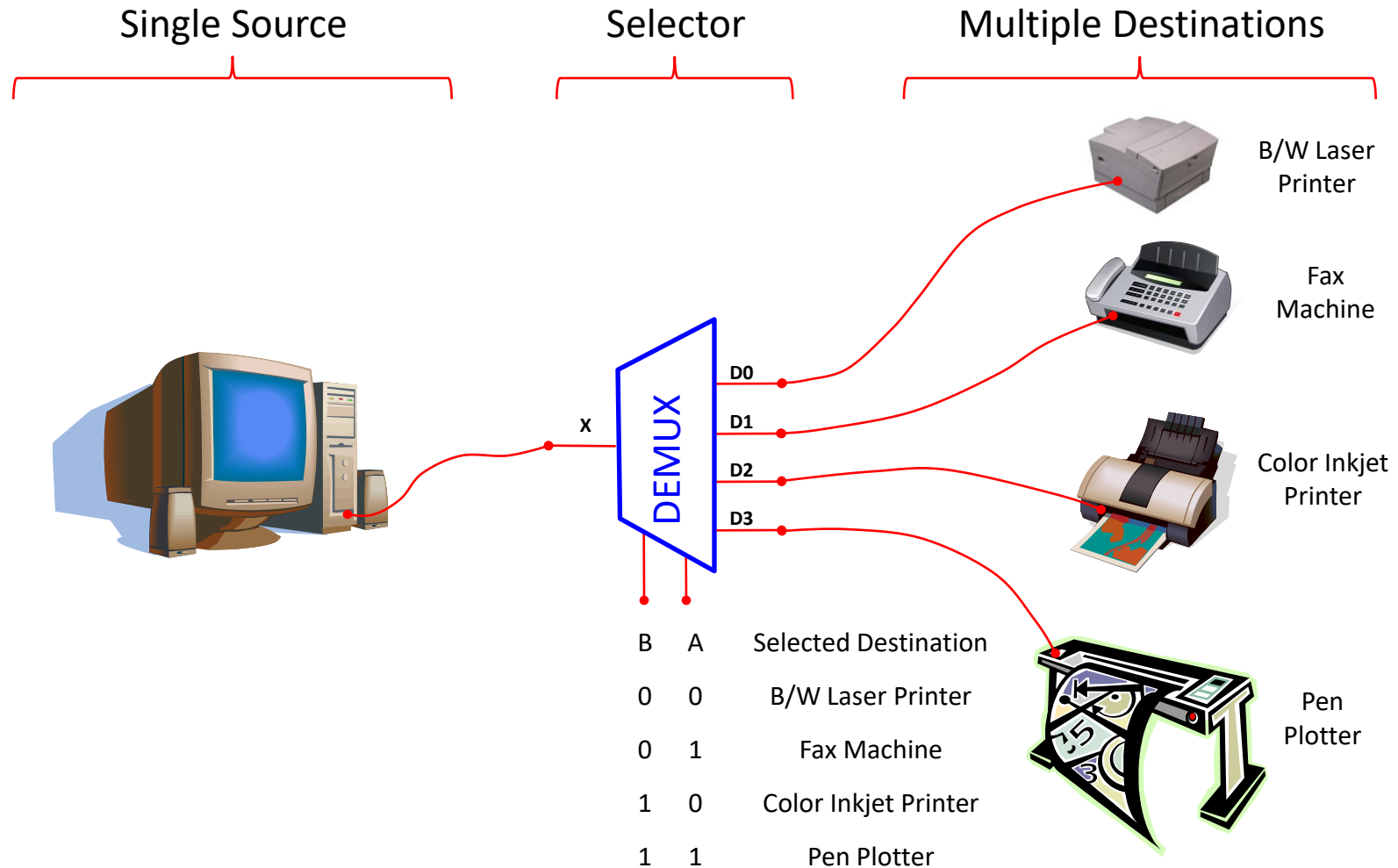

1:2 De-multiplexer (DEMUX)

Block diagram


1 input line

 

Truth table

S_0	D	Out₁	Out₂
0	0	0	0
0	1	1	0
1	0	0	0
1	1	0	1

Logical circuit

 


➤ When S_0 is 0, input **D** is connected to **Out₁**

➤ When S_0 is 1, input **D** is connected to **Out₂**

1:4 De-multiplexer (DEMUX)


Block diagram

 


Truth table

B	A	D0	D1	D2	D3
0	0	Y	0	0	0
0	1	0	Y	0	0
1	0	0	0	Y	0
1	1	0	0	0	Y

Logical circuit

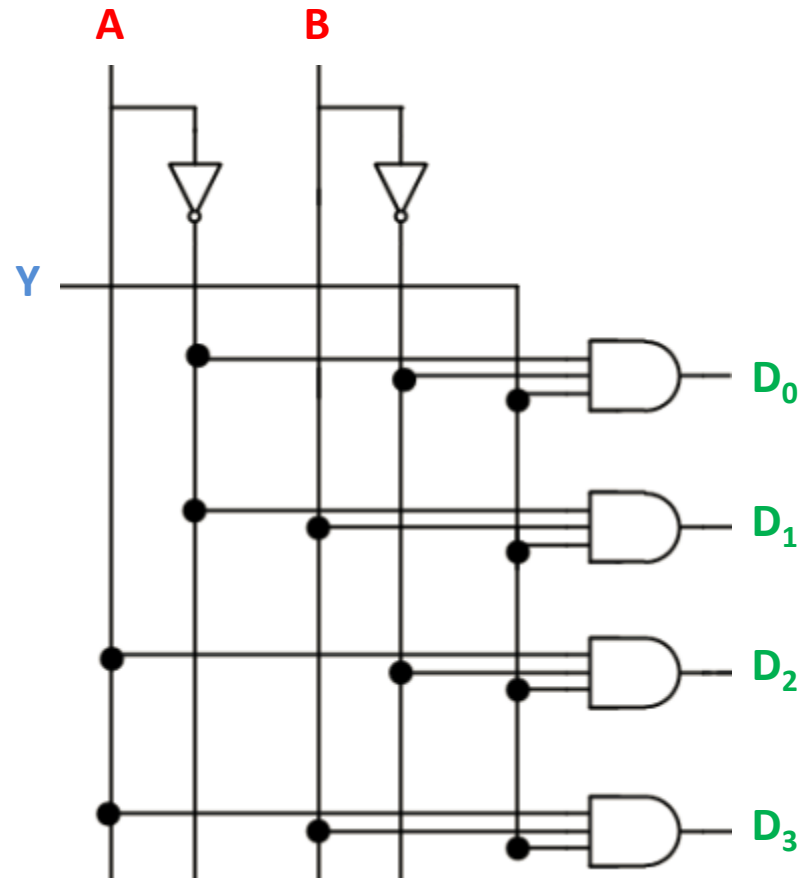


1:4 De-multiplexer waveforms

 


SEQUENTIAL CIRCUITS

Sequential circuits

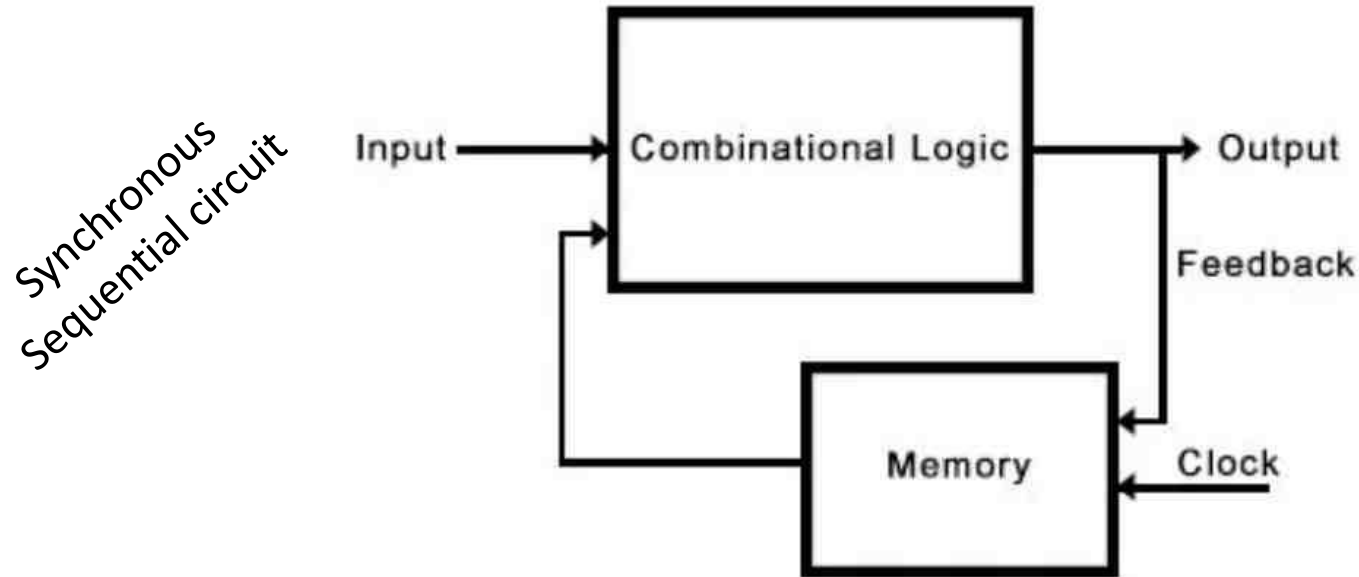

 - MEMORY – remember past values
- CLOCK signal – Periodic logic-1 pulses




Asynchronous sequential circuits

Sequential circuits – Flip flops

Basic building block of sequential circuits – FLIP FLOP (FF)

- Two stable operating states possible in a flipflop, 1 bit of information (0,1) can be stored
- Different types – based on how the clock and input signals control the state (o/p) of the flipflop

Simplest FF – using inverters

 

❖ O/p of top inverter – HIGH, o/p of bottom inverter – LOW.

❖ Hence labeled as \overline{Q}

❖ O/p of top inverter – LOW, o/p of bottom inverter – HIGH.

❖ Any of these states possible and then can remain in this state indefinitely

Acknowledgements

1. Allan R. Hambley, 'Electrical Engineering - Principles & Applications, Pearson Education, First Impression, 6/e, 2013
2. <https://www.circuitstoday.com/half-adder>
3. www.geekyshows.com
4. <http://razorjr.files.wordpress.com/2013/07>
5. <https://www.electronicshub.org/multiplexer-and-demultiplexer/>
6. <https://circuitdigest.com/tutorial/what-is-multiplexer-circuit-and-how-it-works>
7. <https://electricalfundablog.com/demultiplexer-demux/>