

Ex. No. 6

Date:25.10.2020

Design of Single phase Half wave and Full wave Rectifiers

Aim:

To design a circuit to perform single-phase half wave and full wave rectifier using OrCAD Pspice software.


Apparatus/Tool required:

ORCAD / PSpice simulator -> **Diode Library - D1N4002/4007,**
Source Library – Vsin & Ground (GND) – 0(zero)
Analog Library – R
Simulation Settings: **Analysis Type - Time Domain**


Run to time: 40ms (for 2 cycles)

Circuit Diagram:

Single phase Half – wave Rectifier

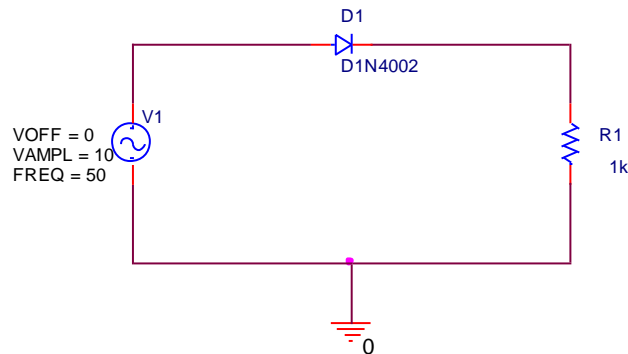

Single phase Full – Wave Rectifier

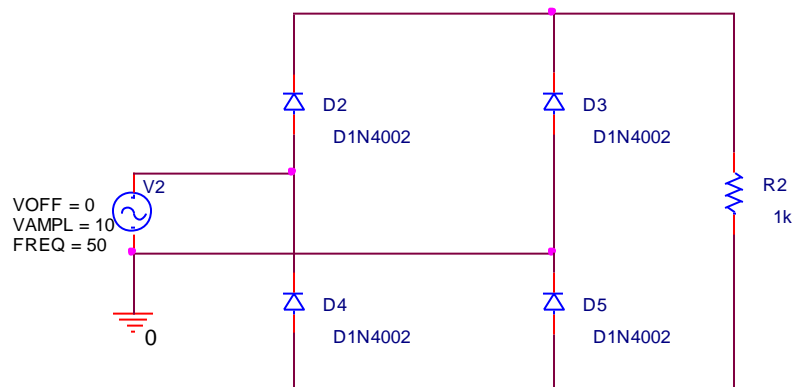

Theory:



Half – wave Rectifier:

A half wave rectifier is defined as a type of rectifier that only allows one half-cycle of an AC voltage waveform to pass, blocking the other half-cycle.



Full – wave Rectifier:

The circuits which rectify both the positive and negative half cycles of an input alternating waveform, the rectifiers are referred as full wave rectifiers.

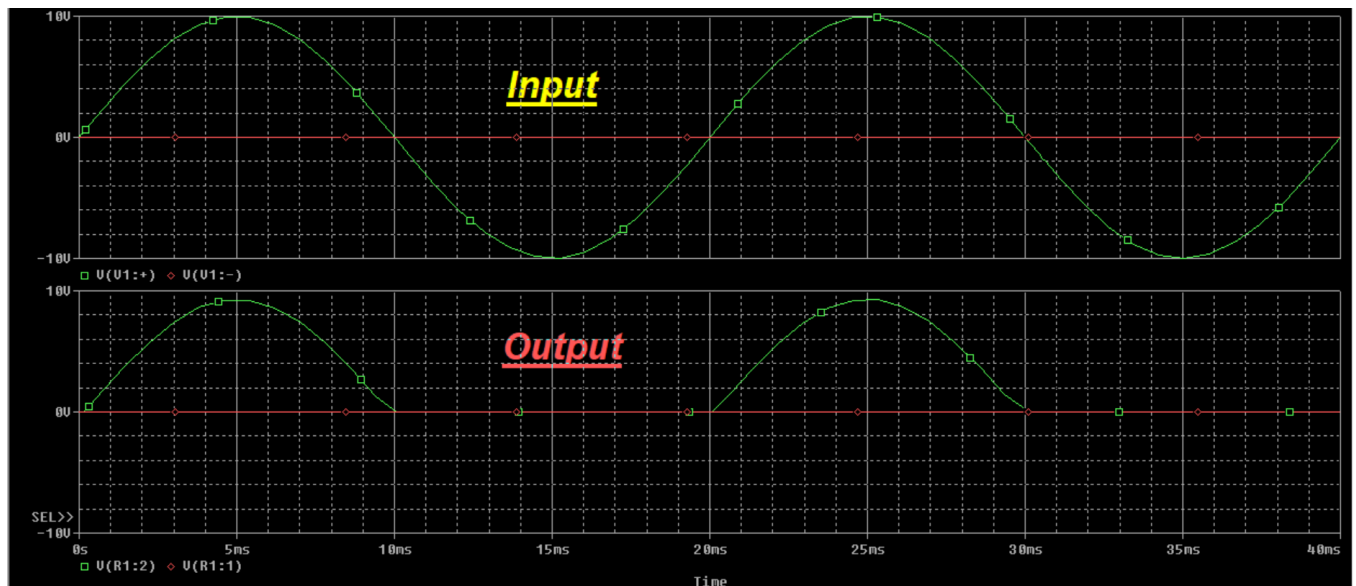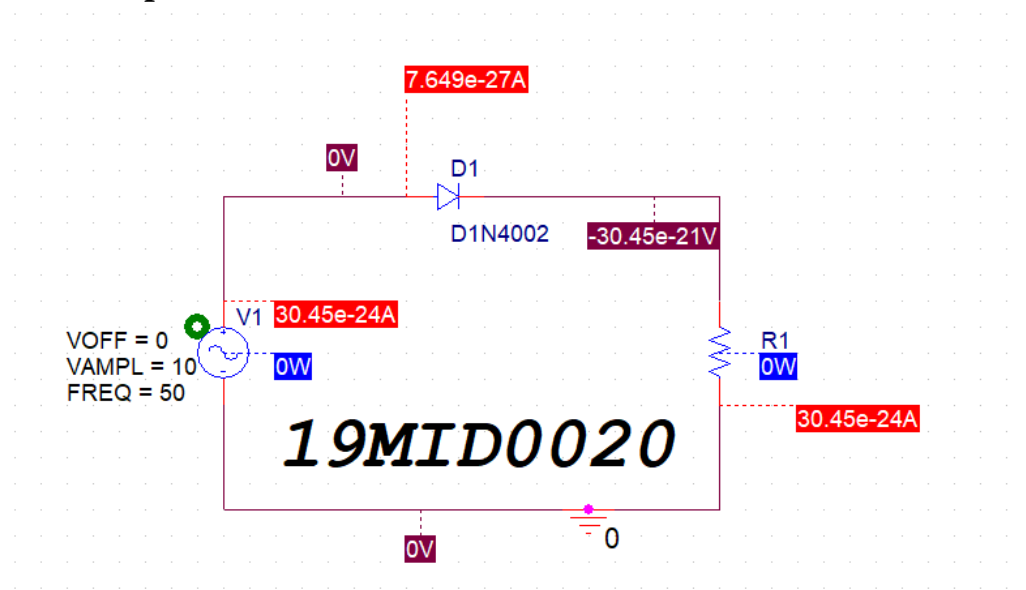Circuit and Output of a Half-wave Rectifier:




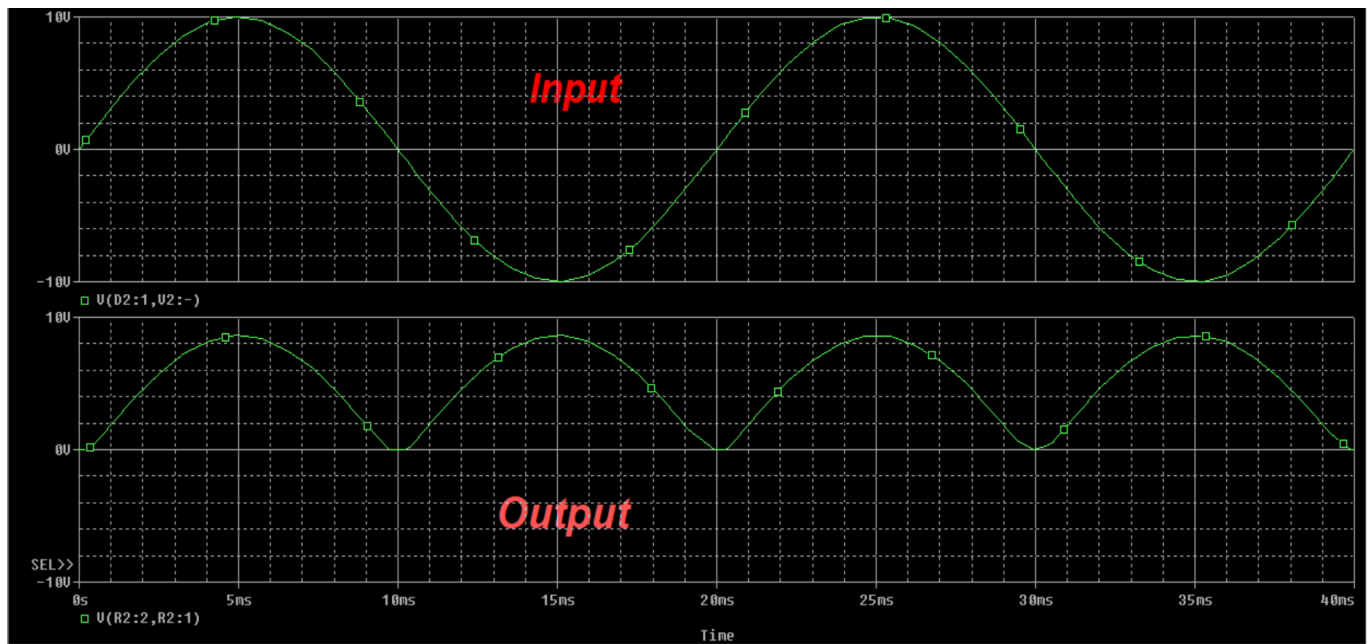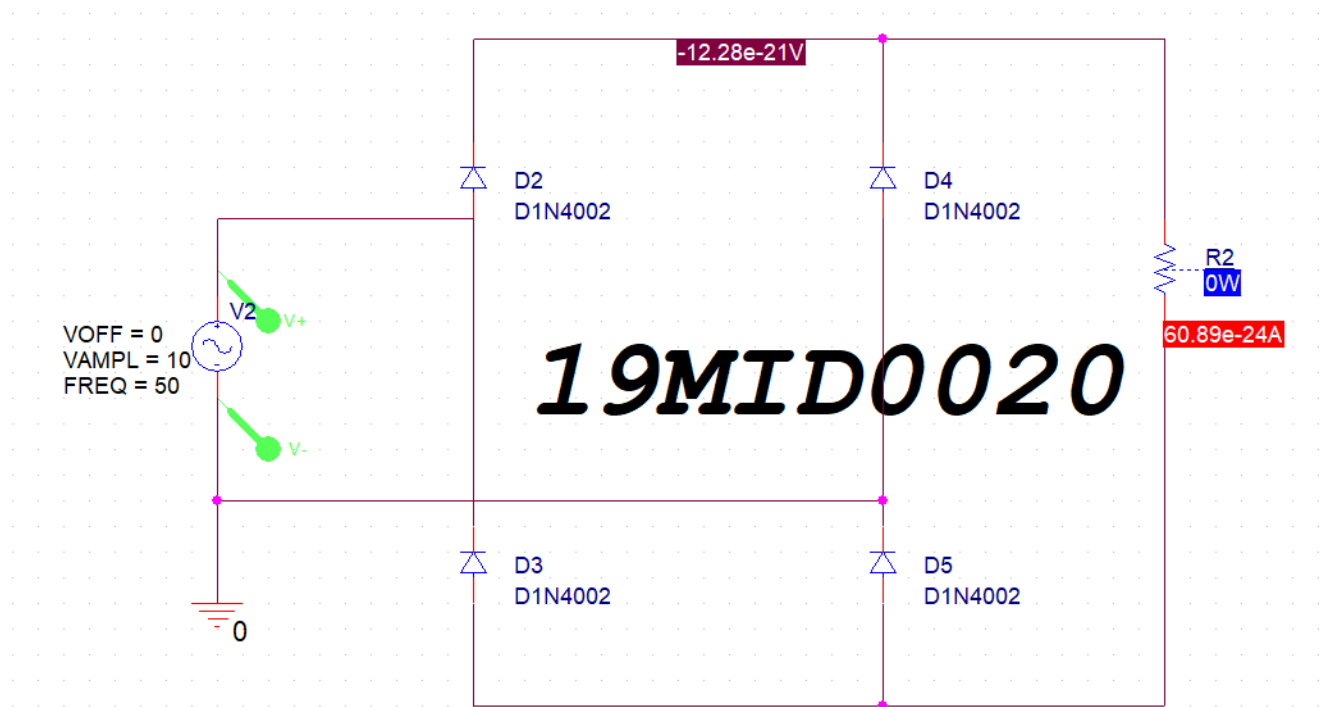Circuit and Output of Full-wave rectifier:



Procedure:

- ✓ Design the circuit using the software
- ✓ Create simulation profile of type “Time Domain” and set the value of Run time as 40ms
- ✓ Place the Voltage differential marker before and after the source to get the input AC wave simulated graph
- ✓ Similarly place it before and after the Load Resistor and run it to get the output DC wave graph.

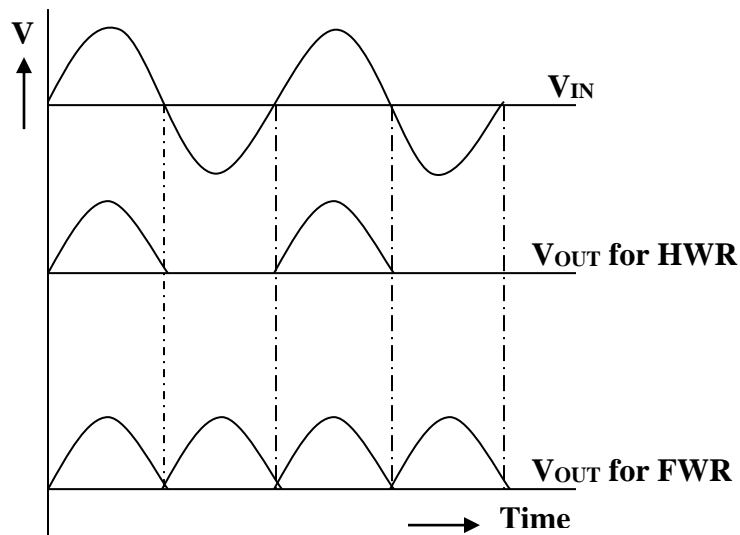Model Graph:**Result:**

The simulation of Single-phase Half wave and Full wave rectifier is performed using OrCAD Pspice software.

Inference:

- ✓ Rectifier converts a AC source to DC form.
- ✓ Half wave rectifier converts the positive half cycles of the AC to DC form
- ✓ Full wave rectifier converts both the positive and negative half cycles of the AC source to DC source.

Reg. No: 19MID0020

Name: Prashanth.S

Date: 25-10-2020