




EEE1024: Fundamentals of Electrical and Electronics Engineering

Dr. Sanchit Khataavkar

Node Voltage Analysis - Practice

Q1:

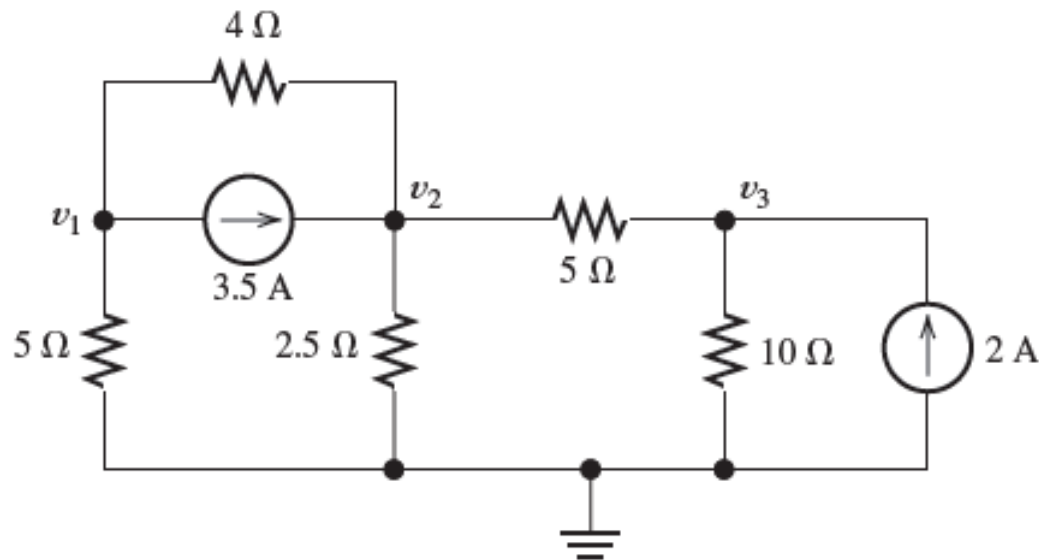

$$\frac{v_1}{5} + \frac{v_1 - v_2}{4} + 3.5 = 0$$

$$0.45v_1 - 0.25v_2 = -3.5$$

@1

$$\frac{v_2 - v_1}{4} + \frac{v_2}{2.5} + \frac{v_2 - v_3}{5} = 3.5$$

$$-0.25v_1 + 0.85v_2 - 0.2v_3 = 3.5$$

@2

$$\frac{v_3 - v_2}{5} + \frac{v_3}{10} = 2$$


$$-0.2v_2 + 0.35v_3 = 2$$

@3

$$V_1 = -5V \quad V_2 = 5V \quad V_3 = 10V$$

Node Voltage Analysis - Practice

Q 2:

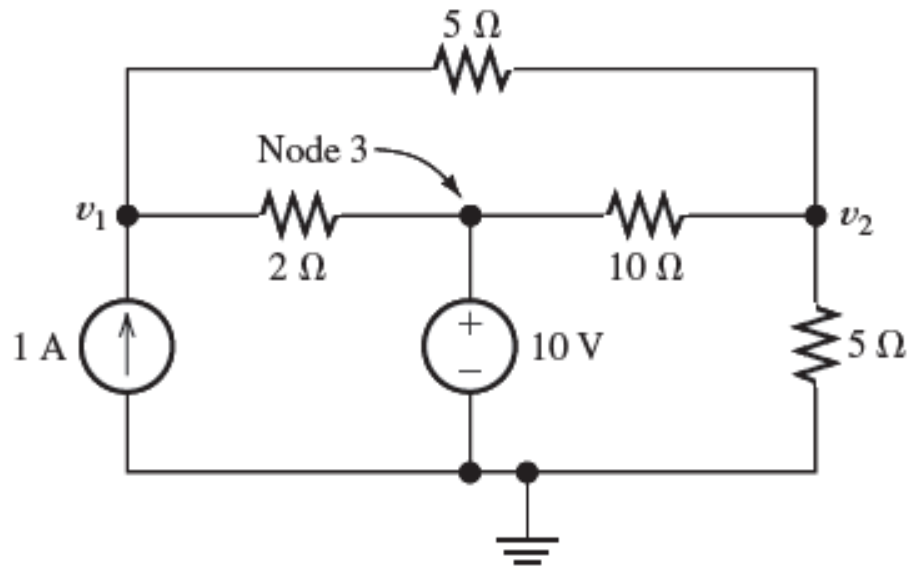

$$\frac{v_1 - v_2}{5} + \frac{v_1 - 10}{2} = 1$$

$$0.7v_1 - 0.2v_2 = 6$$

← @1

$$\frac{v_2}{5} + \frac{v_2 - 10}{10} + \frac{v_2 - v_1}{5} = 0$$

$$-0.2v_1 + 0.5v_2 = 1$$

← @2


$$V_1 = 10.32V$$

$$V_3 = 10V$$


$$V_2 = 6.129V$$

MESH CURRENT ANALYSIS

Mesh Current Analysis

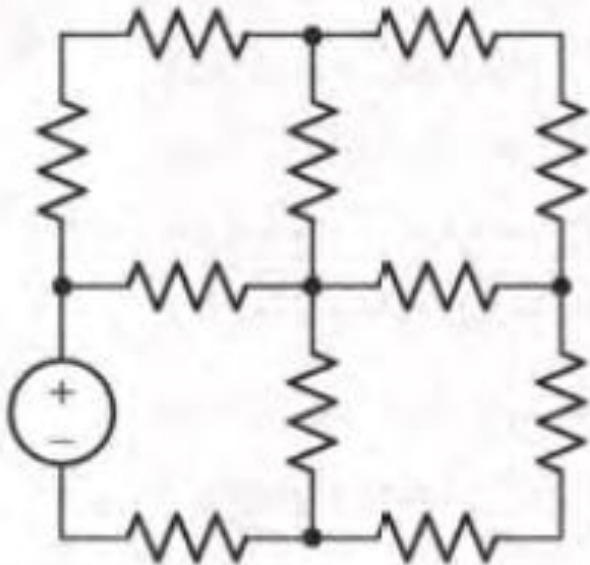


PLANAR Networks

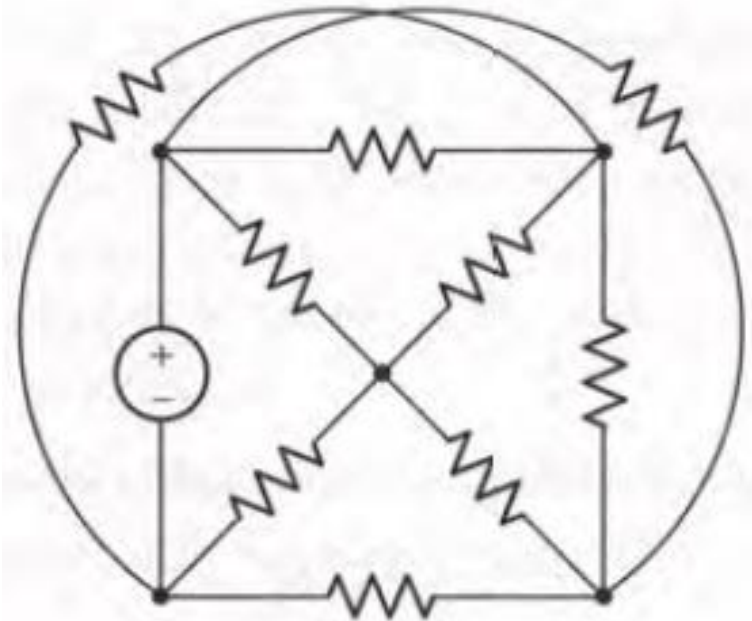

NON-PLANAR
Networks

Mesh Current / Loop Current


Branch current Vs Mesh current

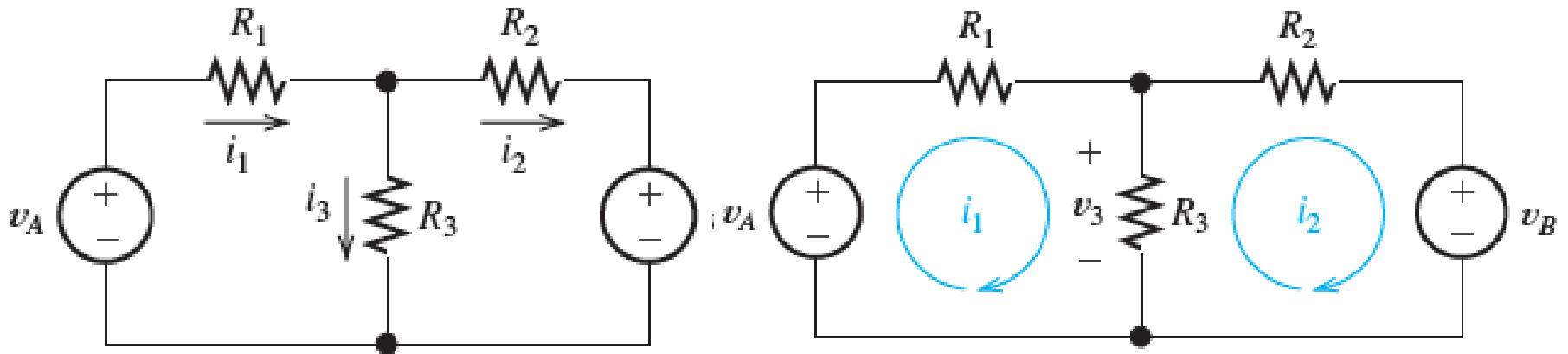

Branch currents –
through elements

Mesh currents

Advantage of Mesh Current Analysis

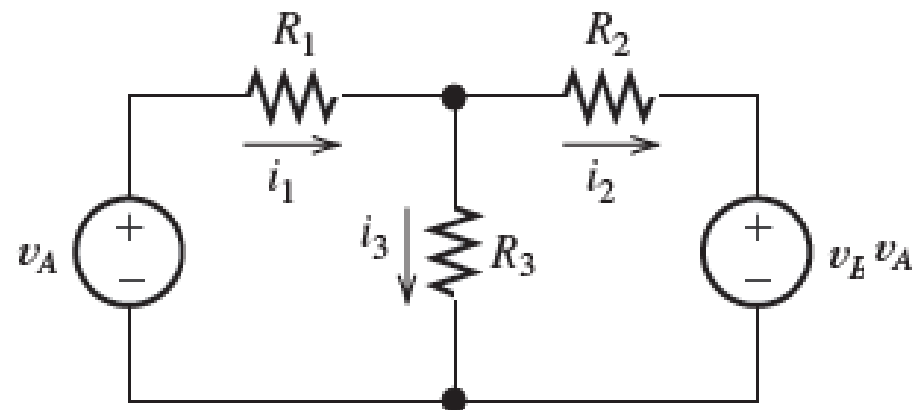

$$R_1 i_1 + R_3 i_3 = v_A$$

$$-R_3 i_3 + R_2 i_2 = -v_B$$

} KVL

$$i_1 = i_2 + i_3$$


} KCL

Substitute for i_3

$$R_1 i_1 + R_3(i_1 - i_2) = v_A$$

$$-R_3(i_1 - i_2) + R_2 i_2 = -v_B$$

Branch currents – i_1, i_2, i_3

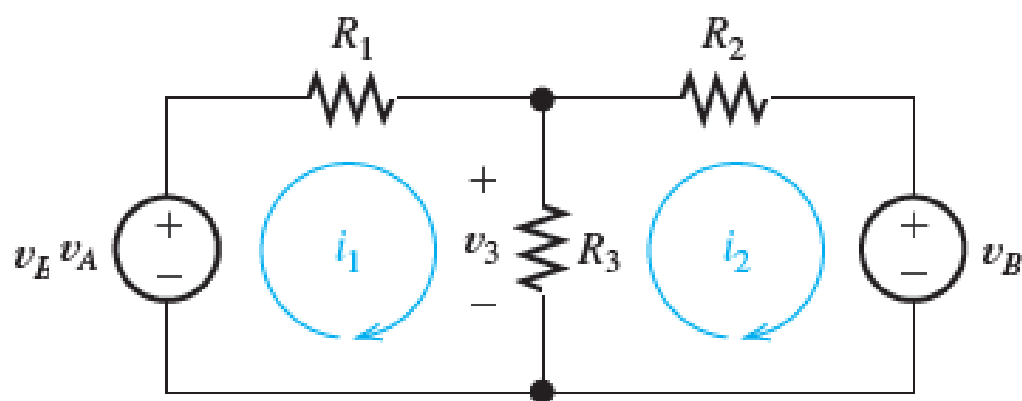


1. Draw meshes
2. Solve easy ones
3. Write KVL for the rest
4. Solve

Apply KVL to each mesh

$$R_1 i_1 + R_3(i_1 - i_2) = v_A$$

$$-R_3(i_1 - i_2) + R_2 i_2 = -v_B$$

Mesh currents - i_1, i_2

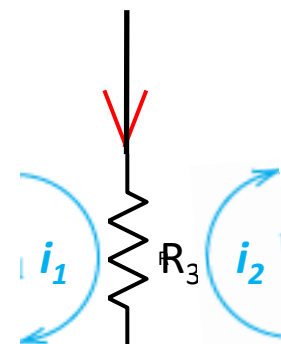


$$i_{R3} = i_1 - i_2$$

Save 2 steps!!!

Mesh current method

Example 1

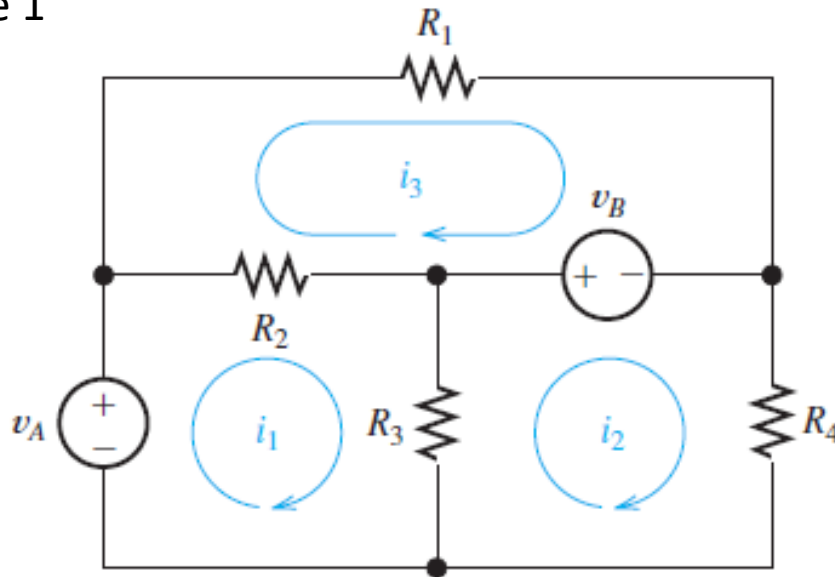

$$\begin{aligned}(R_2 + R_3)i_1 - R_3i_2 - R_2i_3 &= v_A \\ -R_3i_1 + (R_3 + R_4)i_2 &= -v_B \\ -R_2i_1 + (R_1 + R_2)i_3 &= v_B\end{aligned}$$

Apply KVL to each mesh,
starting with Mesh 1


KVL @ Mesh 2

KVL @ Mesh 3

$$R_2(i_1 - i_3) + R_3(i_1 - i_2) - v_A = 0$$

$$R_3(i_2 - i_1) + R_4i_2 + v_B = 0$$

$$R_2(i_3 - i_1) + R_1i_3 - v_B = 0$$

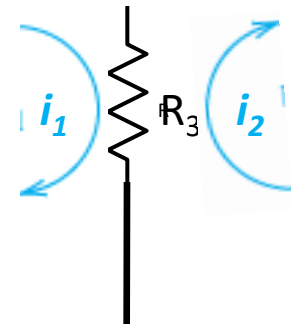

R times current in the mesh under consideration minus the adjacent mesh!

Acknowledgements

1. H. Hayt, J.E. Kemmerly and S. M. Durbin, 'Engineering Circuit Analysis', 6/e, Tata McGraw Hill, New Delhi, 2011
2. Allan R. Hambley, 'Electrical Engineering - Principles & Applications, Pearson Education, First Impression, 6/e, 2013