



EEE1024: Fundamentals of Electrical and Electronics Engineering

Dr. Sanchit Khataavkar

Passive Elements

Linear Resistor: 1827 – G. S. Ohm and later Henry Cavendish


“Voltage across conducting materials is proportional to the current flowing through it”

$$V \propto I \quad V = IR \quad \text{or} \quad R = \frac{V}{I} \quad \text{where } R \text{ is constant of proportionality - resistance}$$

Unit of resistance – ohm “ Ω ”

$$1\Omega = \frac{1V}{1A}$$
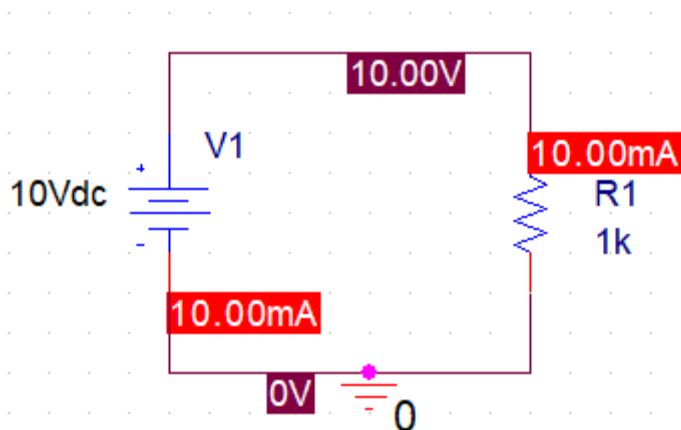
$$\frac{1A}{1V} = 1S \quad \text{where } S \text{ is unit of Conductance 'G'} \quad G = \frac{I}{V} = \frac{1}{R}$$




$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{10}{1 \times 10^3}$$

$$I = 10^{-2} \text{ A}$$

$$I = 10 \text{ mA}$$

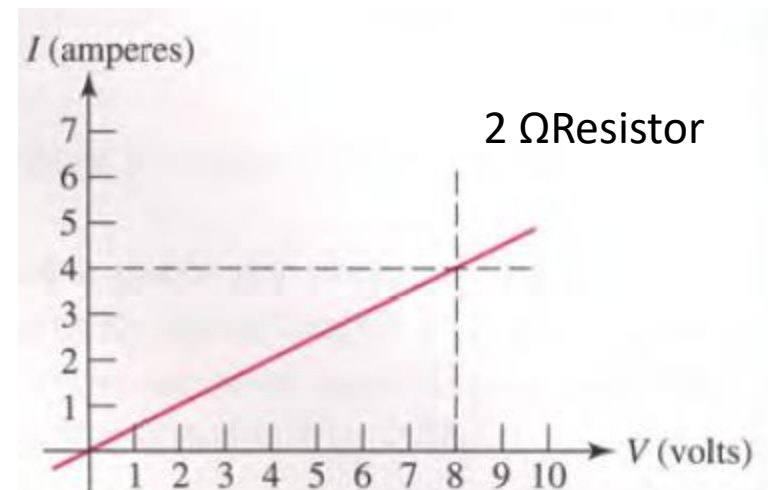


Power

When current flows – from higher potential to lower potential, $V = IR$
 – from lower potential to higher potential $V = -IR$

Power absorbed by an element (in a circuit) =
 product of voltage across it and the current
 flowing through it.


$$P = VI = (IR)I = I^2 R$$

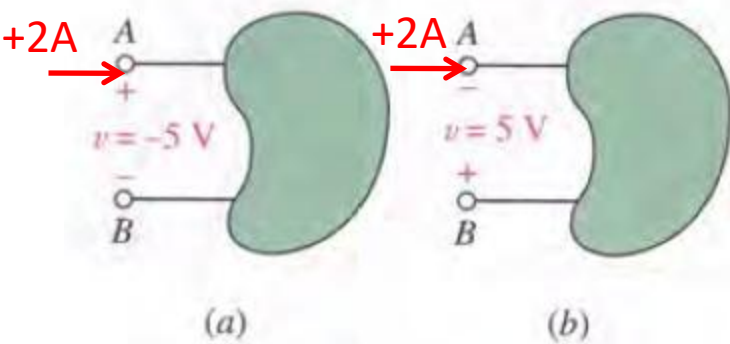

← Terminal B is 5V +ve w.r.t. A

a) $(-5)(+2) = -10W$???


b) $(+5)(+2) = +10W$

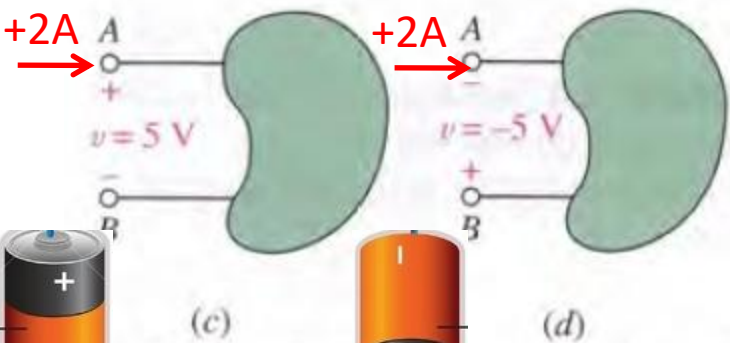

← Terminal A is 5V +ve w.r.t. B

c) $(+5)(+2) = +10W$

d) $(+5)(+2) = +10W$

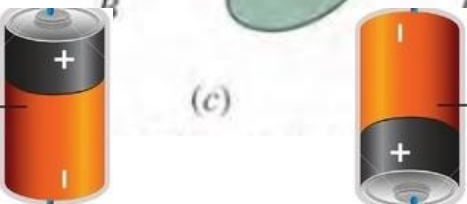


Power – Passive Sign Convention

Negative Power – Object is losing energy or supplying energy to another object! OR
- GENERATING Energy -> **It is a Source!**


One terminal of an element is V volts +ve w.r.t. other, and if current I enters the element through that terminal, power $P = VI$ is absorbed by the element OR Power P is delivered to the element (by a source)

Passive Sign Convention – Power absorbed or dissipated is positive!

Linear Resistor

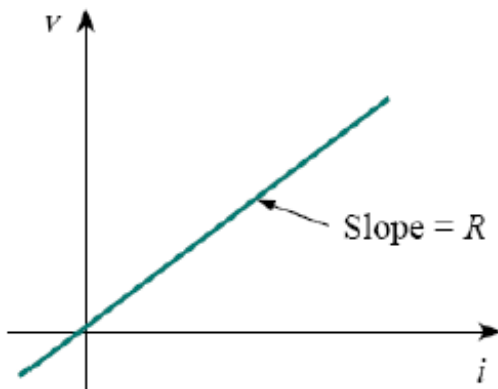


Non-linear Resistor

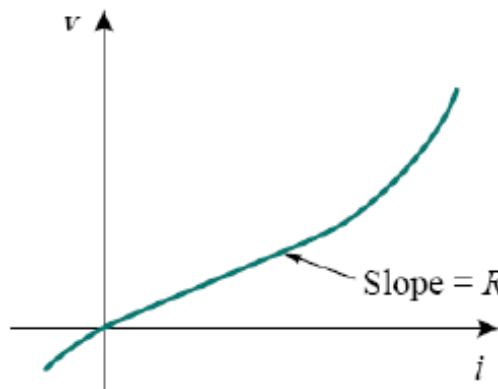

**Non-linear resistor
does NOT obey
Ohm's law!**

Simple Example

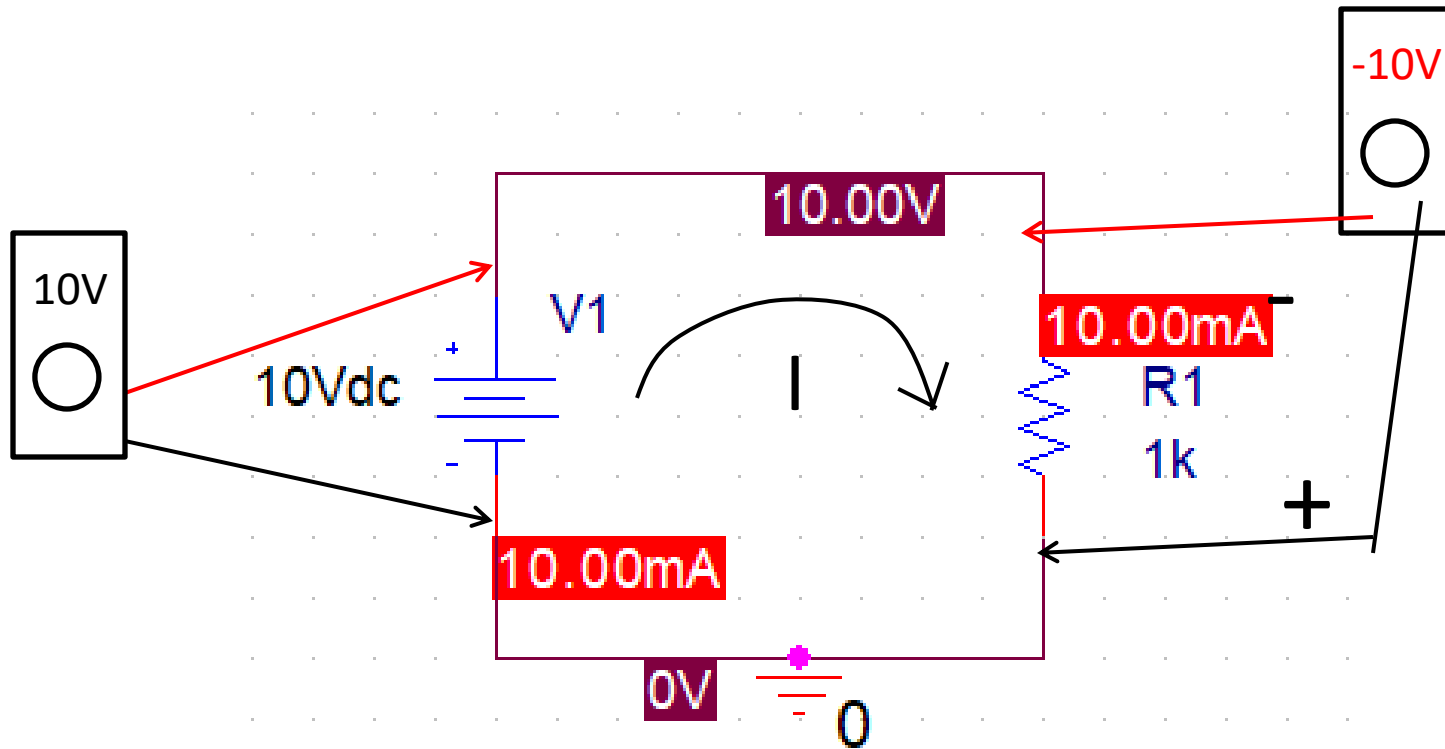

V drop across R1 = +10V

SI Prefixes



Not highlighted are the ones which are *frequently used*

Factor	Name	Symbol	Factor	Name	Symbol
10^{-24}	yocto	y	10^{24}	yotta	Y
10^{-21}	zepto	z	10^{21}	zetta	Z
10^{-18}	atto	a	10^{18}	exa	E
10^{-15}	femto	f	10^{15}	peta	P
10^{-12}	pico	p	10^{12}	tera	T
10^{-9}	nano	n	10^9	giga	G
10^{-6}	micro	μ	10^6	mega	M
10^{-3}	milli	m	10^3	kilo	k
10^{-2}	centi	c	10^2	hecto	h
10^{-1}	deci	d	10^1	deka	da

Nodes, Branches and Loops

Electrical Network: Interconnection of two or more circuit elements

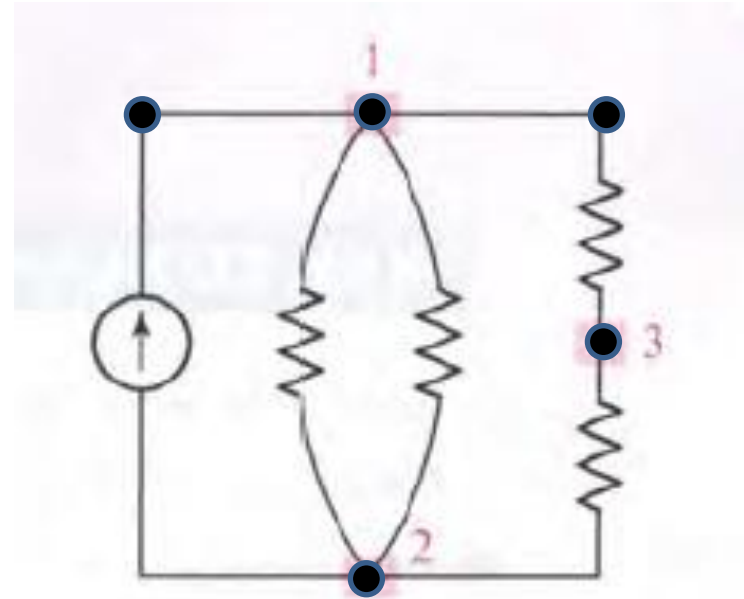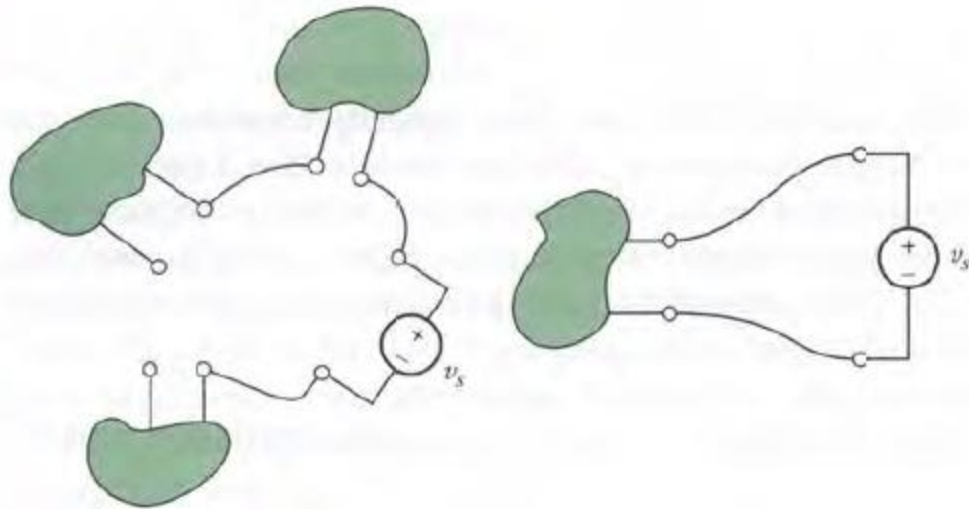Electrical Circuit ?? It is a network which has at least one **closed path**




NODE: A point at which two or more elements have a common connection

How many nodes ? 3

PATH: If we start from one node in a network and pass through different elements, as long as no node is encountered more than once, we have defined a *path*.

Nodes, Branches and Loops

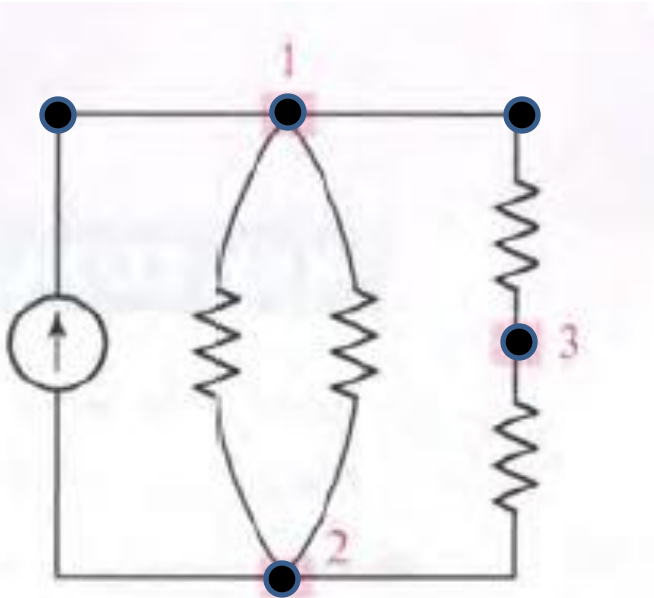

PATH: If we start from one node in a network and pass through different elements, as long as no node is encountered more than once, we have defined a *path*.

LOOP: If the node that we start is the same as the node we end, then the path is called as a *loop*.

Move from node 2 to node 1, then upper right resistor to node 3 – **path** or **loop** ?

When will it become a loop ?

End at node 2

BRANCHES: A single path which is composed of one element and a node at each end of the element.

How many branches in the circuit ? 5

Kirchhoff's Current and Voltage laws

Gustav Robert Kirchhoff – German Univ. Professor - same time as G. S. Ohm
– 2 world famous physical laws

**One law (KCL) –
Principle of conservation of charge**

The total charge of the system
has not and will never change.



Algebraic sum of currents
entering any node is zero


**Second law (KVL) –
Principle of conservation of energy**

Energy is neither created nor
destroyed



Algebraic sum of voltages
around any closed path is zero

Kirchhoff's Current law (KCL)

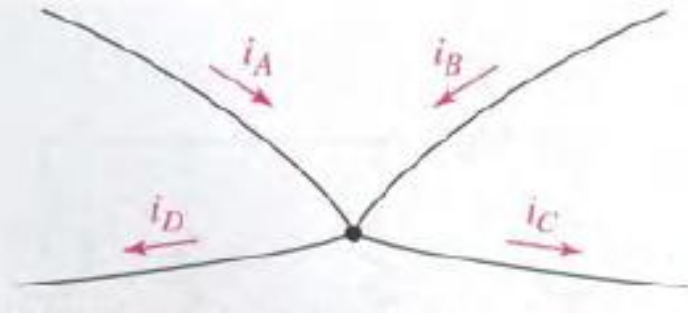

$$i_A + i_B = i_C + i_D$$


Algebraic sum of currents entering any node is zero

Entering the node $i_A + i_B + (-i_C) + (-i_D) = 0$

Leaving the node $(-i_A) + (-i_B) + i_C + i_D = 0$

$$\sum_{n=1}^N i_n = 0$$

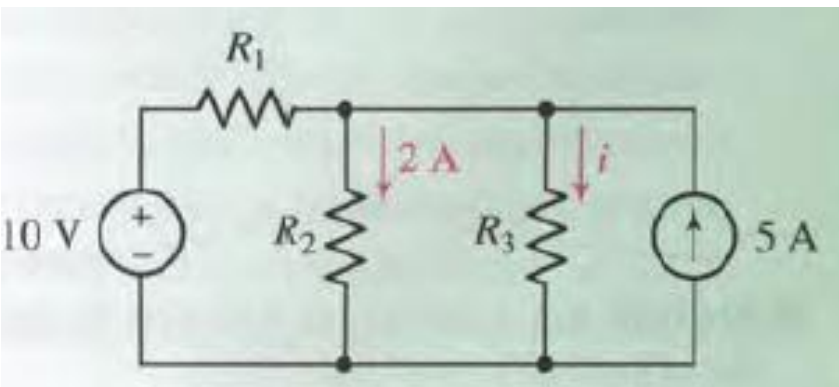Example: If the voltage source supplies 3A of current, compute the current through resistor R_3





Strategy for such questions

- 1) Identify goal of the problem
- 2) Collect known info
- 3) Devise a plan
- 4) Construct proper set of equations.

Kirchhoff's Current law (KCL)

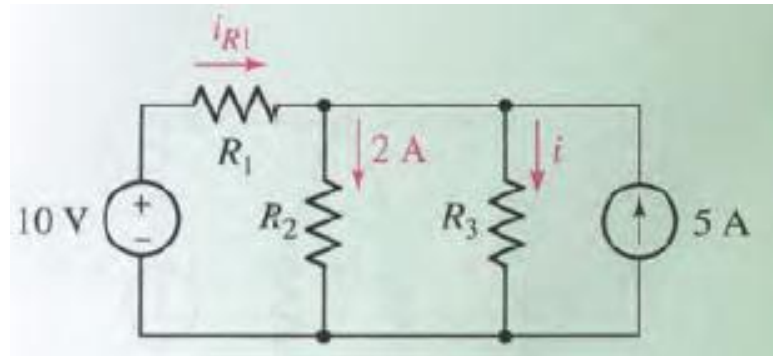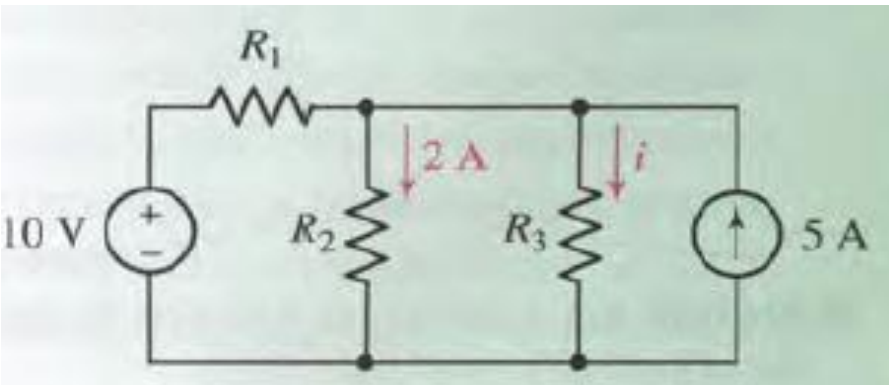Example: If the voltage source supplies 3A of current, compute the current through resistor R_3



- 1) Identify goal of the problem:

Labelled 'i' on the figure

- 2) Collect known info:

Top node of R_3 connected to 3 branches.
Current flowing into this node will have currents from these 3 branches.


- 3) Devise a plan:

Label current thr' R_1 and write KCL at the top node of R_3

- 4) Construct proper set of equations:

Summing up the currents flowing into

the node - $i_{R1} - 2 - i + 5 = 0$

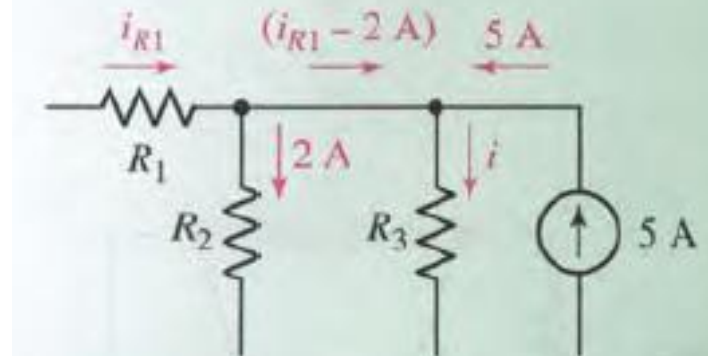

$$i_{R1} - 2 - i + 5 = 0$$

$$3 - 2 + 5 = i$$

$$i = 6A$$