



EEE1024: Fundamentals of Electrical and Electronics Engineering

Dr. Sanchit Khataavkar

RECAP

Sinusoidal form \longleftrightarrow Phasors $v(t) = V_m \cos(\omega t \pm \theta^\circ) \longleftrightarrow V = V \angle \theta^\circ$

Phasors \longleftrightarrow Complex numbers
(rectangular form)

$V = V \angle \theta^\circ \longleftrightarrow z = x + iy$

Phasors \longleftrightarrow Sinusoidal form

$V = V \angle \theta^\circ \longleftrightarrow V_m \cos(\omega t \pm \theta^\circ)$


CONVERSIONS

Resistance


Reactance

Impedance


Units for all 3 – same – Ohms (Ω)

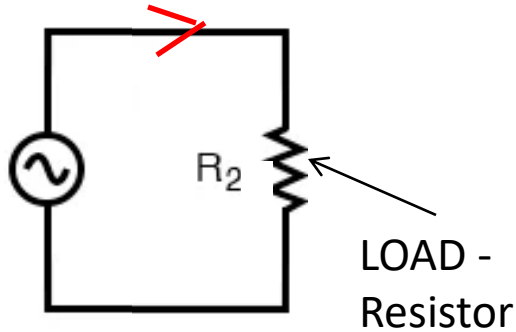

$$R = \frac{V}{I}$$

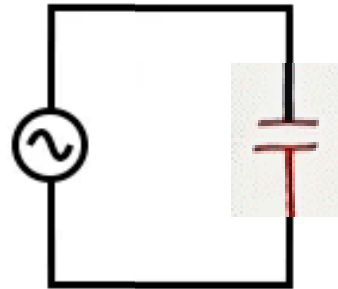

LOAD -
pure Capacitor

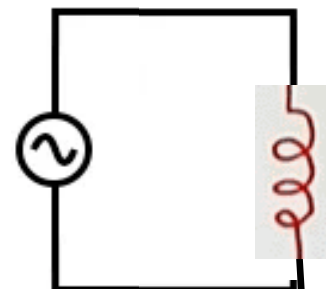


LOAD -
pure Inductor

REACTANCE
- X (Ω)

$$X = \frac{V}{I}$$

If LOAD -

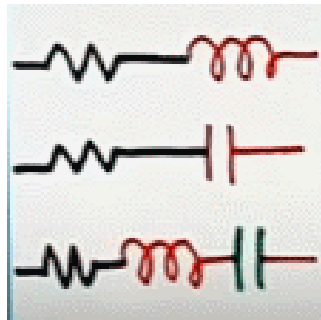

R-L load

R-C load


R-L-C load

IMPEDANCE –
 Z (Ω)

$$Z = \frac{V}{I}$$

COMPLEX IMPEDANCES – *INDUCTANCE*(1)

Inductive circuit

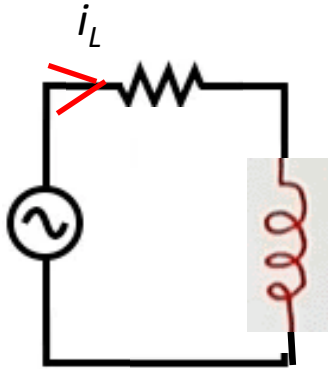

$i_L(t) = I_m \sin(\omega t + \theta)$ Sinusoidal current flowing through inductor

$v_L(t) = L \frac{di_L(t)}{dt}$ Voltage across inductor

$$v(t) = L \frac{di}{dt}$$

$$v_L(t) = \omega L I_m \cos(\omega t + \theta)$$


Phasor for current -

$$\mathbf{I}_L = I_m \angle \theta - 90^\circ$$

Phasor for voltage -



$$\begin{aligned} \mathbf{V}_L &= \omega L I_m \angle \theta \\ &= V_m \angle \theta \end{aligned}$$

Current lags Voltage by 90°

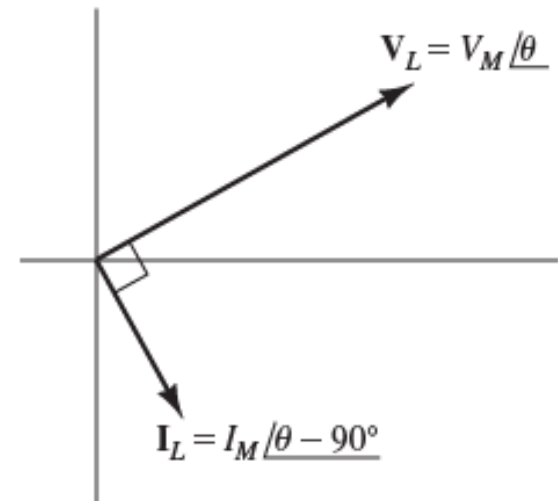

COMPLEX IMPEDANCES – *INDUCTANCE*(2)

Inductive circuit

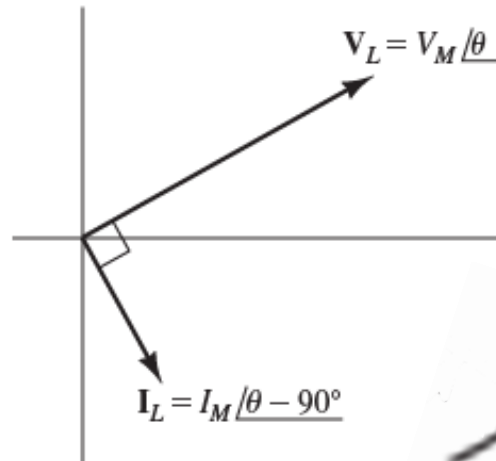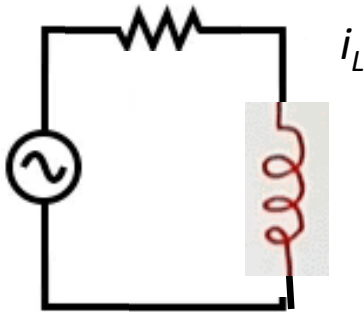

$$\begin{aligned} \mathbf{V}_L &= \omega L I_m \angle \theta \\ &= \omega L I_m \angle (\theta^\circ + 90^\circ - 90^\circ) \\ \mathbf{V}_L &= (\omega L \angle 90^\circ) \times I_m \angle \theta - 90^\circ \end{aligned}$$

$$\mathbf{I}_L = I_m \angle \theta - 90^\circ$$

$$\mathbf{V}_L = (\omega L \angle 90^\circ) \times \mathbf{I}_L$$

$$\mathbf{V}_L = j\omega L \times \mathbf{I}_L \quad \dots\dots\dots j\omega L = \omega L \angle 90^\circ$$

- Impedance of the inductance


$$Z_L = j\omega L = \omega L \angle 90^\circ$$

$$Z_L$$


$$\mathbf{V}_L = Z_L \mathbf{I}_L$$

COMPLEX IMPEDANCES – CAPACITANCE

Capacitive circuit

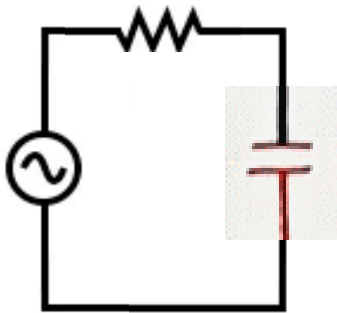
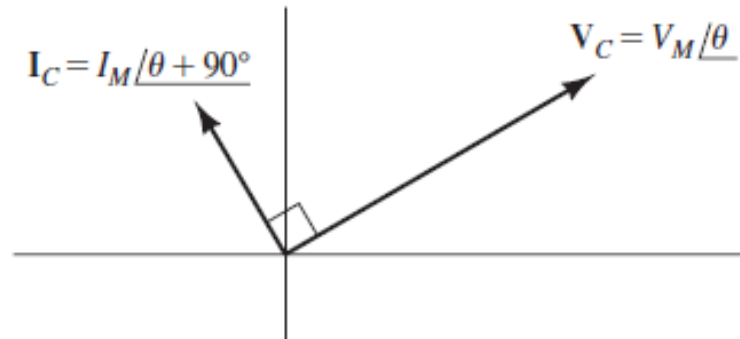
$$\mathbf{V}_C = \mathbf{Z}_C \mathbf{I}_C \quad \text{..... Like,} \quad \mathbf{V}_L = \mathbf{Z}_L \mathbf{I}_L$$



Current LEADS Voltage by 90°


$$\begin{aligned} Z_C &= -j \frac{1}{\omega C} \\ &= \frac{1}{j\omega C} \\ &= \frac{1}{\omega C} \angle -90^\circ \end{aligned}$$

If a phasor voltage \mathbf{V}_C is $\mathbf{V}_C = V_m \angle \theta$


$$\mathbf{I}_C = \frac{\mathbf{V}_C}{\mathbf{Z}_C} = I_m \angle \theta + 90^\circ$$

COMPLEX IMPEDANCES – *RESISTANCE*

Resistive circuit

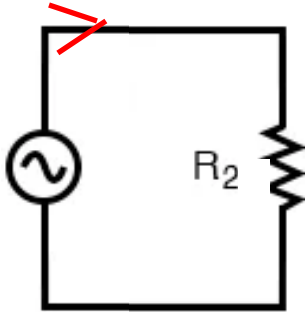

$$\mathbf{V}_R = R\mathbf{I}_R$$

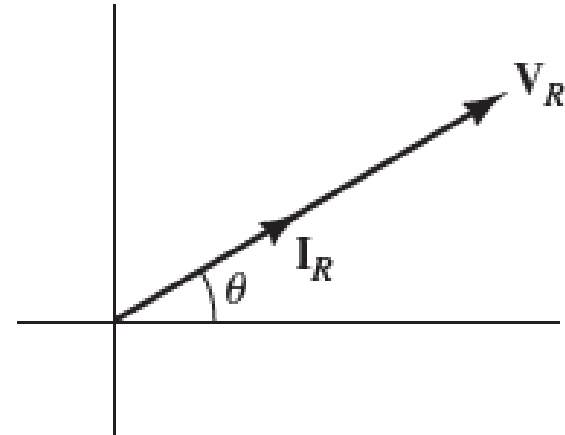

Voltage and Current phasors are - **INPHASE**

COMBINING IMPEDANCES IN SERIES & PARALLEL(1)


*IMPEDANCES of
Capacitances/Inductances*

—————→ Combined as —————→

Resistances

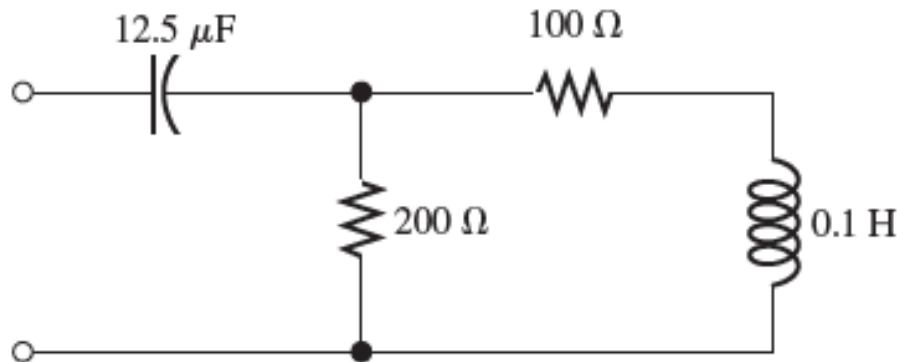Example –

Determine the complex impedance between terminals shown in the figure. $\omega = 1000$ rad/s



$$Z_L = j\omega L$$

$$Z_L = j \times 1000 \times 0.1 = 100j$$

Step 1: Calculate *impedances*


$$Z_c = \frac{-j}{\omega C}$$

$$Z_c = \frac{-j}{1000 \times 12.5 \times 10^{-6}}$$

$$Z_c = \frac{-1}{1000 \times 12.5 \times 10^{-6}}$$

$$= -80j$$

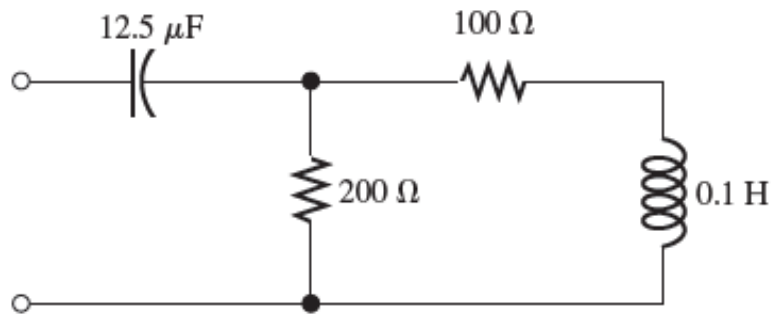COMBINING IMPEDANCES IN SERIES & PARALLEL(2)




Step 1: Calculate *impedances*-
DONE

$$Z_c = -80j \Omega$$

$$Z_L = 100j \Omega$$


Step 2:
Find equivalent resistance in the "ALL RESISTANCE -like" Circuit

→ 100Ω and $100j \Omega$ -
in series

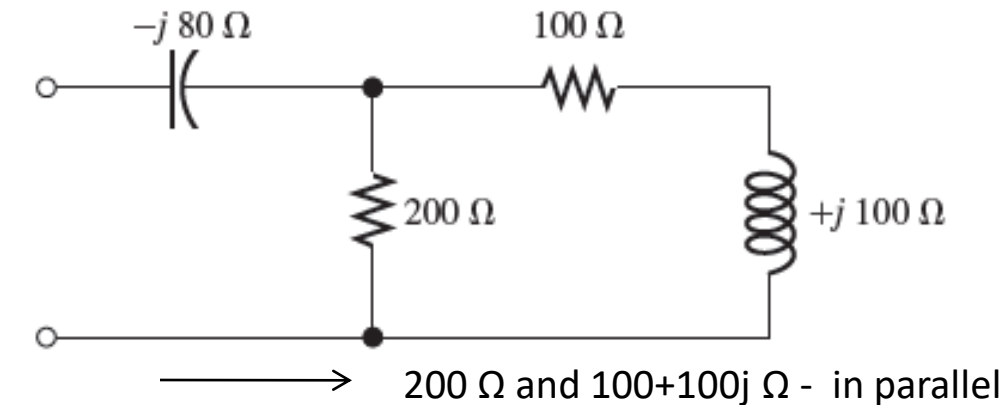


$$= \frac{1}{\left(\frac{1}{200} + \frac{1}{100 + 100j}\right)}$$
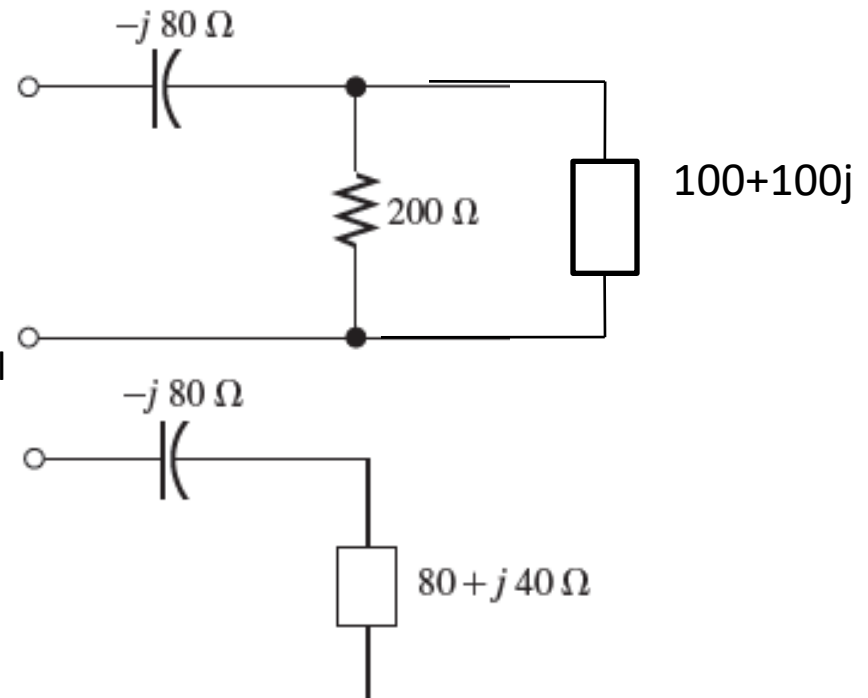
$$= 1 / (1/200 + 1/(100 + 100i)) = 80 + 40i$$



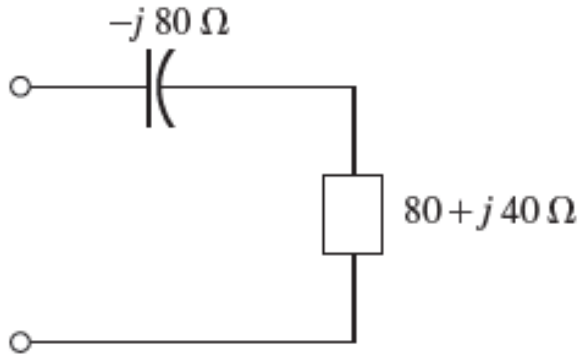COMBINING IMPEDANCES IN SERIES & PARALLEL(3)



$$-j80 + 80 + j40 = 80 - j40 : \longleftarrow \text{ANS}$$

Example 2: A voltage $v_L(t) = 100 \cos(200t)$ is applied to a 0.25H inductance. Notice that $\omega=200$ rad/s.

- Find impedance of inductance, phasor current and phasor voltage (of inductor)
- Draw phasor diagram

ASSIGNMENT

Example 3: A voltage $v_C(t) = 100 \cos(200t)$ is applied to a 100 μ F capacitance.

- Find impedance of capacitance, phasor current and phasor voltage (of capacitor)
- Draw phasor diagram

CIRCUIT ANALYSIS with PHASORS and COMPLEX IMPEDANCES

KIRCHOFF'S LAWS


NODE VOLTAGE ANALYSIS

MESH CURRENT ANALYSIS

Steady state AC analysis of an AC circuit

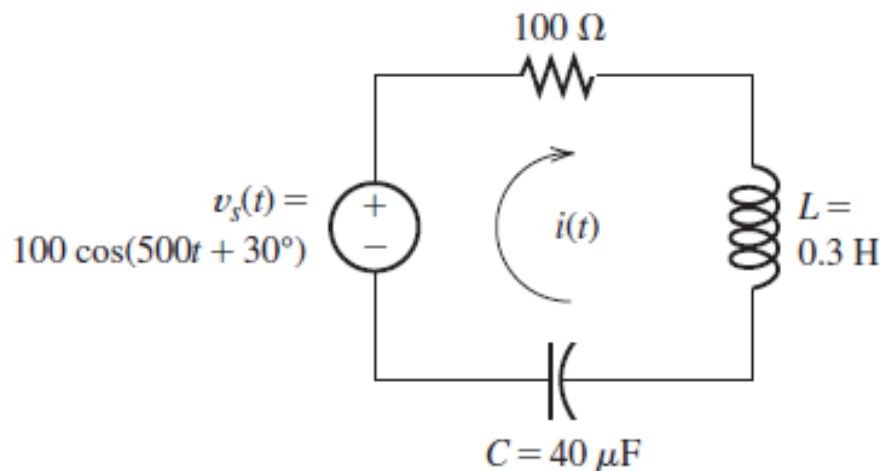Example:

- Find the steady state current in the given circuit
- Find the voltage across each element in the circuit and construct a phasor diagram



Step 1: Calculate *impedances*


$$Z_L = j\omega L = j500 \times 0.3 = j150 \, \Omega$$

$$Z_C = -j\frac{1}{\omega C} = -j\frac{1}{500 \times 40 \times 10^{-6}} = -j50 \, \Omega$$


Step 2: Replace $v(t)$ by phasors

$$\mathbf{V}_s = 100 \angle 30^\circ$$

STEADY STATE ANALYSIS of an AC Circuit

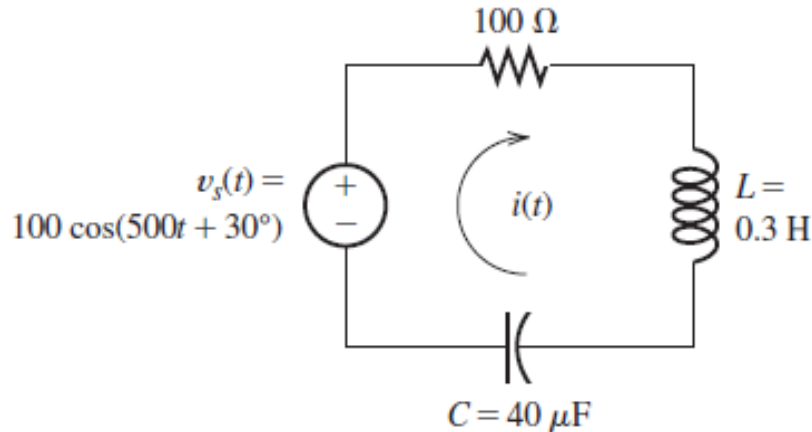

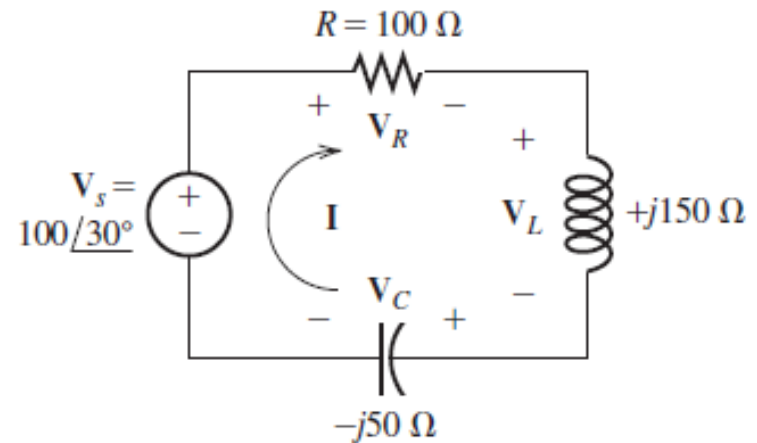Step 2: Replace $v(t)$ and $i(t)$ by phasors



Step 3a: Use KVL

$$-V_s + 100I + (150i)I + (-50i)I = 0$$

$$V_s = (100 + 150i - 50i)I$$

$$V_s = (100 + 100i)I$$

$$I = \frac{V_s}{100 + 100i} = \frac{100\angle 30}{100 + 100i}$$

$$\begin{aligned} 100\angle 30 &= 100(\cos(30) + i \sin(30)) \\ &= 100(0.866 + i(0.5)) \\ &= 86 + 50i \end{aligned}$$

$$I = \frac{86 + 50i}{100 + 100i}$$

$$I = \frac{(86 + 50i)}{(100 + 100i)} \times \frac{(100 - 100i)}{(100 - 100i)} = 0.68 - 0.18i$$

STEADY STATE ANALYSIS of an AC Circuit

Step 3b: Use the properties of a series circuit

Series circuit – Current remains same!

$$Z_{eq} = R + Z_L + Z_C$$

$$Z = \frac{V}{I}$$

$$Z_{eq} = 100 + j150 - j50 = 100 + j100$$

$$Z_{eq} = 141.4 \angle 45^\circ$$

$$\mathbf{I} = \frac{\mathbf{V}_s}{Z} = \frac{100 \angle 30^\circ}{141.4 \angle 45^\circ} = 0.707 \angle -15^\circ$$

$$i(t) = 0.707 \cos(500t - 15^\circ)$$

Step 4: Calculate voltages across each element


$$\mathbf{V}_R = R \times \mathbf{I} = 100 \times 0.707 \angle -15^\circ = 70.7 \angle -15^\circ$$

$$\mathbf{V}_L = j\omega L \times \mathbf{I} = \omega L \angle 90^\circ \times \mathbf{I} = 150 \angle 90^\circ \times 0.707 \angle -15^\circ = 106.1 \angle 75^\circ$$

$$\begin{aligned} \mathbf{V}_C &= -j \frac{1}{\omega C} \times \mathbf{I} = \frac{1}{\omega C} \angle -90^\circ \times \mathbf{I} = 50 \angle -90^\circ \times 0.707 \angle -15^\circ \\ &= 35.4 \angle -105^\circ \end{aligned}$$

CIRCUIT ANALYSIS with PHASORS and COMPLEX IMPEDANCES

MESH CURRENT ANALYSIS

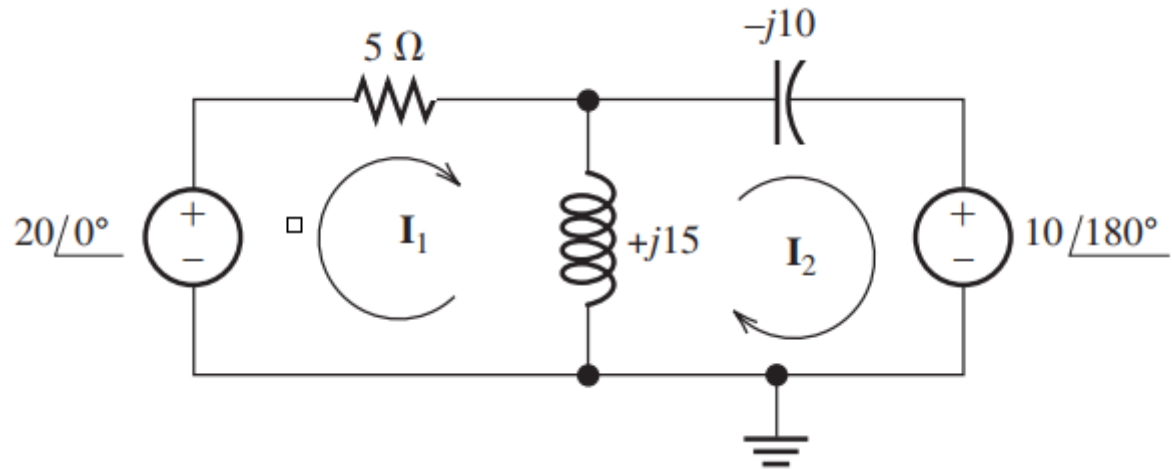

@Loop1

$$-20\angle 0 + I_1(5) + (I_1 - I_2)15j = 0$$


@Loop2

$$10\angle 180 + (I_2 - I_1)15j + I_2(-10j) = 0$$

AC Power Calculations


Current, Voltage and POWER

RESISTIVE Load

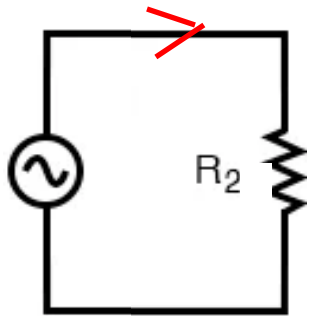


$$v(t) = V_m \cos(\omega t) \quad i(t) = I_m \cos(\omega t)$$
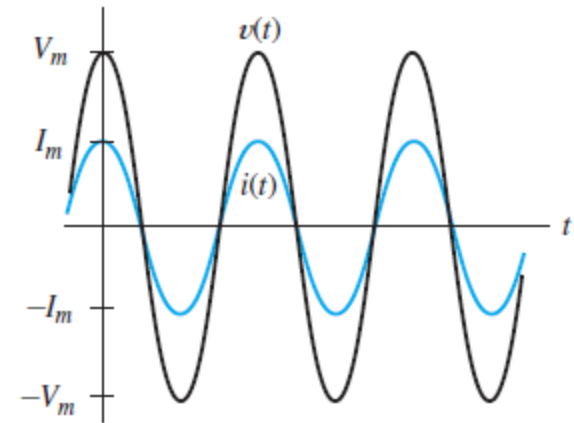
$$p(t) = v(t)i(t) = V_m I_m \cos^2(\omega t)$$



INDUCTIVE Load

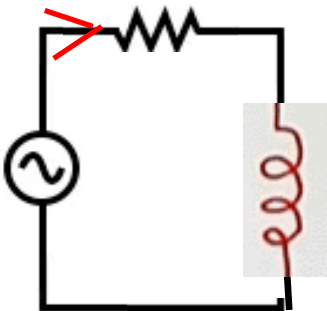

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t - 90^\circ) = I_m \sin(\omega t)$$


$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t) \sin(\omega t)$$

Using the trigonometric identity $\cos(x) \sin(x) = (1/2) \sin(2x)$

$$p(t) = \frac{V_m I_m}{2} \sin(2\omega t)$$

Current, Voltage and POWER

CAPACITIVE
Load

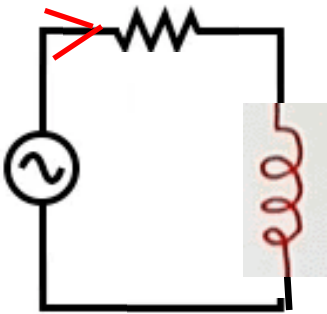

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t + 90^\circ) = -I_m \sin(\omega t)$$

$$p(t) = v(t)i(t) = -V_m I_m \cos(\omega t) \sin(\omega t)$$

$$= -\frac{V_m I_m}{2} \sin(2\omega t)$$

Using the trigonometric identity $\cos(x) \sin(x) = (1/2) \sin(2x)$

POWER calculations for a general RLC Load (1)

RLC load where phase θ can be any value from -90° to $+90^\circ$

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t - \theta)$$

$$p(t) = V_m I_m \cos(\omega t) \cos(\omega t - \theta)$$

Average Power

$$P = \frac{V_m I_m}{2} \cos(\theta)$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$P = V_{rms} I_{rms} \cos(\theta)$$

Average Power – ACTIVE power

Units: W

$\cos(\theta)$ – POWER FACTOR

POWER calculations for a general RLC Load (2)

RLC load where phase θ can be any value from -90° to $+90^\circ$

ACTIVE power

$$P = V_{\text{rms}} I_{\text{rms}} \cos(\theta)$$

Units: W

POWER FACTOR

$$\cos(\theta)$$

For phase $\theta = 0^\circ$

For phase θ value other than 0°

$$\theta = \theta_v - \theta_i$$

θ_v = Phase of voltage

θ_i = Phase of current

REACTIVE Power

$$Q = V_{\text{rms}} I_{\text{rms}} \sin(\theta)$$

Units: VAR

APPARENT Power

$$P^2 + Q^2 = (V_{\text{rms}} I_{\text{rms}})^2$$

Units: VA