

# BASIC CIRCUIT ELEMENTS AND SOURCES, OHMS LAW

Module 1: Fundamentals of DC Circuits

EEE 1024 Fundamentals of Electrical and Electronics Engineering

1



# BIOGRAPHY

- Dr. Kishore Bingi
- Assistant Professor Senior Grade 1
- School of Electrical Engineering
- PhD from Universiti Teknologi PETRONAS, Malaysia
- <https://www.kishorebingi.co.in/>
- kishore.bingi@vit.ac.in



Team Name: EEE1024 A2 Slot Monday & Wednesday Morning



Syllabus: Teams - General – Files



Material: Teams – Module – Files



Attendance: Teams – Time in & Time Out – VTOP



Questions during Presentation: Raise Hand



Queries in General: Teams – Channel – Chat



Assignments – End of each module through Moodle

# MICROSOFT TEAMS & OTHERS




# TOPICS

- Electrical Circuit
- Circuit Elements
- Charge
- Electrical Current
- Electrical Voltage
- Power & Energy
- Resistors and Ohm's Law
- Ohm's Law Triangle
- Power Triangle
- Ohm's Law Pie Chart


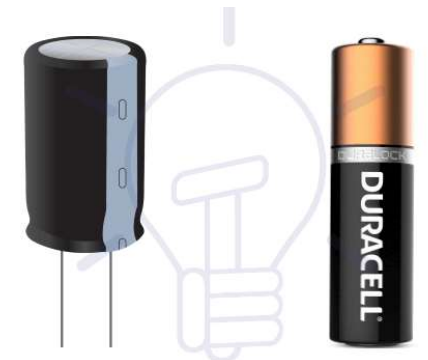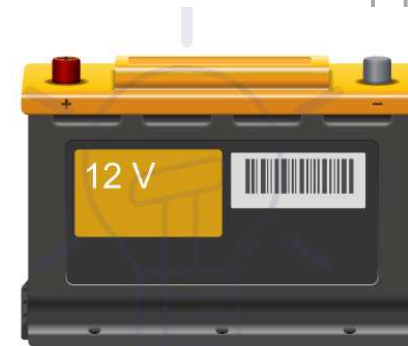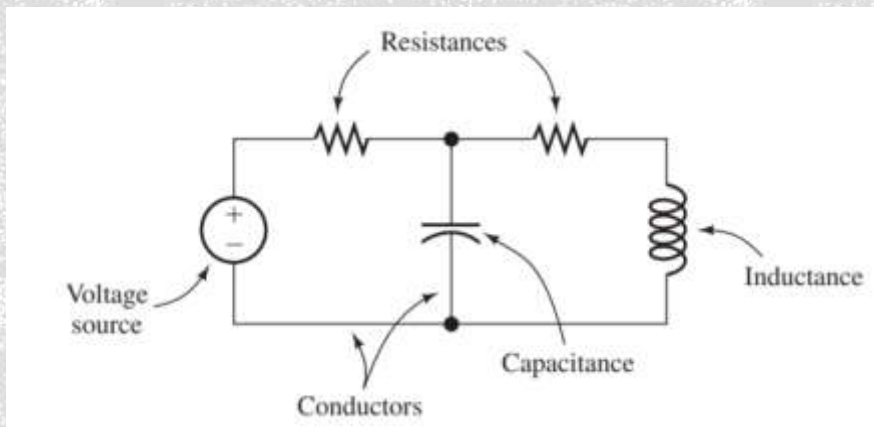
# ELECTRICAL CIRCUIT

- An **electrical circuit** consists of various types of circuit elements connected in closed paths by conductors.
- The circuit elements can be **resistances, inductances, capacitances, and voltage sources**, among others



# CHARGE



- Charge flows easily through conductors, which are represented by lines connecting circuit elements.
- Voltage sources create forces that cause charge to flow through the conductors and other circuit elements.
- As a result, energy is transferred between the circuit elements, resulting in a useful function.

# ELECTRICAL CURRENT

- Electrical current is the time rate of flow of electrical charge ( $q(t)$ ) through a conductor or circuit element.

$$i(t) = \frac{dq(t)}{dt}$$

- The units are amperes (A), which are equivalent to coulombs per second (C/s).
- The charge on an electron is  $-1.602 \times 10^{-19}\text{C}$ .
- To find charge given current, we must integrate.

$$q(t) = \int_{t_0}^t i(t)dt + q(t_0)$$

- $t_0$  is some initial time at which the charge is known.



# EXAMPLE 1: DETERMINING CURRENT GIVEN CHARGE

- Suppose that charge versus time for a circuit element is given by

$$q(t) = \begin{cases} 0 & \text{for } t < 0 \\ 2 - 2e^{-100t} \text{ C} & \text{for } t > 0 \end{cases}$$

- Calculate  $i(t)$  and Plot  $i(t)$  and  $q(t)$

- Solution:

$$i(t) = \frac{dq(t)}{dt}$$

$$\text{For } t < 0 \rightarrow i(t) = \frac{dq(t)}{dt} \rightarrow 0$$

$$\text{For } t > 0 \rightarrow i(t) = \frac{dq(t)}{dt} \rightarrow \frac{d}{dt}(2 - 2e^{-100t}) \rightarrow 200e^{-100t} \text{ A}$$



# EXAMPLE 2: DETERMINING CURRENT GIVEN CHARGE



- The charge that passes through a circuit element is given by

$$q(t) = 0.01 \sin(200t) \text{ C}$$



- Find the current as a function of time.
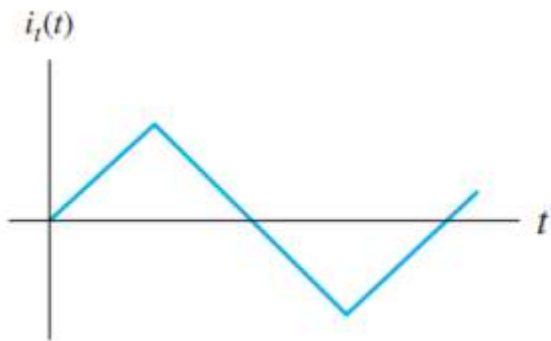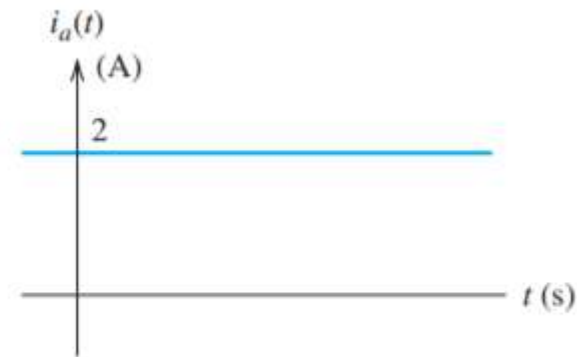
# DIRECT CURRENT (DC) AND ALTERNATING CURRENT (AC)

- When a **current is constant with time**, we say that we have **direct current**, abbreviated as **dc**
- When current that varies with time, reversing direction periodically, is called alternating current, abbreviated as **ac**.




?

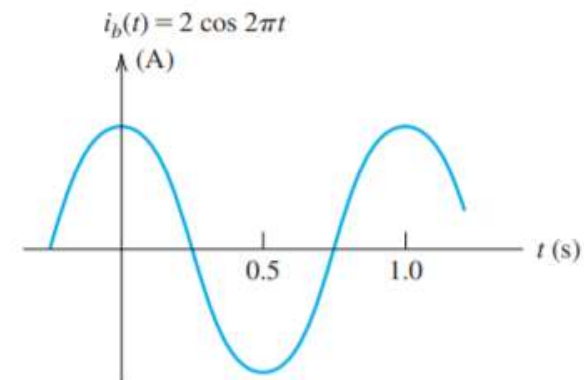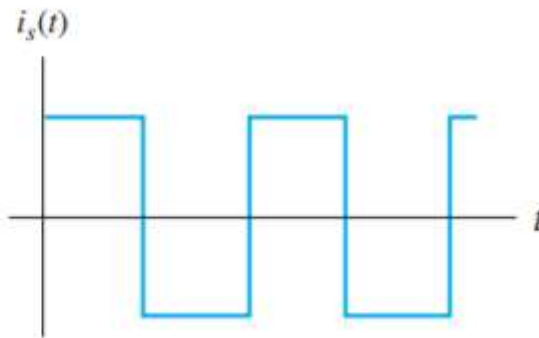
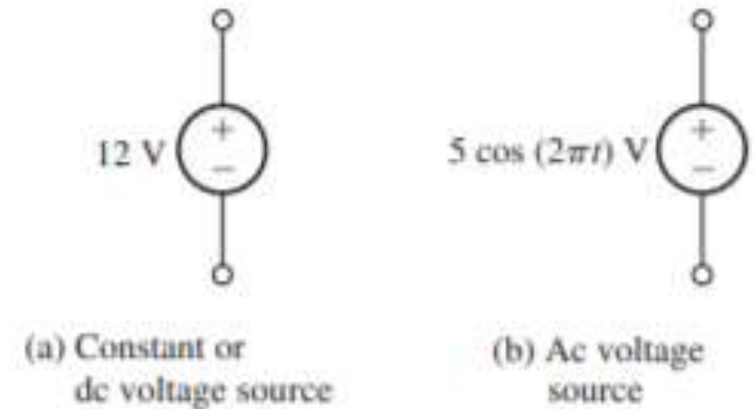
# DIRECT VOLTAGE (DC) AND ALTERNATING VOLTAGE (AC)

- The **voltage** associated with a circuit element is the energy transferred per unit of charge that flows through the element.
- The units of voltage are volts (V), which are equivalent to joules per coulomb (J/C).
- Voltage constant with time is called **dc voltage**.
- Voltage that change in magnitude and alternate in polarity with time is called **ac voltage**.



# BASIC CIRCUIT ELEMENTS

- Resistance
- Inductance
- Capacitor

$$i(t) = \frac{dq(t)}{dt}$$

$$q(t) = \int_{t_0}^t i(t)dt + q(t_0)$$

## SOURCES

- Voltage (V or J/C) – dc & ac
- Current (A or C/s) – dc & ac



# POWER & ENERGY

- The current  $i$  is the rate of flow of charge and the voltage  $v$  is a measure of the energy transferred per unit of charge, the product of the current and the voltage is the rate of energy transfer.
- Thus, the product of current and voltage is power.

$$p = v * i$$

- Volts \* Amperes = (joules/coulomb) \* (coulombs/second) = joules/second = watts

# POWER & ENERGY

- To calculate the energy  $w$  delivered to a circuit element between time instants  $t_1$  and  $t_2$ , we integrate power

$$w = \int_{t_1}^{t_2} p(t) dt$$

- The units of energy is joules (J)

# EXAMPLE 3 & 4: ENERGY & POWER

- Voltage is 12V and Current is 2 A.  
Calculate the power

$$p = v * i$$

$$p = 24 \text{ W}$$

- Voltage is 12V and Current is  $2e^{-t}$ .  
Calculate the power and energy for the intervals from  $t_1 = 0$  to  $t_2 = \infty$

$$p = 12 * 2e^{-t}$$

$$p = 24e^{-t} \text{ W}$$

- Energy:

$$w = \int_0^{\infty} 24e^{-t} dt$$


$$p = 24 \text{ J}$$

# RESISTORS AND OHM'S LAW



- The relationship between Voltage, Current and Resistance in any DC electrical circuit was firstly discovered by the German physicist Georg Ohm.
- The voltage  $V$  across an ideal resistor is proportional to the current  $I$  through the resistor  $R$ .

$$V = I * R$$

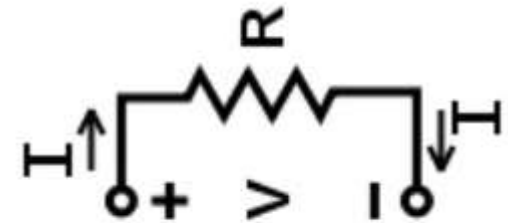
- The units of resistance are V/A, which are called ohms. The uppercase Greek letter omega ( $\Omega$ ) represents ohms.






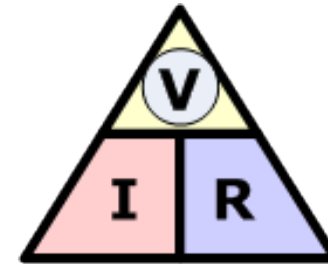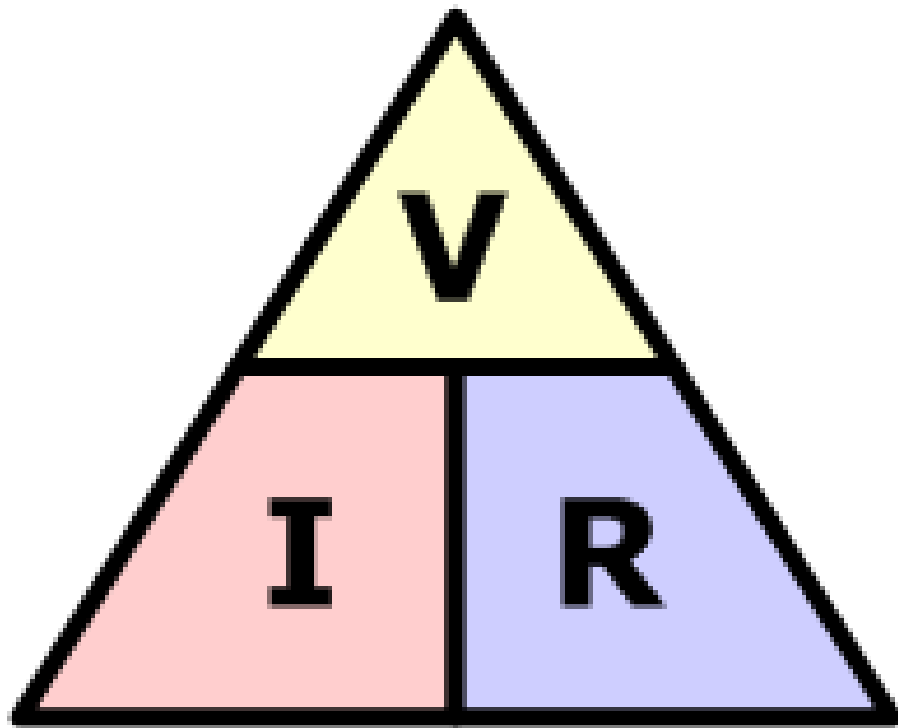

$$\textcircled{V} = I \times R$$


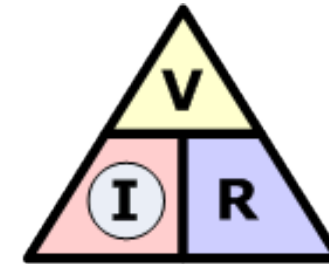


$$\textcircled{I} = \frac{V}{R}$$

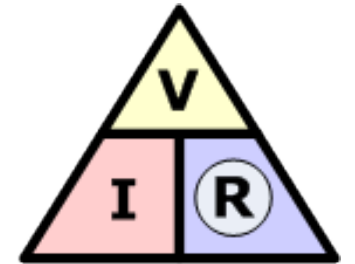


$$\textcircled{R} = \frac{V}{I}$$


# OHMS LAW TRIANGLE

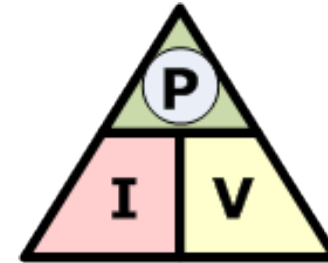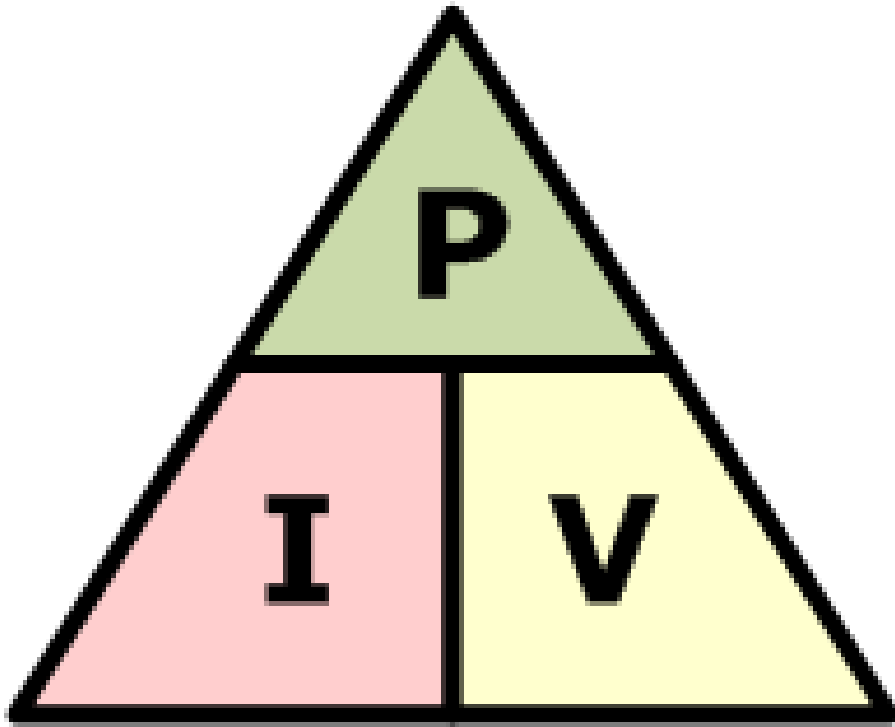

$$\textcircled{P} = I \times V$$

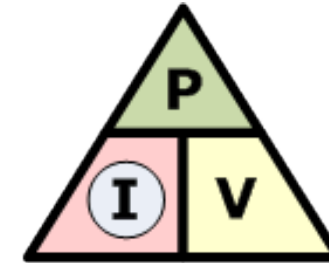

$$\textcircled{I} = \frac{P}{V}$$

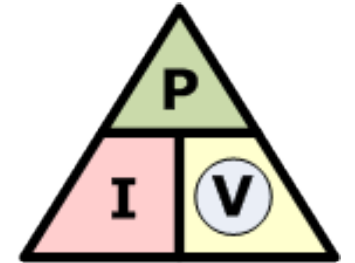


$$\textcircled{V} = \frac{P}{I}$$

# POWER TRIANGLE

I = Amps

V = Volts

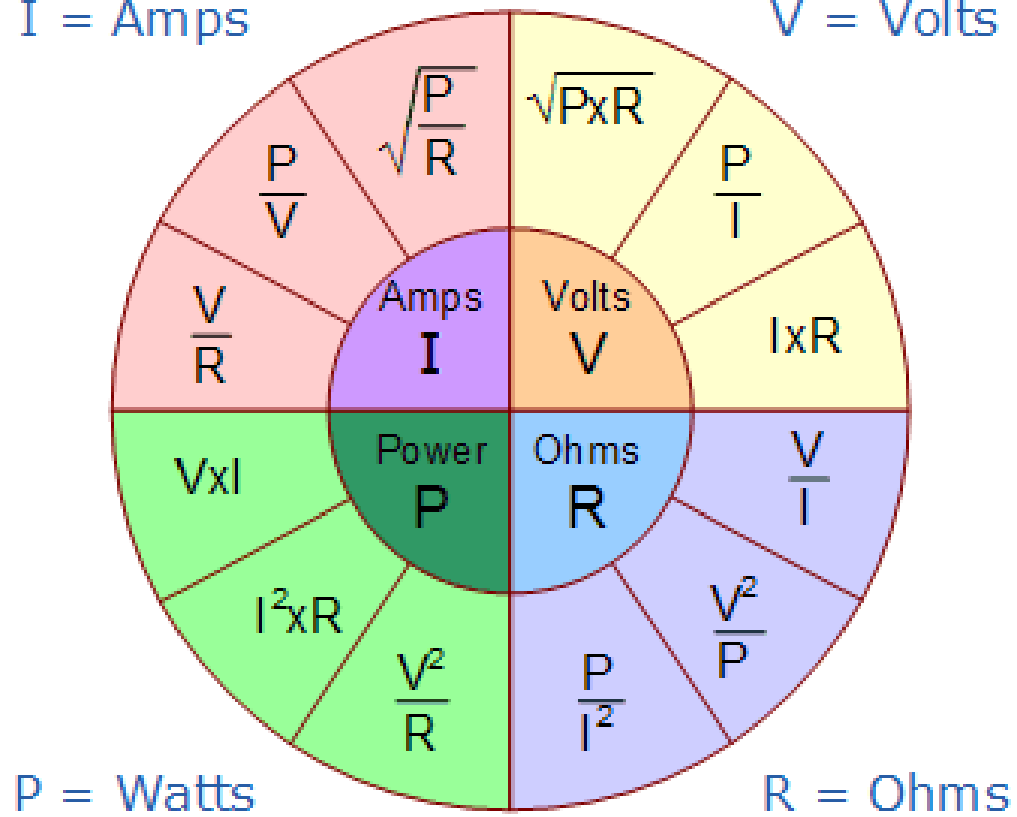

# OHMS LAW PIE CHART



# CONDUCTANCE

- Solving Ohm's law for current, we have

$$i = \frac{1}{R} v$$


- We call the quantity  $\frac{1}{R}$  a conductance.
- It is customary to denote conductance with the letter G.

$$G = \frac{1}{R}$$

- Conductance's have the units of inverse ohms ( $\Omega^{-1}$ ), which are called siemens (abbreviated S). Thus, we can write Ohm's law as

$$i = G * v$$



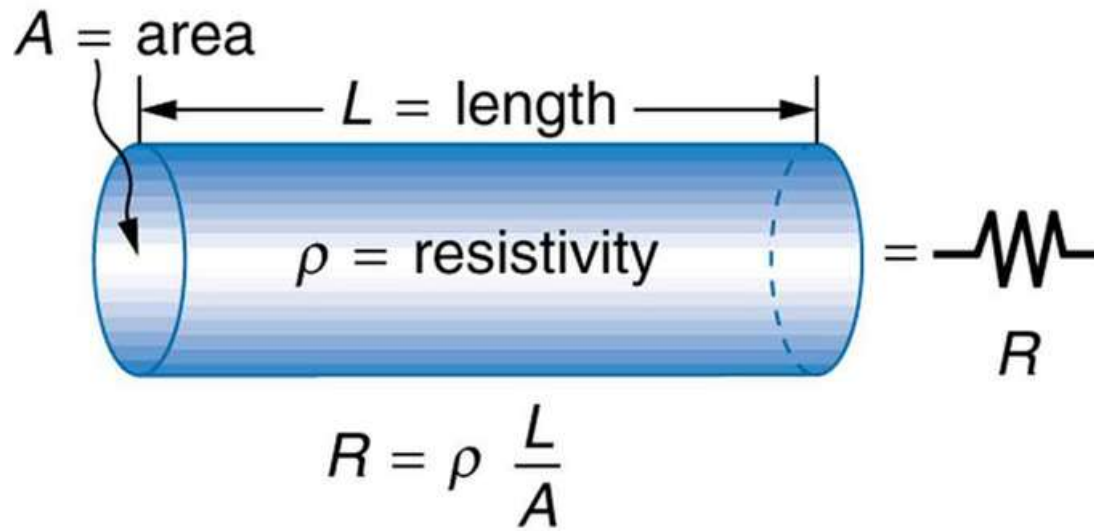

- The cross-sectional area  $A$  is constant along the length of the cylinder or bar. If the length  $L$  of the resistor is much greater than the dimensions of its cross section, the resistance is approximately given by

$$R = \frac{\rho L}{A}$$

- $\rho$  is the resistivity of the material used to construct the resistor.
- The units of resistivity are ohm meters ( $\Omega\text{m}$ )

# RESISTANCE RELATED TO PHYSICAL PARAMETERS

# RESISTANCE RELATED TO PHYSICAL PARAMETERS

- Materials can be classified as **conductors**, **semiconductors**, or **insulators**, depending on their resistivity.
- **Conductors** have the **lowest resistivity** and **easily conduct electrical current**.
- **Insulators** have **very high resistivity** and **conduct very little current** (at least for moderate voltages).
- **Semiconductors** fall between conductors and insulators.



- Insulator
- conductors
- semiconductors



# ASSIGNMENT 1: RESISTANCE CALCULATION

Compute the resistance of a copper wire having a diameter of 2.05 mm and a length of 10 m. Note the resistivity of a copper is given as  $1.72 \times 10^{-8} \Omega\text{m}$ .



# ASSIGNMENT 2: MATCH THE FOLLOWING

- |                         |                      |
|-------------------------|----------------------|
| 1. Units of Voltage     | a. Watt              |
| 2. Units of Current     | b. $V=I \cdot R$     |
| 3. Units of Power       | c. Ohm ( $\Omega$ )  |
| 4. Units of Resistance  | d. Ampere (A or C/s) |
| 5. Units of Charge      | e. Volt (V or J/C)   |
| 6. Units of Energy      | f. $P=V \cdot I$     |
| 7. Units of Conductance | g. Siemens (S)       |
| 8. Ohm's law            | h. $(R \cdot A)/L$   |
| 9. Power                | i. Joules (J)        |
| 10. Resistivity         | j. C                 |