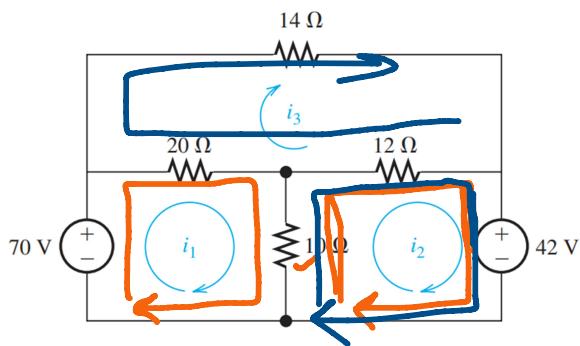


# Mesh Current Analysis Example 1

Thursday, 23 July, 2020 11:36 AM

Solve for the current in each element of the circuit shown in Figure



$$\begin{aligned} (30) \quad & i_1 + (-10) i_2 + (-20) i_3 = 70 \\ (-10) \quad & i_1 + (22) i_2 + (-12) i_3 = -42 \\ (-20) \quad & i_1 + (-12) i_2 + (46) i_3 = 0 \end{aligned}$$

Mesh Currents - 3

$i_1, i_2, i_3$

Loop 1:

$$-70 + 20(i_1 - i_3) + 10(i_1 - i_2) = 0$$

Loop 2:

$$(i_2 - i_1)10 + (i_2 - i_3)12 + 42 = 0$$

Loop 3:


$$(i_3 - i_1)20 + 14(i_3) + (i_3 - i_2)12 = 0$$

$$\begin{bmatrix} 30 & -10 & -20 \\ -10 & 22 & -12 \\ -20 & -12 & 46 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 70 \\ -42 \\ 0 \end{bmatrix}$$

$$I_1 = 4 \text{ A}$$

$$I_2 = 1 \text{ A}$$

$$I_3 = 2 \text{ A}$$

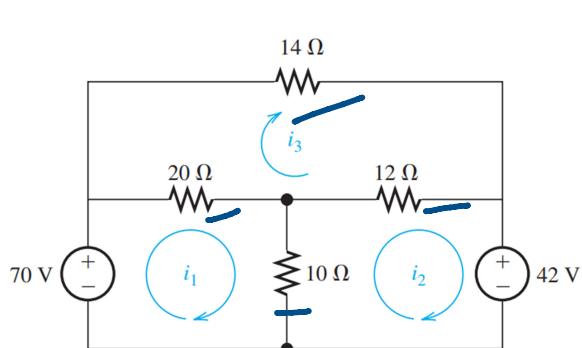

$$20 \text{ Ohms} = i_1 - i_3 = 2 \text{ A}$$

$$10 \text{ Ohms} = i_1 - i_2 = 3 \text{ A}$$

$$12 \text{ Ohms} = i_3 - i_2 = 1 \text{ A}$$


$$14 \text{ Ohms} = i_3 = 2 \text{ A}$$

## Example 2

Thursday, 23 July, 2020

11:38 AM

- Write Mesh-Current Equations in Matrix form

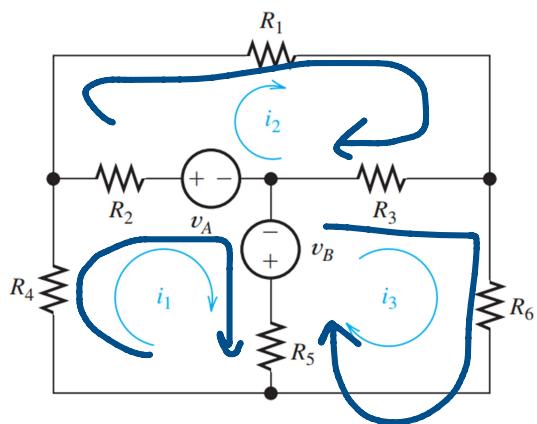

Loop 1:

$$I_1 R_4 + (i_1 - i_2)R_2 + V_a - V_b + (i_1 - i_3)R_5 = 0$$

Loop 2:

$$(i_2)R_1 + (i_2 - i_3)R_3 - V_a + (i_2 - i_1)R_2 = 0$$

Loop 3:

$$(i_3 - i_2)R_3 + (i_3)R_6 + (i_3 - i_1)R_5 + V_b = 0$$

$$(R_2 + R_4 + R_5) i_1 + (-R_2) i_2 + (-R_5) i_3 = -V_a + V_b$$


$$(-R_2) i_1 + (R_1 + R_2 + R_3) i_2 + (-R_3) i_3 = V_a$$

$$(-R_5) i_1 + (-R_3) i_2 + (R_3 + R_5 + R_6) i_3 = -V_b$$

$$\begin{bmatrix} (R_2 + R_4 + R_5) & (-R_2) & (-R_5) \\ (-R_2) & (R_1 + R_2 + R_3) & (-R_3) \\ (-R_5) & (-R_3) & (R_3 + R_5 + R_6) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_b - V_a \\ V_a \\ -V_b \end{bmatrix}$$

## Example 3 - Mesh Currents in Circuits Containing Current Sources

Thursday, 23 July, 2020 11:38 AM

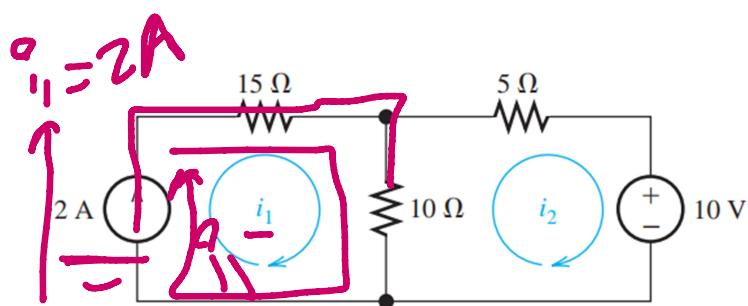

- Solve for mesh-currents

Loop 2:

$$(i_2 - i_1)10 + (i_2)5 + 10 = 0$$

Loop 1:

$$I_1 = 2A$$


$$(-10)i_1 + (15)i_2 = -10$$

$$I_2 = 0.67A$$

## Example 4

Thursday, 23 July, 2020 11:38 AM

## Solve for Mesh Currents

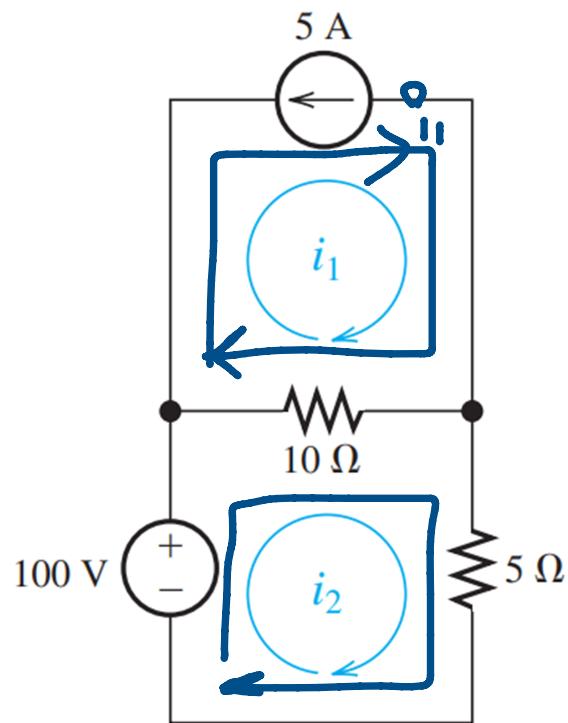

Loop 1:

$$I1 = -5A$$

Loop 2:

$$(i_2 - i_1)10 + 5(i_2) - 100 = 0$$


$$-10i_1 + 15i_2 = 100$$

$$I2 = 3.33 A$$
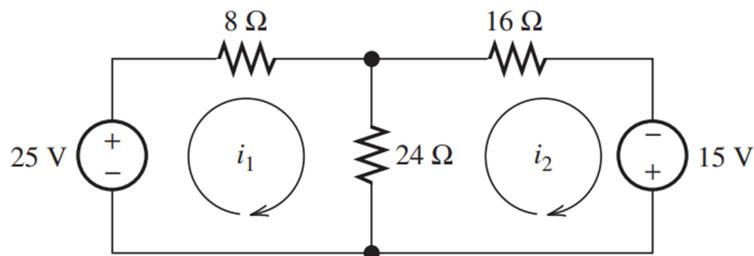
## Example 5

Thursday, 23 July, 2020 11:38 AM

- Solve for the power delivered to the 24 Ohms resistor and for the mesh currents shown in Figure



$$P|24\text{Ohms} = V * I$$

$$= V * (I_1 - I_2)$$

$$= ((I_1 - I_2) * 24) (I_1 - I_2)$$

$$= 3.84 \text{ W}$$

Loop 1:

$$8i_1 + 24(i_1 - i_2) - 25 = 0$$

Loop 2:

$$(i_2 - i_1)24 + (i_2) 16 - 15 = 0$$

$$(32)i_1 + (-24)i_2 = 25$$

$$(-24)i_1 + (40)i_2 = 15$$


$$I_1 = 1.93 \text{ A}$$

$$I_2 = 1.53 \text{ A}$$

## Example 6

Thursday, 23 July, 2020 11:38 AM

- Use mesh-current analysis to find the value of  $i_1$  in the circuit of Figure

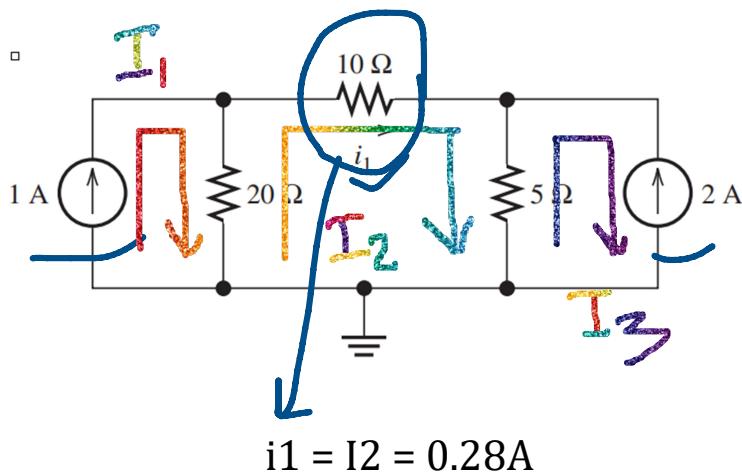

Loop 1:

$$I_1 = 1A$$

Loop 2:

$$(I_2 - I_1)20 + 10I_2 + (I_2 - I_3)5 = 0$$

Loop 3:

$$I_3 = -2A$$


$$(-20)I_1 + (35)I_2 + (-5)I_3 = 0$$

$$(-20*1) + (35)I_2 + (-5*-2) = 0$$

$$-20 + 35I_2 + 10 = 0$$


$$35I_2 = 10$$

$$I_2 = 10/35 = 0.28A$$

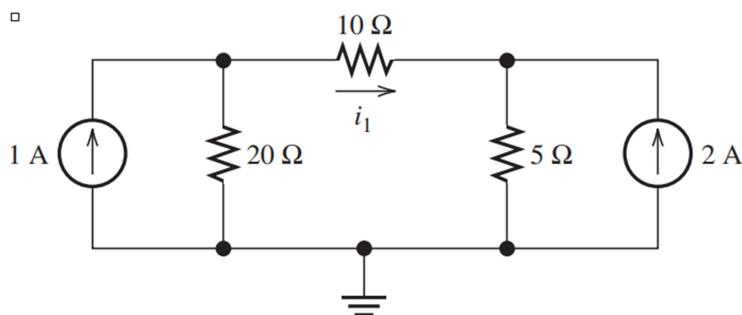

## Example 7

Thursday, 23 July, 2020 11:38 AM

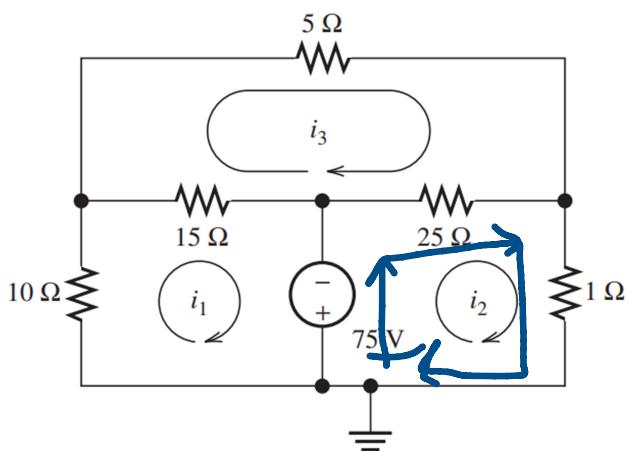

- Solve for the power delivered by the voltage source in Figure, using the mesh current method.

Loop 1:

$$10i_1 + (i_1 - i_3)15 - 75 = 0$$

Loop 2:

$$25(i_2 - i_3) + (i_2)1 + 75 = 0$$

Loop 3:

$$(i_3 - i_1)15 + (i_3)5 + (i_3 - i_2)25 = 0$$

$$I_1 = 1.64 \text{ A}$$

$$I_2 = -5.06 \text{ A}$$

$$I_3 = -2.27 \text{ A}$$

$$P|75V = V * I$$

$$= 75 * (I_2 - I_1)$$

$$= 75 (-5.06 - 1.64)$$

$$= W$$

$$(25) i_1 + (0) i_2 + (-15) i_3 = 75$$

$$(0) i_1 + (26) i_2 + (-25) i_3 = -75$$

$$(-15) i_1 + (-25) i_2 + (45) i_3 = 0$$

## Example 8

Thursday, 23 July, 2020 11:38 AM

- Use mesh-current analysis to determine the voltage magnitude for each resistor

