

Ex. No.:3

Date:07/08/2020

**Verification of NETWORK THEOREMS –
Thevenin's and Maximum Power Transfer**

Aim:

- 1. Calculate the V_{th} and R_{th} of the given circuit**
- 2. Draw the Thevenin's equivalent circuit and connect load resistor R_L .**
- 3. Find the power delivered to the load resistor for three values of R_L – 6 ohms, R_{th} and 9 ohms and get the maximum power transferred.**

Apparatus/Tool required:

ORCAD / Capture CIS --> kAnalog Library – R,


Source Library – Vdc, Idc &

Ground (GND) – 0 (zero)

Simulation Settings: Analysis Type - Bias Point

Circuit

Diagram:

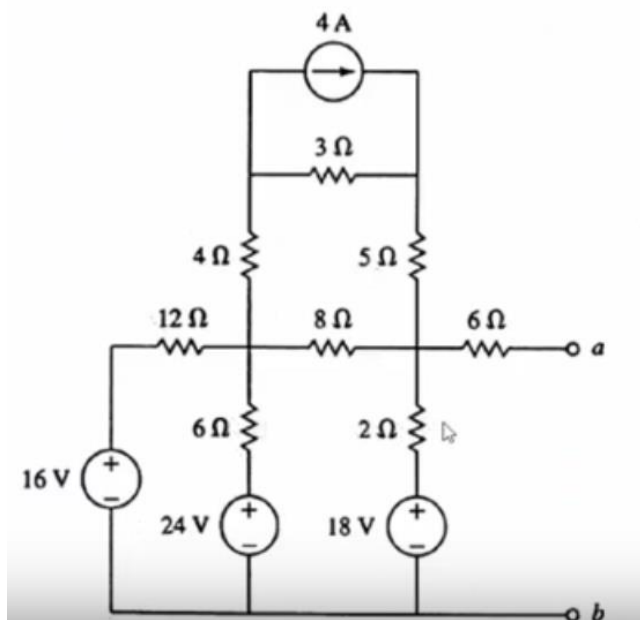


Statement:**Thevenin's Theorem:**

Any linear electrical network with voltage and current sources and only resistances can be replaced at terminals A-B by an equivalent voltage source V_{th} in series connection with an equivalent resistance R_{th} . This equivalent voltage V_{th} is the voltage obtained at terminals A-B of the network with terminals A-B open circuited. This equivalent resistance R_{th} is the resistance obtained at terminals A-B of the network with all its independent current sources open circuited and all its independent voltage sources short circuited

Maximum Power Transfer Theorem:

The maximum power from a source is delivered to a network (black box) which has an internal resistance (R_{th}) and source (V_{th}) with an external load resistance (R_L) in series, if the resistances connected in series are equal.

Manual Calculations:**To Find V_{th} :**

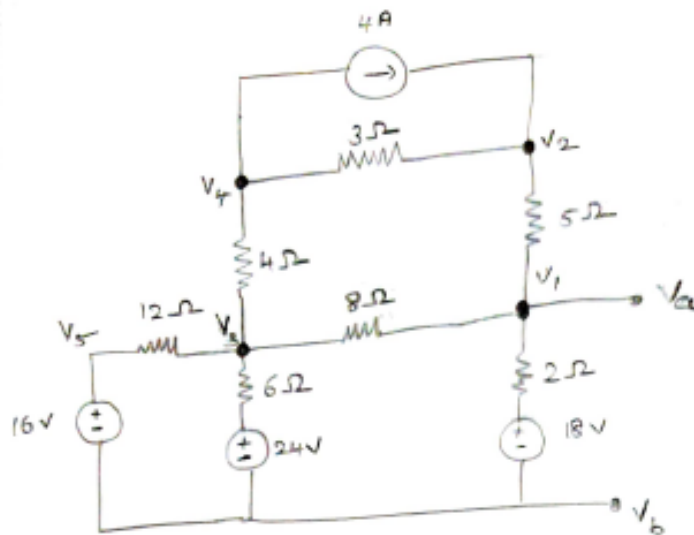

$$V_5 \Rightarrow 16V$$

At Node 1)

$$\frac{V_3 - V_5}{12} + \frac{V_3 - V_4}{4} + \frac{V_3 - 24}{6} + \frac{V_3 - V_1}{8} \Rightarrow 0$$

$$\frac{V_3 - 16}{12} + \frac{V_3 - V_4}{4} + \frac{V_3 - 24}{6} + \frac{V_3 - V_1}{8} \Rightarrow 0$$

$$\frac{V_3}{12} - \frac{16}{12} + \frac{V_3}{4} - \frac{V_4}{4} + \frac{V_3}{6} - \frac{24}{6} + \frac{V_3}{8} - \frac{V_1}{8} \Rightarrow 0$$

$$0.083V_3 - 1.33 + 0.25V_3 - 0.25V_4 + 0.166V_3 - 4 + 0.125V_3 - 0.125V_1 \Rightarrow 0$$

$$-0.125V_1 + (0.083 + 0.25 + 0.166 + 0.125)V_3 - 0.25V_4 - 1.33 - 4 \Rightarrow 0$$

$$-0.125V_1 + 0.624V_3 - 0.25V_4 - 5.33 \Rightarrow 0$$

$$-0.125V_1 + 0.624V_3 - 0.25V_4 - 5.33 \Rightarrow 0$$

$$0.125V_1 - 0.624V_3 + 0.25V_4 \Rightarrow -5.33$$

Node 2)

$$\frac{V_4 - V_2}{3} + \frac{V_4 - V_3}{4} + 4 \Rightarrow 0$$

$$V_4/3 - V_2/3 + V_4/4 - V_3/4 \Rightarrow -4$$

$$0.33V_4 - 0.33V_2 + 0.25V_4 - 0.25V_3 \Rightarrow -4$$

$$0.33V_2 + 0.25V_3 - 0.58V_4 \Rightarrow 4$$

Node 3)

$$\frac{V_2 - V_4}{3} + \frac{V_2 - V_1}{5} - 4 \Rightarrow 0$$

$$0.33V_2 - 0.33V_4 + 0.2V_2 - 0.2V_1 \Rightarrow 4$$

$$0.2V_1 - 0.53V_2 + 0.33V_4 \Rightarrow -4$$

Node 4)

$$\frac{V_1 - V_2}{5} + \frac{V_1 - V_3}{8} + \frac{V_1 - 18}{2} \Rightarrow 0$$

$$0.2V_1 - 0.2V_2 + 0.125V_1 - 0.125V_3 + 0.5V_1 - 9 \Rightarrow 0$$

$$0.825V_1 - 0.2V_2 - 0.125V_3 \Rightarrow 9$$

$$\begin{array}{r} 0.2 \\ 0.5 \\ 0.125 \\ \hline 0.825 \end{array}$$

$$\therefore V_1 \Rightarrow 19.52 \text{ V}$$

$$V_2 \Rightarrow 24.07 \text{ V}$$

$$V_3 \Rightarrow 18.34 \text{ V}$$

$$V_4 \Rightarrow 14.70 \text{ V}$$


since, it is an open circuit the voltage across V_1 is the ~~the~~ ~~theven~~ voltage

$$V_{th} \Rightarrow V_{ab}$$

$$\Rightarrow 19.52 - 0$$

$$V_{th} \Rightarrow 19.52 \text{ V}$$

To Find R_{th} :

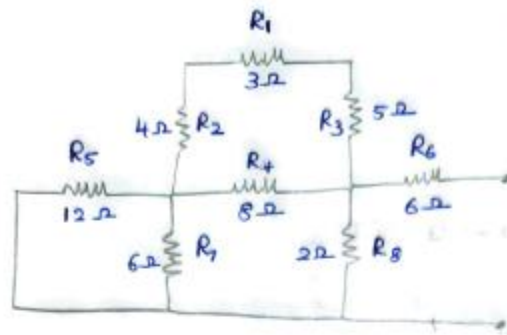

R_1, R_2 and R_3 are in series

$$R_{123} \Rightarrow 4 + 3 + 5 \Rightarrow 12 \Omega$$

R_{123} and R_4 are parallel

$$R_{1234} \Rightarrow \frac{R_{123} R_4}{R_{123} + R_4} \Rightarrow \frac{12(8)}{12+8} \Rightarrow \frac{96}{20} \Rightarrow 4.8 \Omega$$

R_5 and R_7 are parallel

$$R_{57} \Rightarrow \frac{12(6)}{12+6} \Rightarrow \frac{72}{18} \Rightarrow 4 \Omega$$

R_6 and R_8 are parallel

$$R_{68} \Rightarrow \frac{2(6)}{2+6} \Rightarrow \frac{12}{8} \Rightarrow 1.5 \Omega$$

R_{1234}, R_{57}, R_{68} are in series

$$R_{eq} \Rightarrow R_{1234} + R_{57} + R_{68}$$

$$\Rightarrow 4.8 + 4 + 1.5$$

R_{1234} and R_{57} and R_8 are in series

$$R_{123457} \Rightarrow 4.8 + 4 \\ \Rightarrow 8.8 \Omega$$


R_{123457} and R_6 are in parallel

$$R_{1234578} \Rightarrow R_{eq} \Rightarrow \frac{8.8(2)}{8.8+2} \Rightarrow \frac{17.6}{10.8} \Rightarrow 1.629 \Omega$$

$$R_{1234578} + R_6 \Rightarrow R_{eq} \Rightarrow 1.629 + 6$$

$R_{eq} \Rightarrow 7.629 \Omega$

To Find Power:

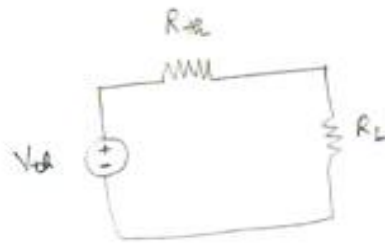

In this thevenin equivalent circuit,

$$V_{th} \approx 19.417 \text{ V}$$

$$R_{th} \approx 7.629 \Omega$$

Maximum }
$$P_L \approx \frac{V_{th}^2 R_L}{(R_{th} + R_L)^2}$$

power }

i) When $R_L \approx 6 \Omega$

$$P_L \approx \frac{(19.417)^2 (6)}{(6 + 7.629)^2}$$

$$P_L \approx 12.178 \text{ W}$$

ii) When $R_L \approx 9 \Omega$

$$P_L \approx \frac{(19.417)^2 (9)}{(9 + 7.629)^2}$$

$$P_L \approx 12.270 \text{ W}$$

ii) When $R_{th} = R_L$

$$P_L \Rightarrow \frac{V_{th}^2 R_L}{(R_{th} + R_L)^2}$$

$$R_{th} = R_L$$

$$\Rightarrow \frac{V_{th}^2 R_L}{(2 R_{th})^2} \Rightarrow \frac{V_{th}^2 \cancel{R_L}}{4 \cancel{R_{th}}}$$


$$\Rightarrow \frac{V_{th}^2}{4 R_{th}}$$

$$\Rightarrow \frac{(19.417)^2}{(4 * 7.629)}$$


$$P_{L_{max}} \Rightarrow 12.335 \text{ W}$$

The maximum power transferred is 12.335 W



To Find V_{th} :

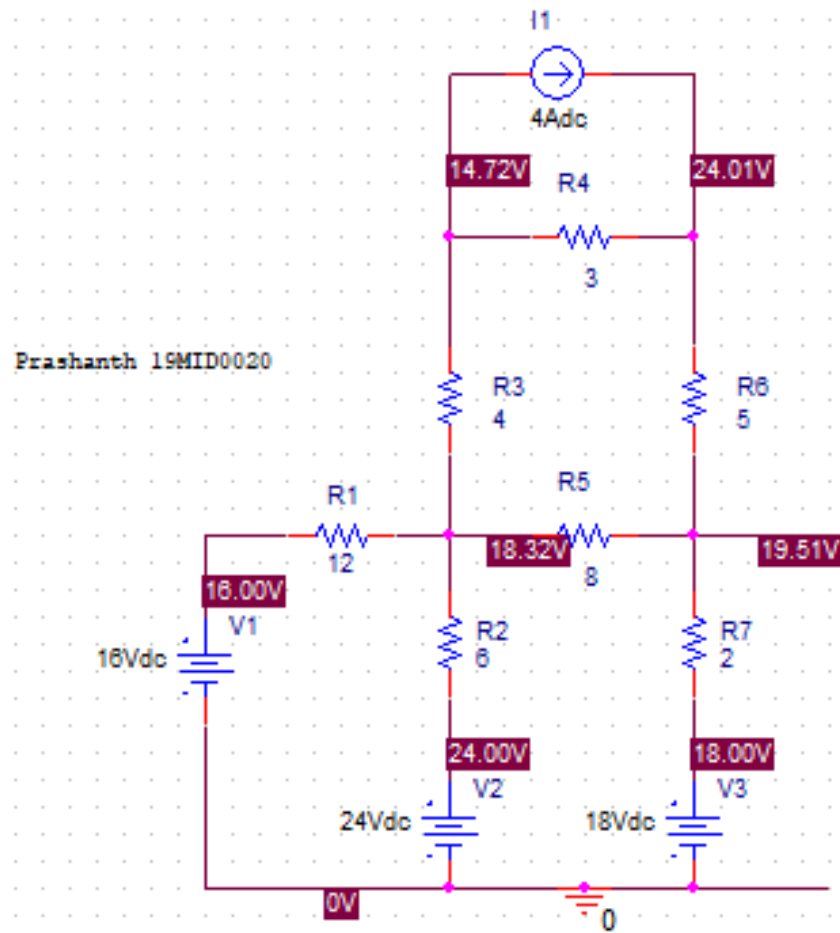


To Find R_{th} :

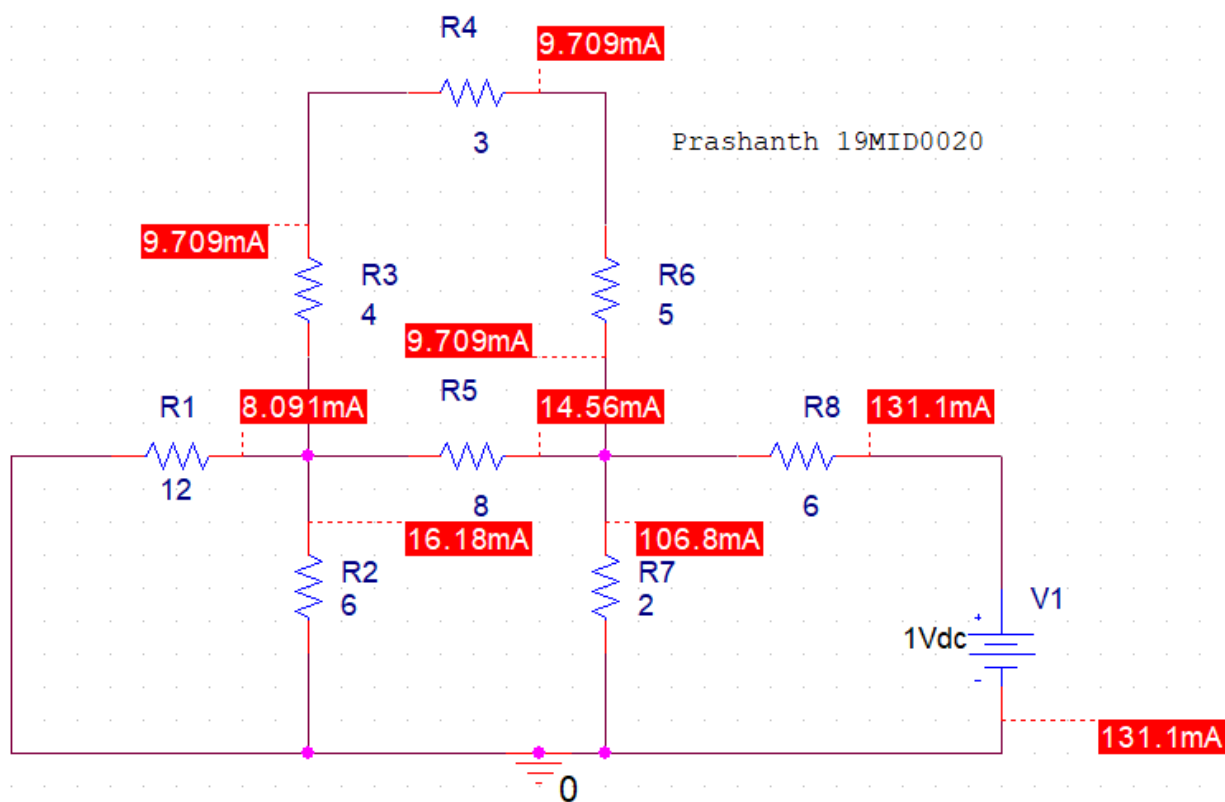

To Find Power:

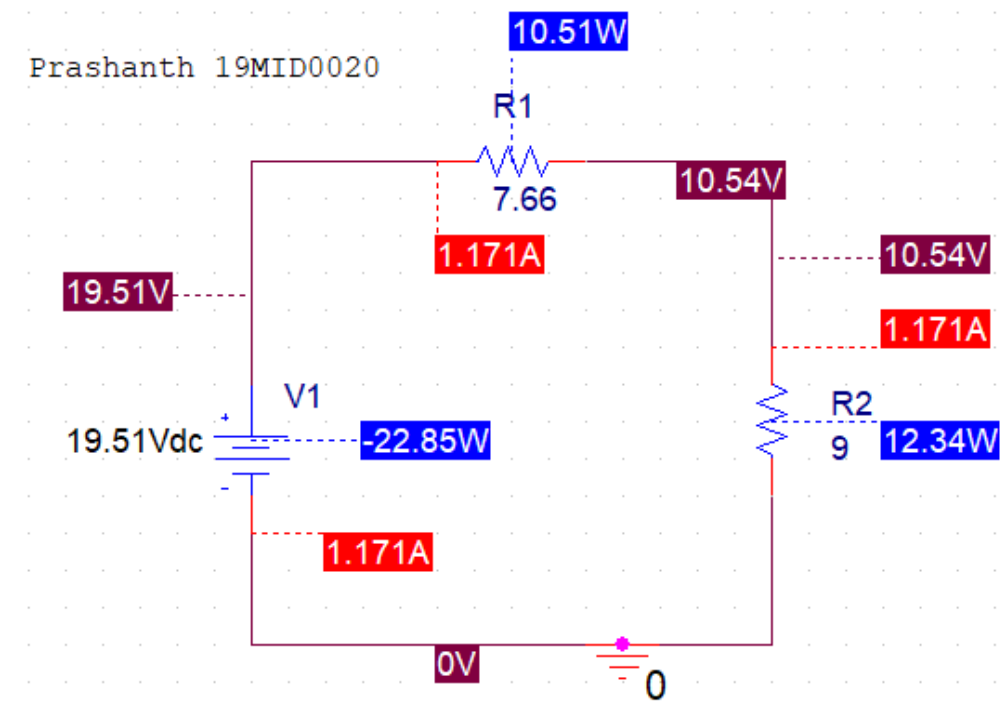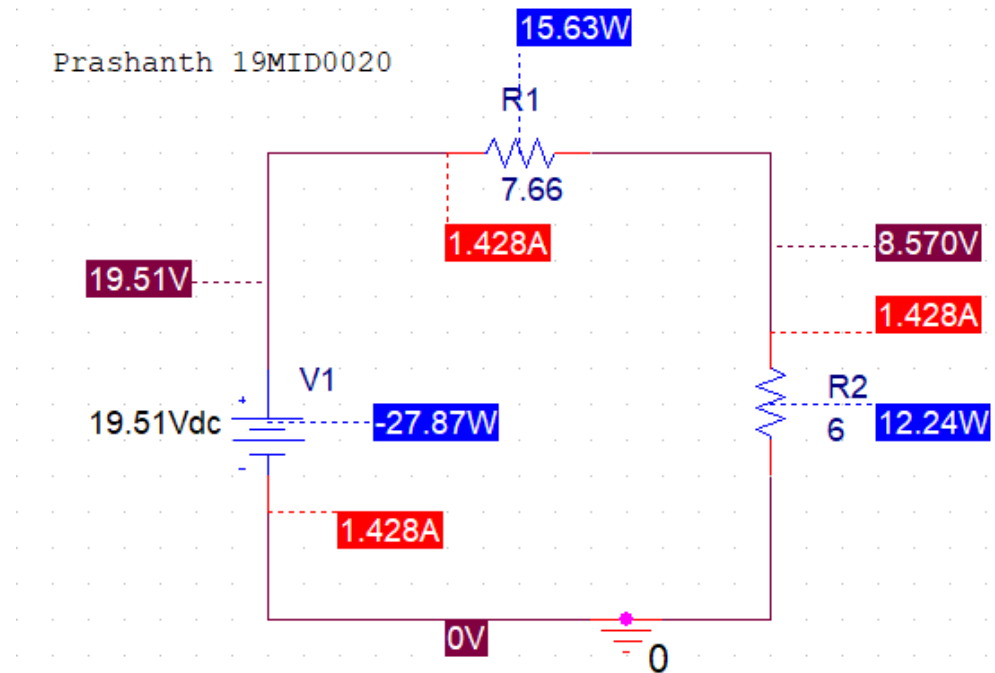

Prashanth 19MID0020

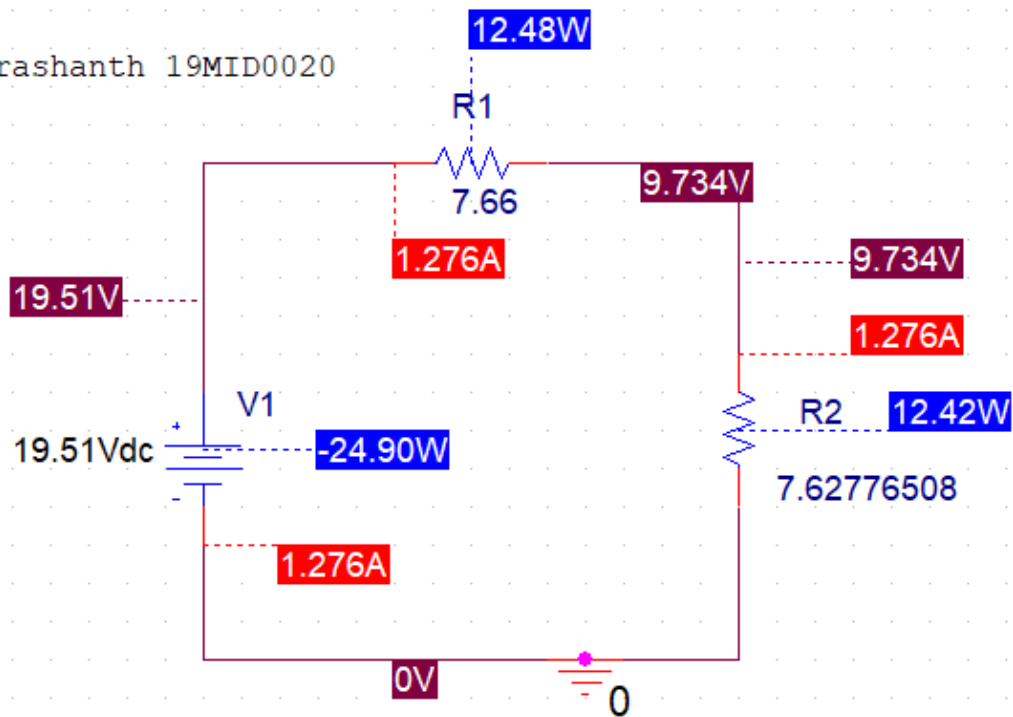

Result:

Thevenin's theorem & Max.Power transfer	Manual calulation	Simulation Result
V_{Th}	19.506 V	19.51 V
R_{Th}	7.629 Ω	7.62776506 Ω
P_L	12.29 W	12.30 W
P_L	12.383 W	12.39 W
P_{Lmax}	12.468 W	12.48 W

Inference :

The values of Manual calculations and Simulated circuit result are similar approximately equal. Hence Thevenin's theorem is verified

Inference :

The values of Manual calculations and Simulated circuit result are similar approximately equal. Hence Maximum Power Transfer theorem is verified

Reg. No: 19MID0020

Name: Prashanth.S

Date: 07/08/2020