
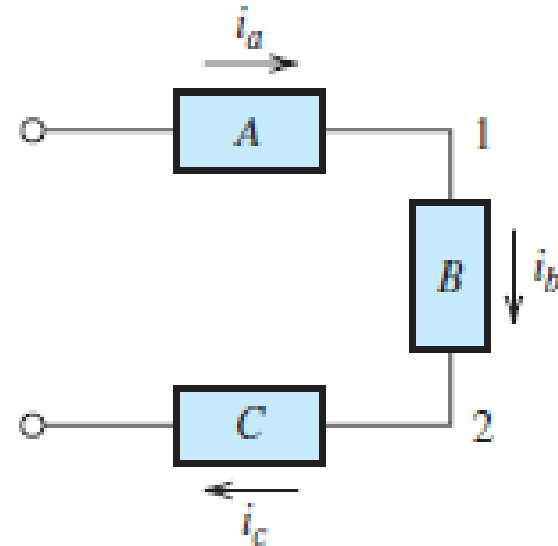


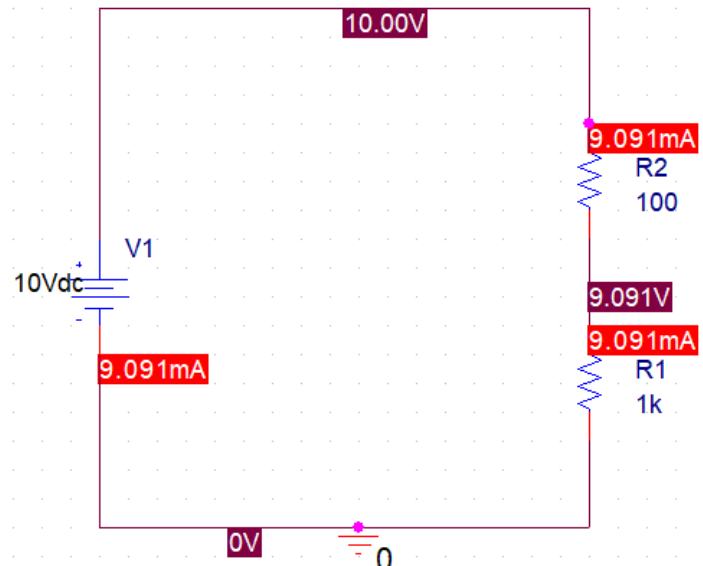

# **EEE1024: Fundamentals of Electrical and Electronics Engineering**

**Dr. Sanchit Khataavkar**

# Kirchhoff's Current law (KCL)



Elements connected from end to end ——— Series circuit

**CURRENT** in a **SERIES** circuit – remains same!


Apply KCL to check this!

@ Node 1,  $i_a = i_b$

@ Node 2,  $i_b = i_c$

Thus,  $i_a = i_b = i_c$

# Series Circuit

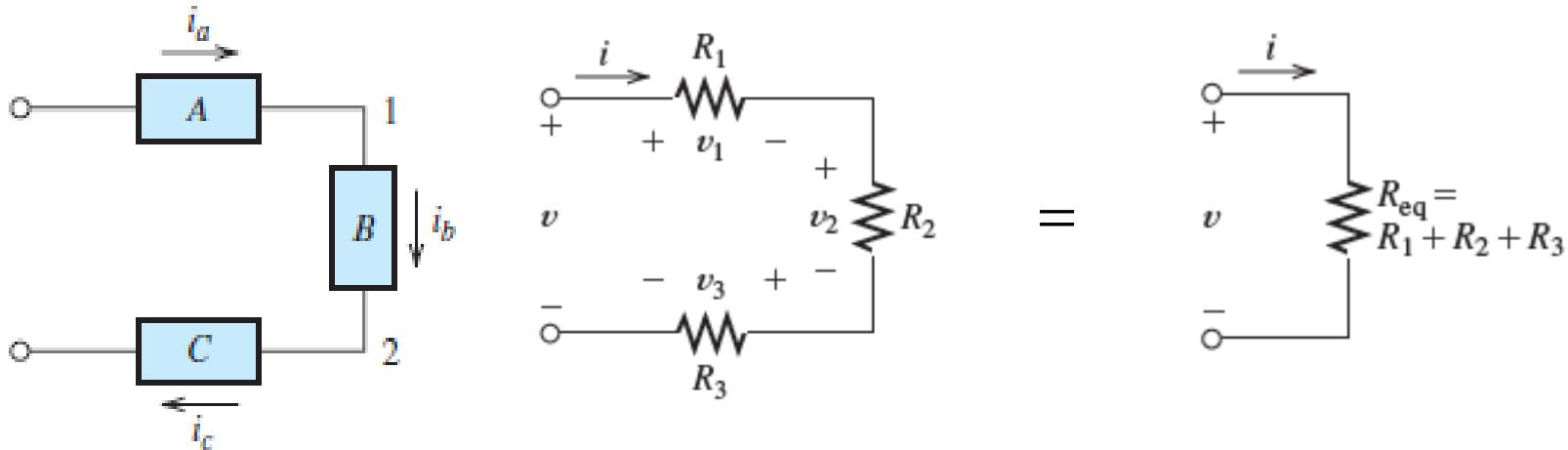

Ohm's law

$$\begin{aligned} v_1 &= R_1 i \\ v_2 &= R_2 i \\ v_3 &= R_3 i \end{aligned}$$

Apply KVL

$$v = v_1 + v_2 + v_3$$

Substituting

$$v = R_1 i + R_2 i + R_3 i$$

Factoring out

$$v = (R_1 + R_2 + R_3) i$$



Define an **equivalent resistance** -  $R_{eq}$

$$R_{eq} = R_1 + R_2 + R_3$$

$$v = R_{eq} i$$

Series combination of resistances has an **equivalent resistance** which is equal to sum of individual resistances

# Kirchhoff's Voltage law (KVL)

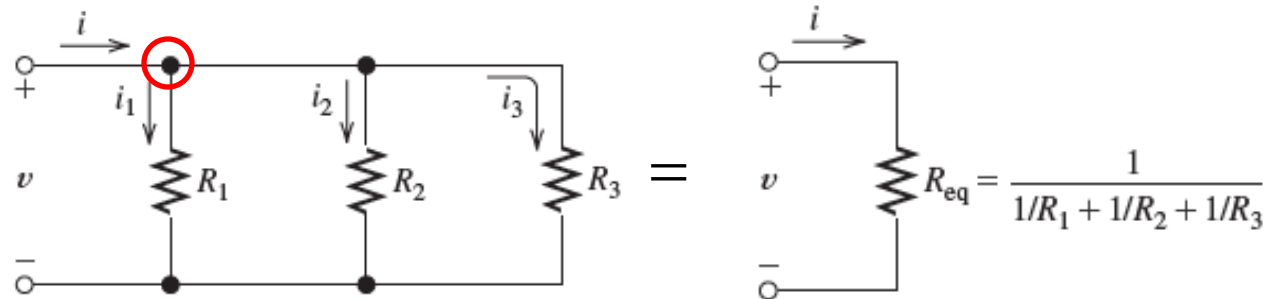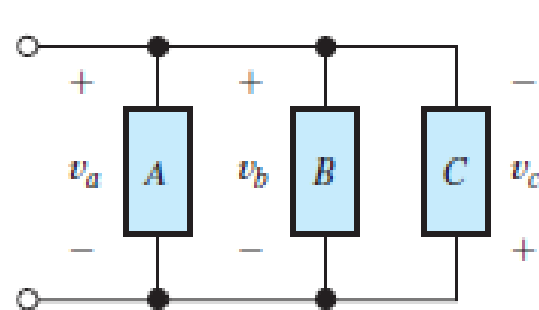


Ohm's law

$$i_1 = \frac{v}{R_1}$$

$$i_2 = \frac{v}{R_2}$$

$$i_3 = \frac{v}{R_3}$$

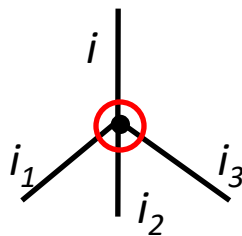

Apply KCL

$$i = i_1 + i_2 + i_3$$

Substituting

$$i = \frac{v}{R_1} + \frac{v}{R_2} + \frac{v}{R_3}$$

Factoring

$$i = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) v$$

Define an **equivalent resistance** -  $R_{eq}$

$$R_{eq} = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$$

$$i = \frac{1}{R_{eq}} v$$

Parallel combination of resistances also has an **equivalent resistance**.  
It can be replaced in place of the parallel combination, without changing V's and I's in other parts of circuit !

# Combining Resistances in series and parallel

For 3 resistances  
in llcl,

$$R_{eq} = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$$


For 2 resistances  
in llcl,

$$R_{eq} = \frac{1}{1/R_1 + 1/R_2}$$


OR

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


Example:

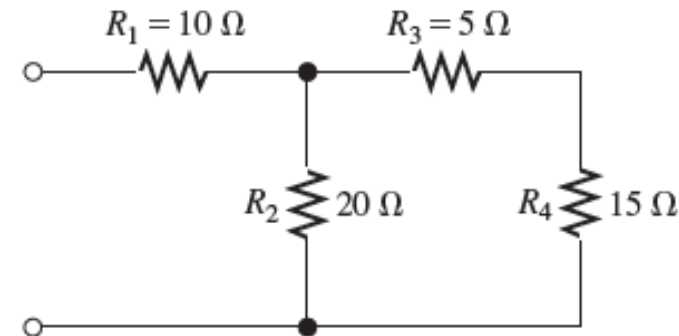

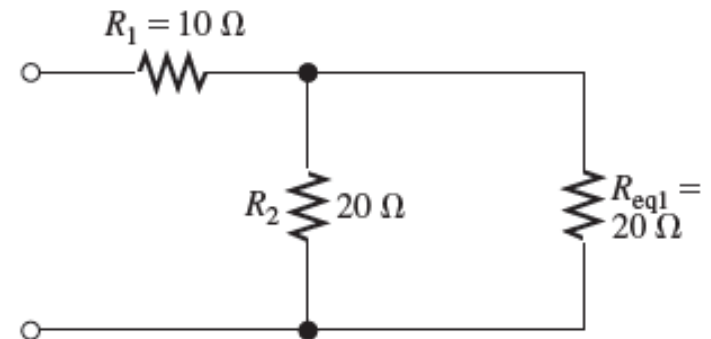
A)  $R_{eq1} = R_3 + R_4 = 5 + 15 = 20\ \Omega$



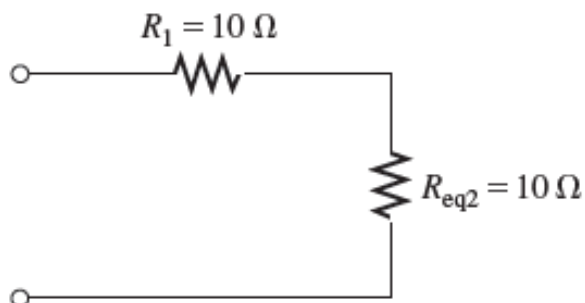
B)  $R_{eq2} = \frac{1}{1/R_{eq1} + 1/R_2} = \frac{1}{1/20 + 1/20} = 10\ \Omega$



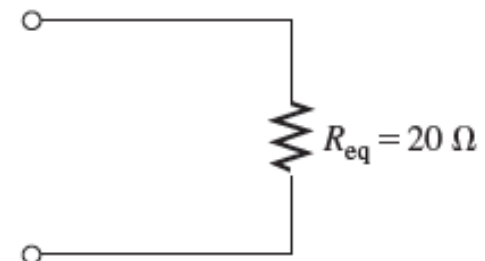C)  $R_{eq} = R_1 + R_{eq2} = 10 + 10 = 20\ \Omega$



# Node Voltage Analysis

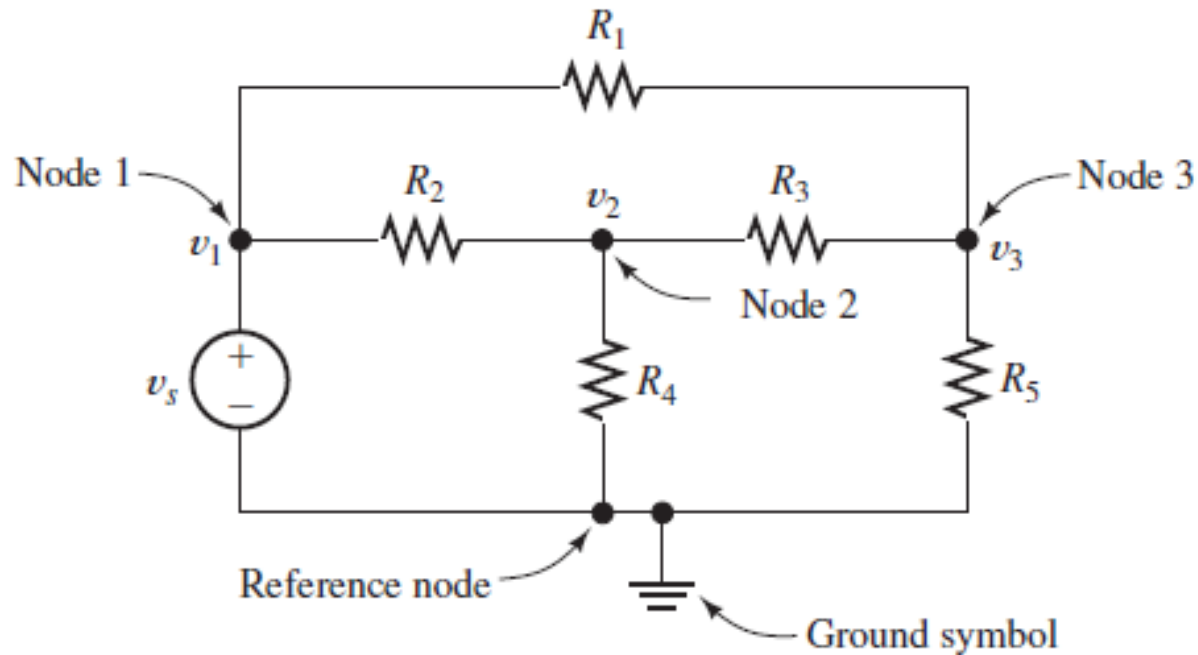

Series or parallel combinations – no use for this circuit!

# Acknowledgements

1. H. Hayt, J.E. Kemmerly and S. M. Durbin, 'Engineering Circuit Analysis', 6/e, Tata McGraw Hill, New Delhi, 2011
2. Allan R. Hambley, 'Electrical Engineering - Principles & Applications, Pearson Education, First Impression, 6/e, 2013