
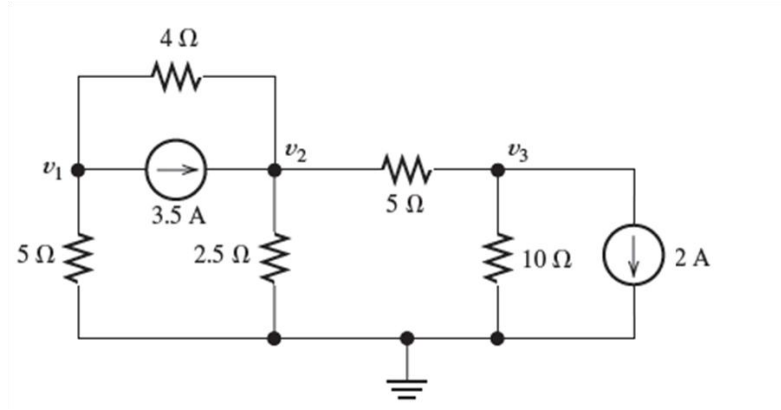


## PRACTICE EXAMPLES


1) Find node voltages

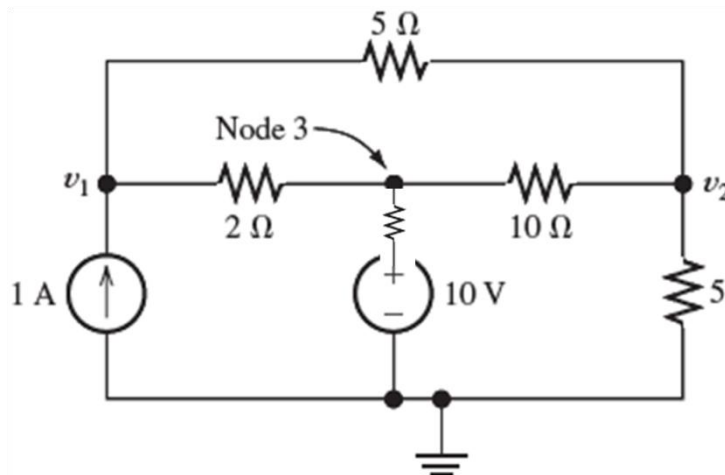


2) Find node voltages




3) Find mesh currents

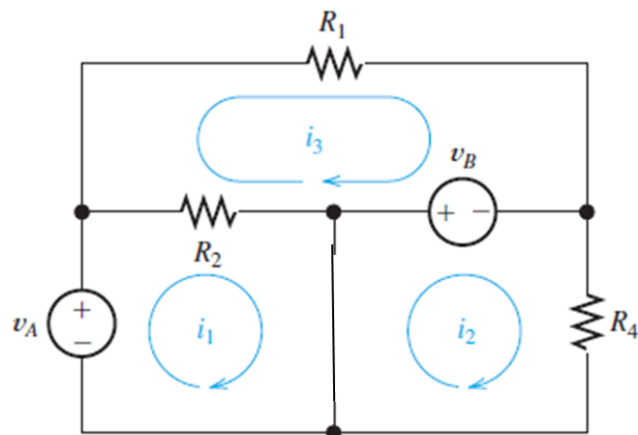

4) Find unknown currents

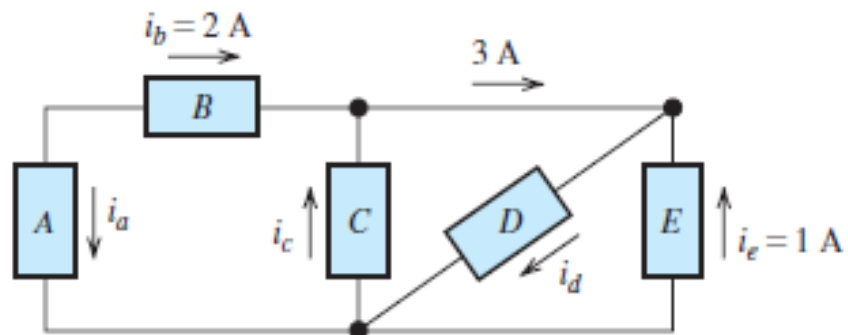

5) Find unknown voltages

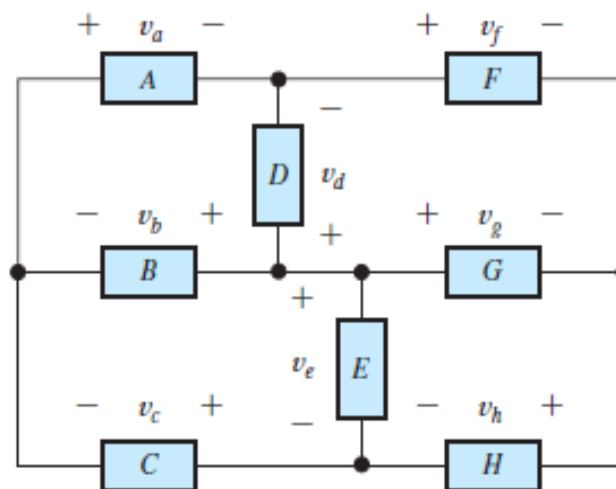

6) Find Thevenin resistance of circuit given below

