



# **EEE1024: Fundamentals of Electrical and Electronics Engineering**

**Dr. Sanchit Khataavkar**

# Course Outline

Comm.  
Systems

**Sensors**

**$\mu$  processor  
&  
 $\mu$  controller**

**Semiconductor  
Devices**

**Digital  
Systems**

**AC  
Circuits -  
Basics**

**DC  
Circuits -  
Basics**


# Direct Current Vs Alternating Current

*Thomas Elva Edison*

Current remains constant with time

Unidirectional

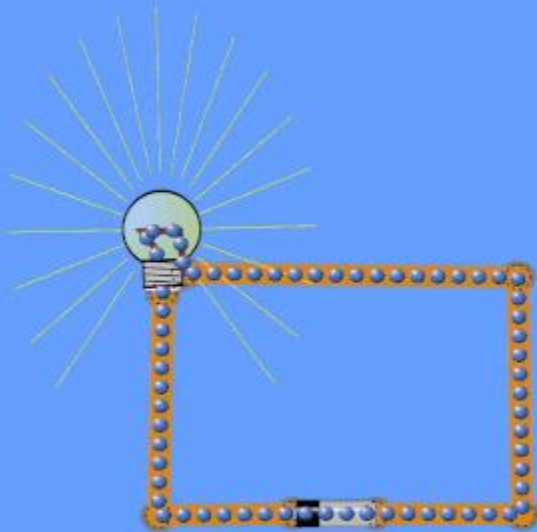DC: Constant flow of electrons from an area of high electron density to an area of low electron density.



Nikola Tesla

Current varies sinusoidally with time

Bi-directional

AC: Current will flip the direction of charge flow (60 times a second in USA (60 Hz) and 50 times a second in Europe (50 Hz) and also in ?






# Direct Current Vs Alternating Current

DC voltage



AC voltage

(the sine wave)

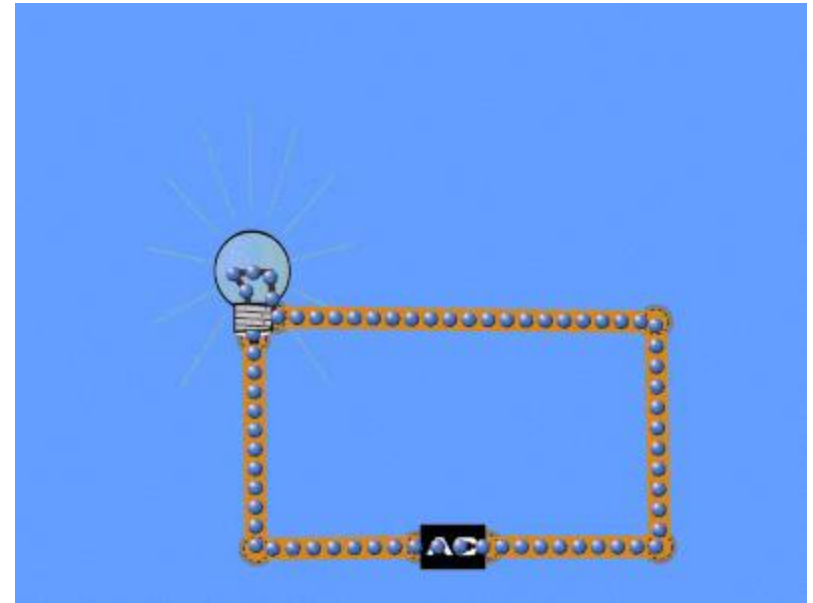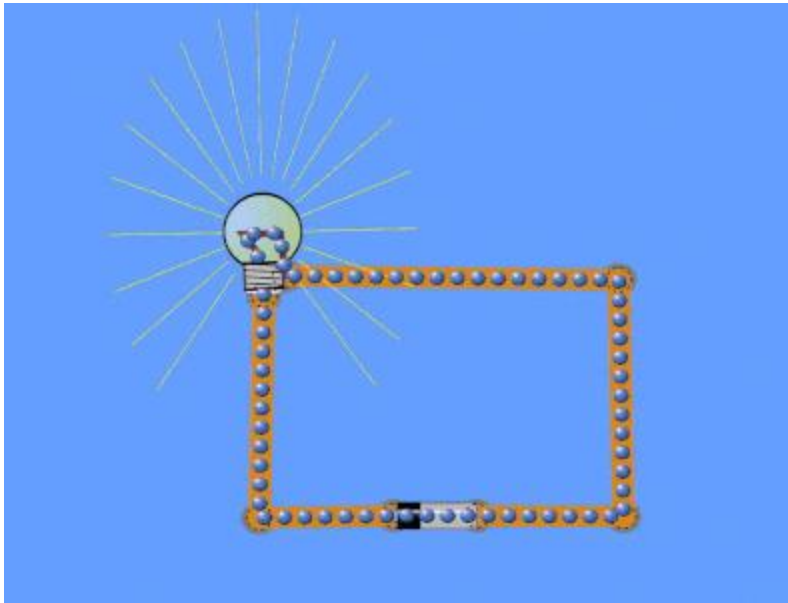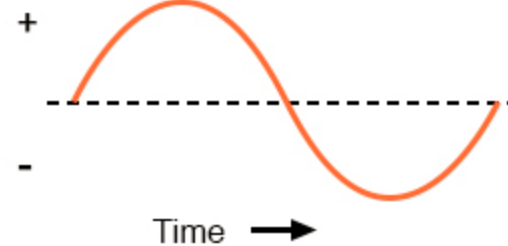


# Direct Current Vs Alternating Current


DC voltage



AC voltage

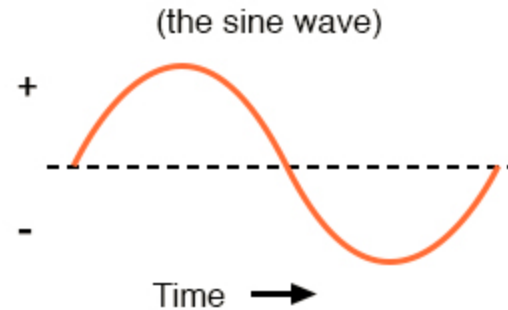

Periodic Motion

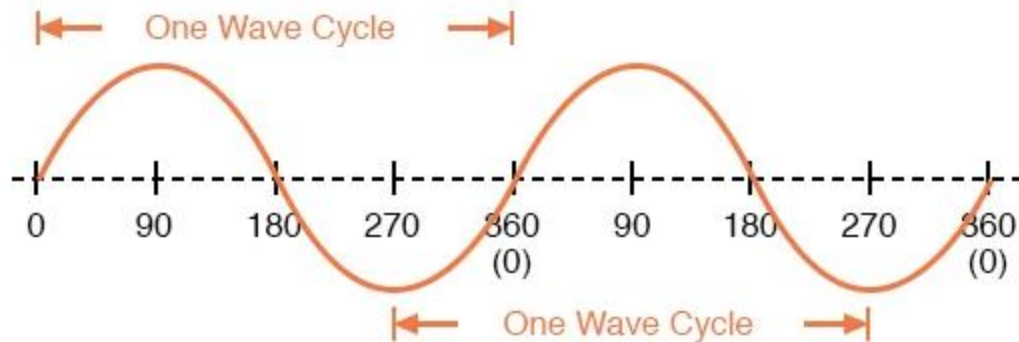


$$Frequency(Hz) = \frac{1}{Period(s)}$$


# Direct Current Vs Alternating Current

## *Types of waves*



Square Wave

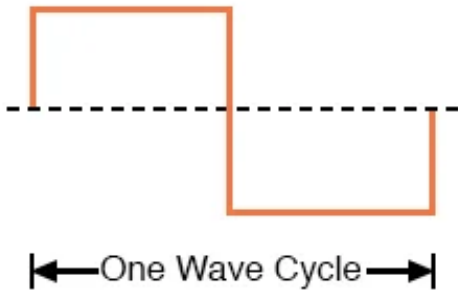


Triangle Wave

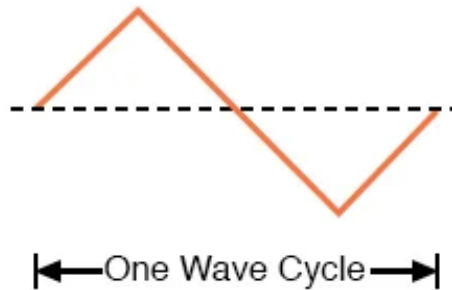


Sawtooth Wave

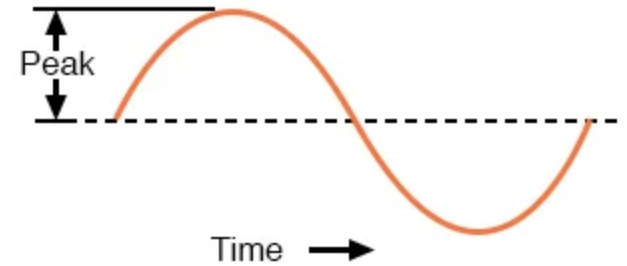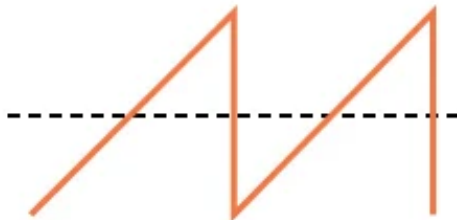



*Peak voltage of a waveform.*

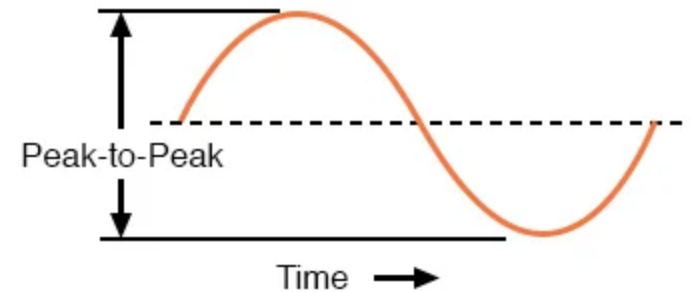


# Direct Current Vs Alternating Current

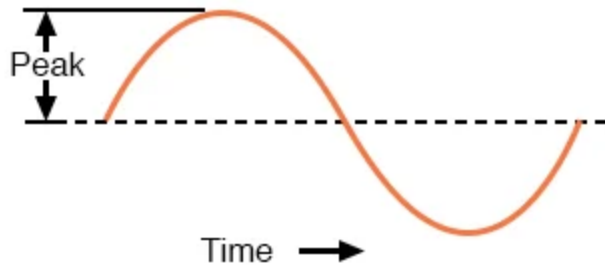

*Peak voltage of a waveform.*

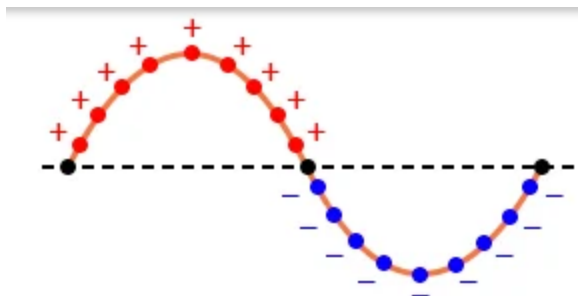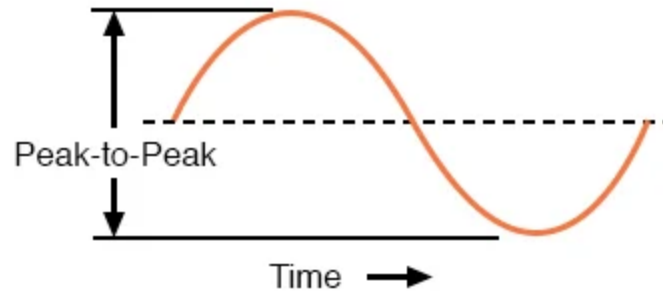

*True Average*

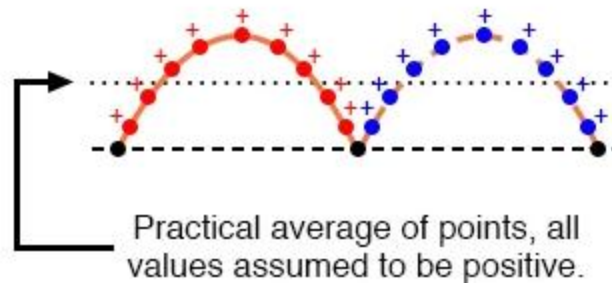

*Practical Average –  
Measured by meter*

AC




RMS –  
Root Mean Square



DC


# Direct Current Vs Alternating Current

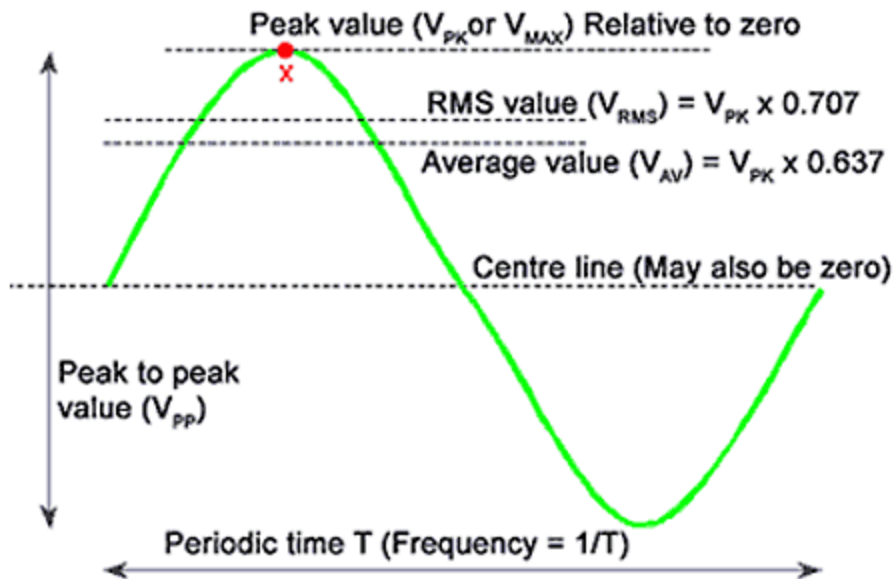

$$V_{AV} = V_{PK} \times 0.637$$

$$V_{RMS} = V_{PK} \times 0.707$$


$$V_{PP} = V_{PK} \times 2$$

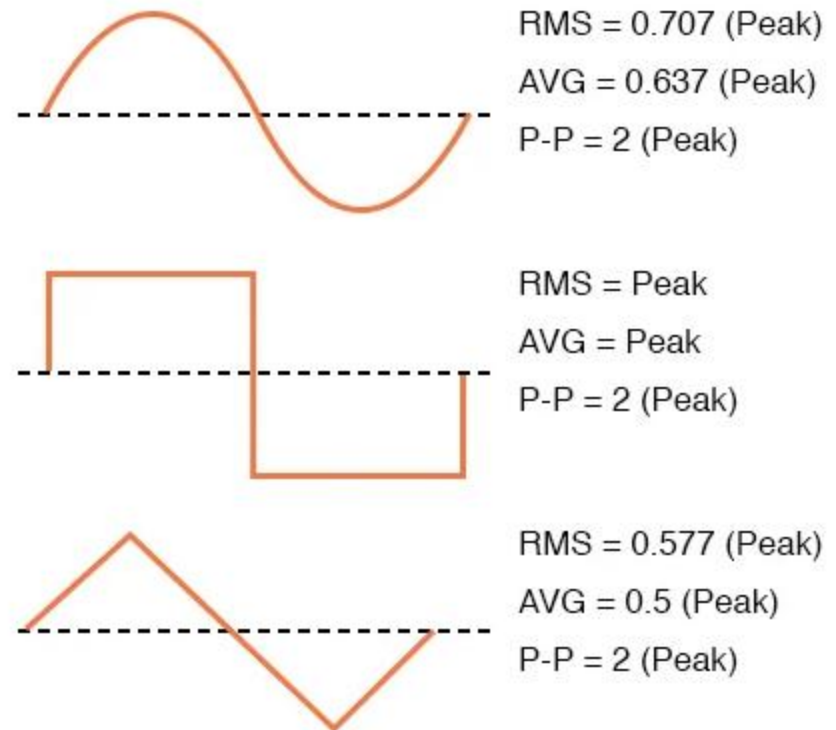



# Direct Current Vs Alternating Current

## *Resistive Circuit*

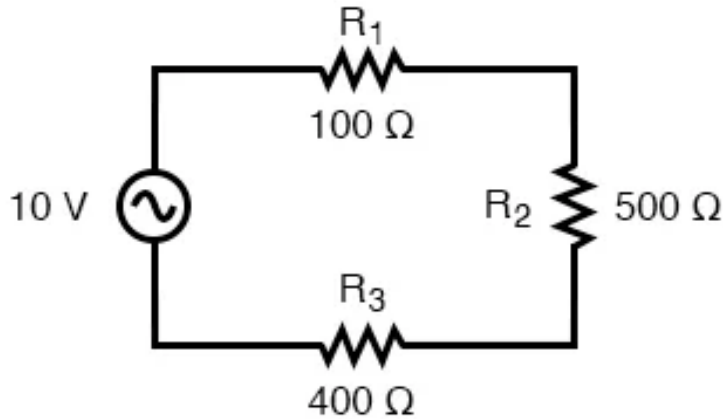

$$I = \frac{V}{R_{eq}}$$

$$R_{eq} = 100 + 500 + 400 = 1000\Omega (1k\Omega)$$

Series circuit – current same

$$I = \frac{10}{1000} = 0.01A = 10mA$$

$$V_{R1} = I \times R_1 = 1V$$


$$V_{R2} = I \times R_2 = 5V$$

$$V_{R3} = I \times R_3 = 4V$$

*AC circuit calculations for resistive circuits are the same as for DC!*

# Practice 1

Q1:

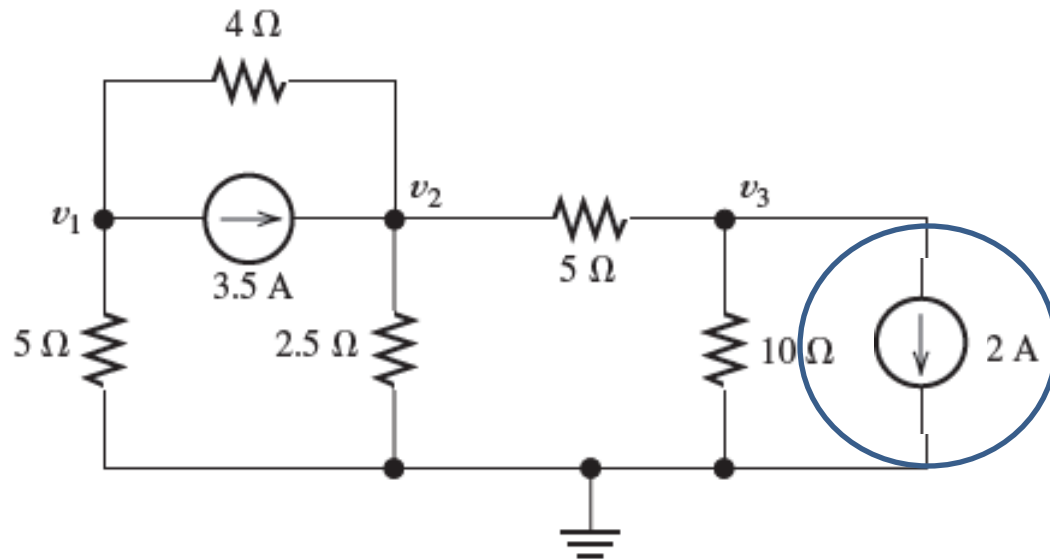

$$\frac{v_1}{5} + \frac{v_1 - v_2}{4} + 3.5 = 0$$

$$0.45v_1 - 0.25v_2 = -3.5$$

@1

$$\frac{v_2 - v_1}{4} + \frac{v_2}{2.5} + \frac{v_2 - v_3}{5} = 3.5$$

$$-0.25v_1 + 0.85v_2 - 0.2v_3 = 3.5$$

@2

$$\frac{v_3 - v_2}{5} + \frac{v_3}{10} = -2$$


$$-0.2v_2 + 0.35v_3 = 2$$

@3

$$V_1 = -5V \quad V_2 = 5V \quad V_3 = 10V$$


# Practice 2

Q 2:

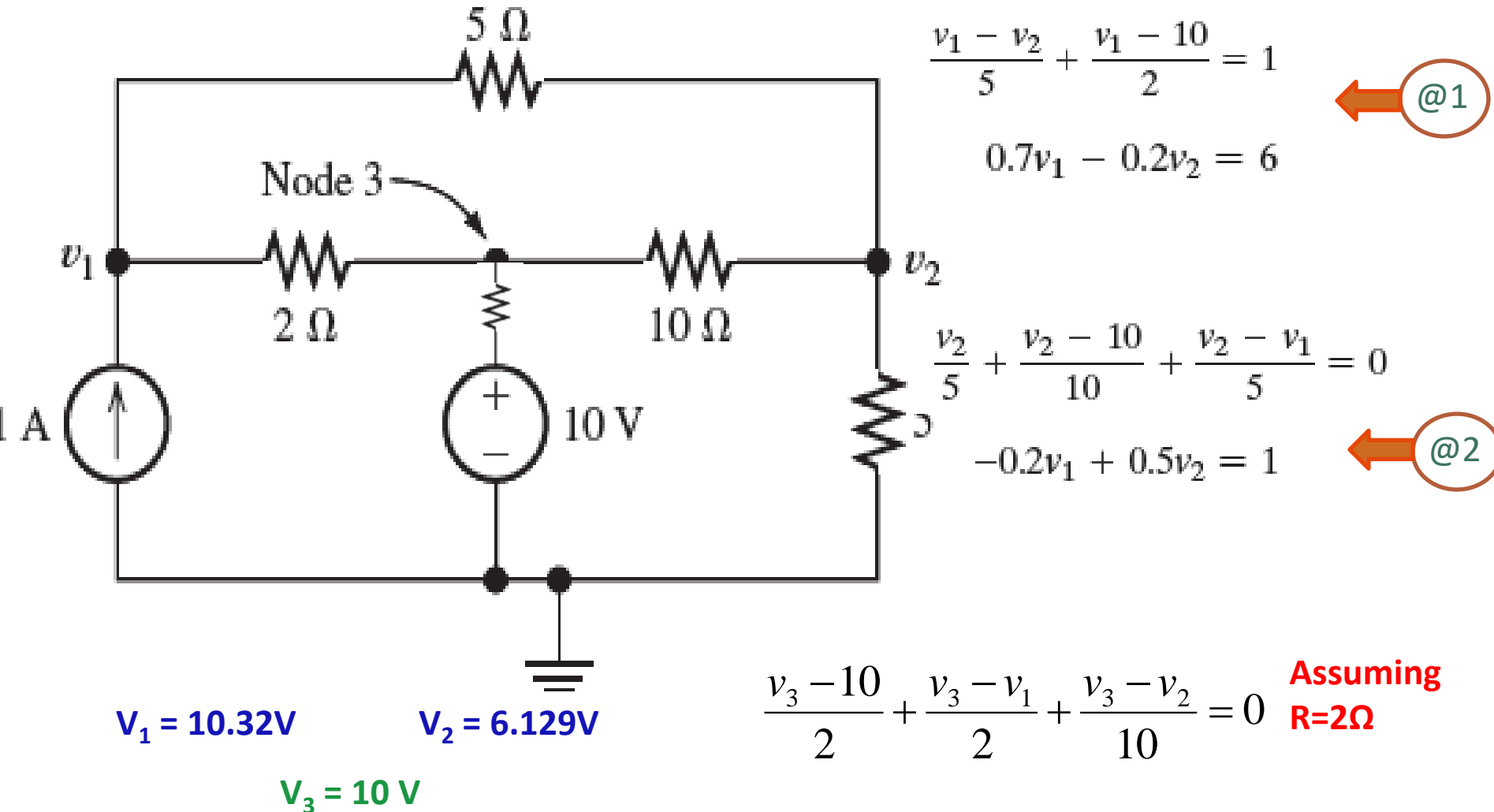

# Practice - 3

## Example 1

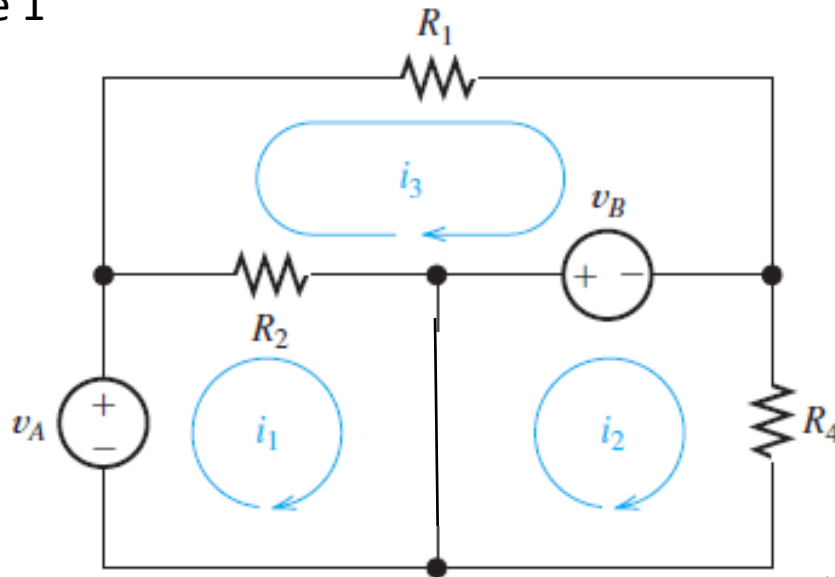


$$\begin{aligned}(R_2 + R_3)i_1 - R_3i_2 - R_2i_3 &= v_A \\ -R_3i_1 + (R_3 + R_4)i_2 &= -v_B \\ -R_2i_1 + (R_1 + R_2)i_3 &= v_B\end{aligned}$$

Apply KVL to each mesh,  
starting with Mesh 1

KVL @ Mesh 2


KVL @ Mesh 3
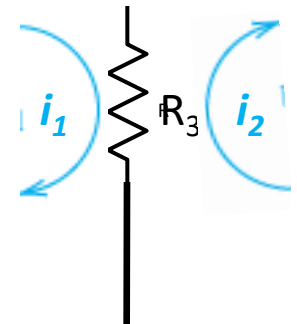
$$\begin{aligned}R_2(i_1 - i_3) &= v_A \\ R_2(i_1 - i_3) + R_3(i_1 - i_2) - v_A &= 0 \\ R_4i_2 &= -v_B \\ R_3(i_2 - i_1) + R_4i_2 + v_B &= 0 \\ R_2(i_3 - i_1) + R_1i_3 - v_B &= 0\end{aligned}$$



R times current in the mesh under consideration minus the adjacent mesh!


# Practice - 4

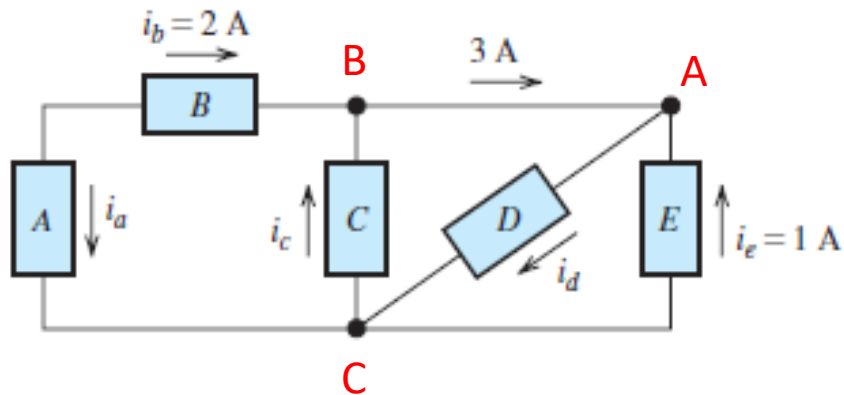

@A  $3 + 1 = i_d$   
 $i_d = 4A$

@B  $2 + i_c = 3$   
 $i_c = 1A$

@C  $i_a + 4 = 1 + 1$   
 $i_a = -2A$

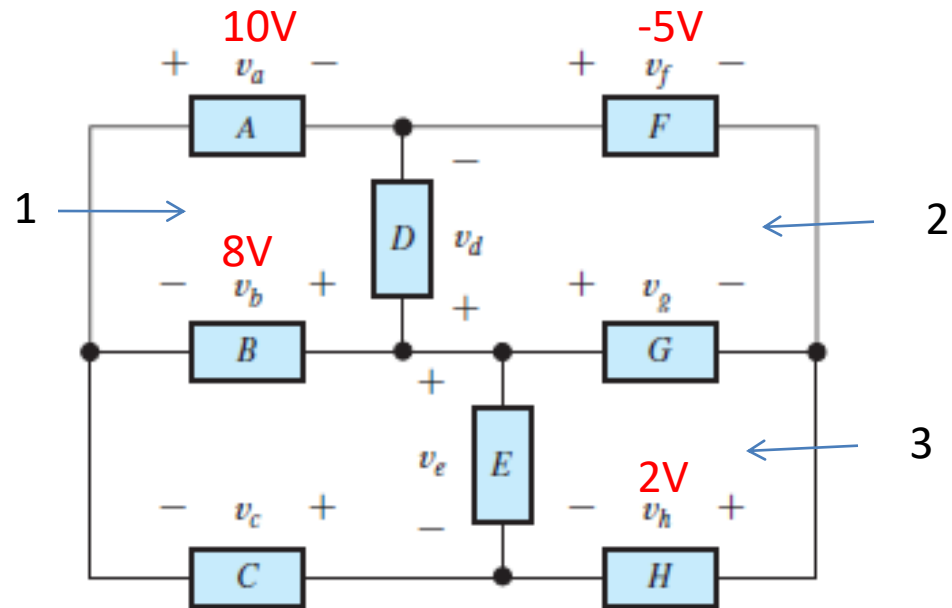


$$10 - v_d + 8 = 0 \quad v_d = 18V$$

$$18 - 5 - v_g = 0 \quad v_g = 13V$$

$$13 + 2 - v_e = 0 \quad v_e = 15V$$

$$-8 + 15 + v_c = 0 \quad v_c = -7V$$

## Practice - 5

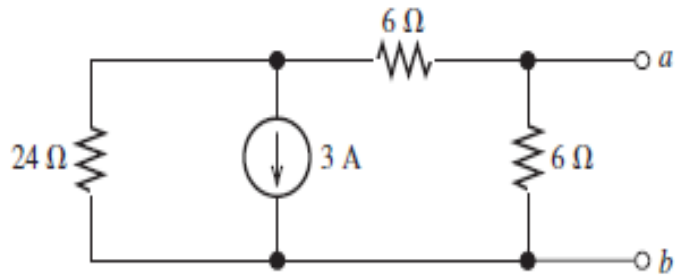


Solving for  $R_{th}$

$$R_{eq1} = 24 + 6 = 30\Omega$$

$$R_{th} = R_{eq1} // 6\Omega$$
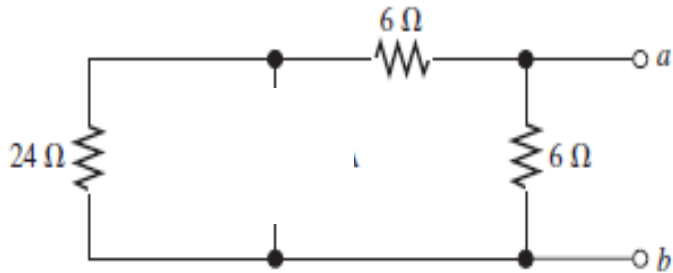
$$R_{th} = \frac{30 \times 6}{30 + 6} = \frac{180}{36} = 5\Omega$$



# Acknowledgements

1. <https://www.allaboutcircuits.com>
2. <https://learnabout-electronics.org>