




EEE1024: Fundamentals of Electrical and Electronics Engineering

Dr. Sanchit Khataavkar

“p-n” Junction Diode

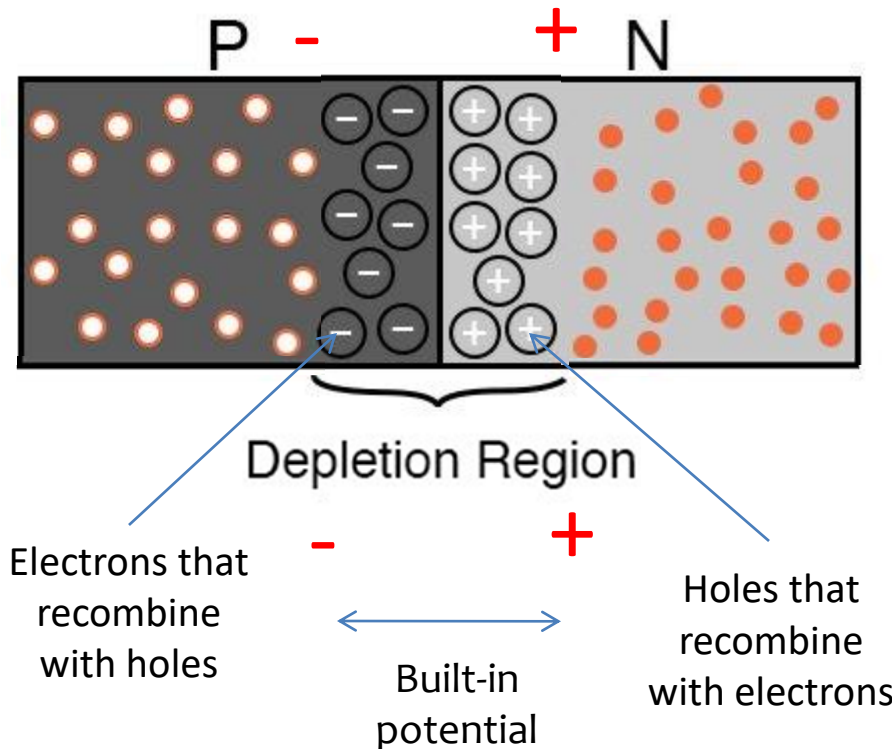This device is formed by joining a p-type semiconductor with an n-type semiconductor



● —————> electrons

○ —————> holes

Because p and n type semiconductors are joined –


Holes from p-type can diffuse into n type

Electrons from n-type can diffuse into p-type

Built-In potential for Silicon – 0.6 to 0.7V


Will this happen till all holes come into n-type and electrons into p-type?

“p-n” Junction Diode – Working (RB)

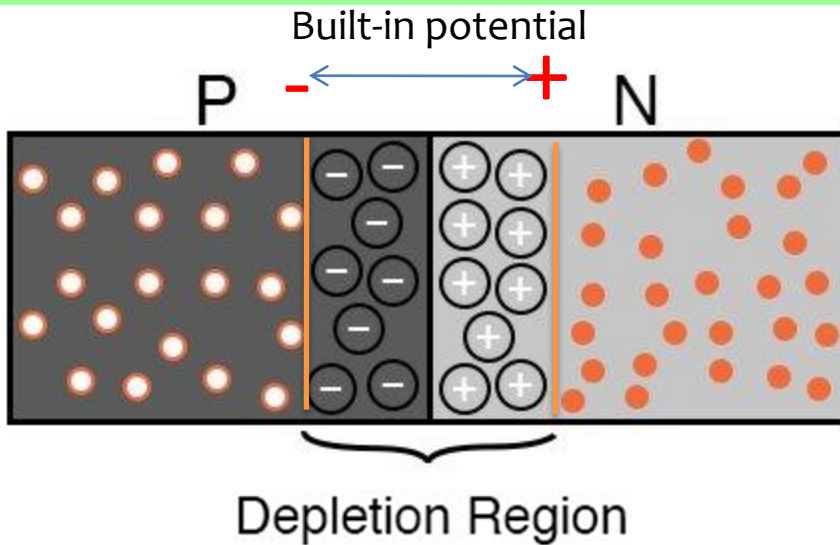

The built-in potential will restrict the flow of diffusion current to either sides of the junction!


Built in potential = Barrier voltage

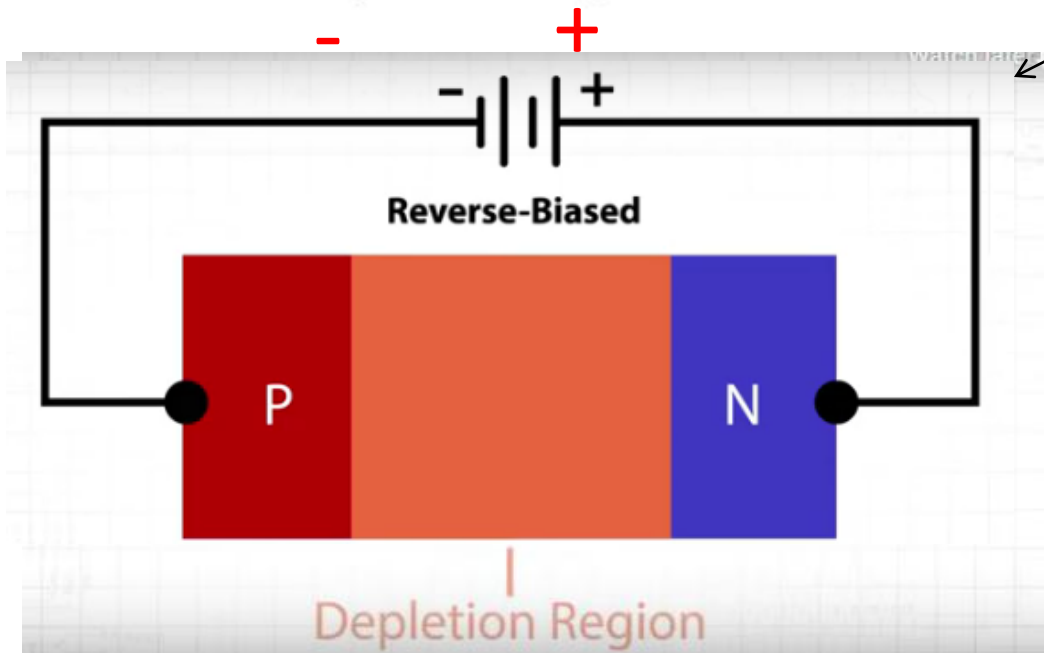

REVERSE - BIAS


- Holes in p-type: Attracted towards -ve terminal & Electrons in n-type: Attracted towards +ve terminal
- Depletion region increases
- Barrier voltage increases
- Diffusion current further reduced

"p-n" Junction Diode – Working (FB)

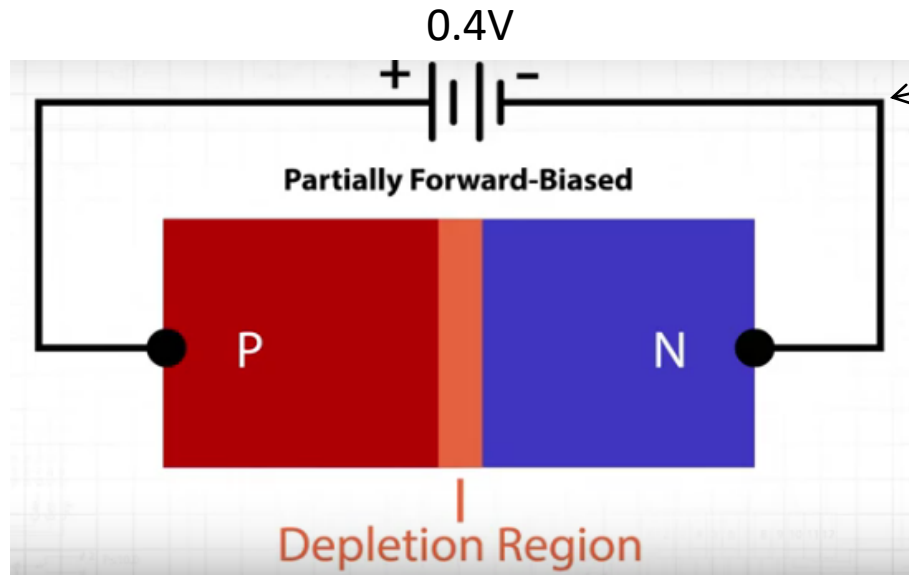

FORWARD – BIAS(partial)

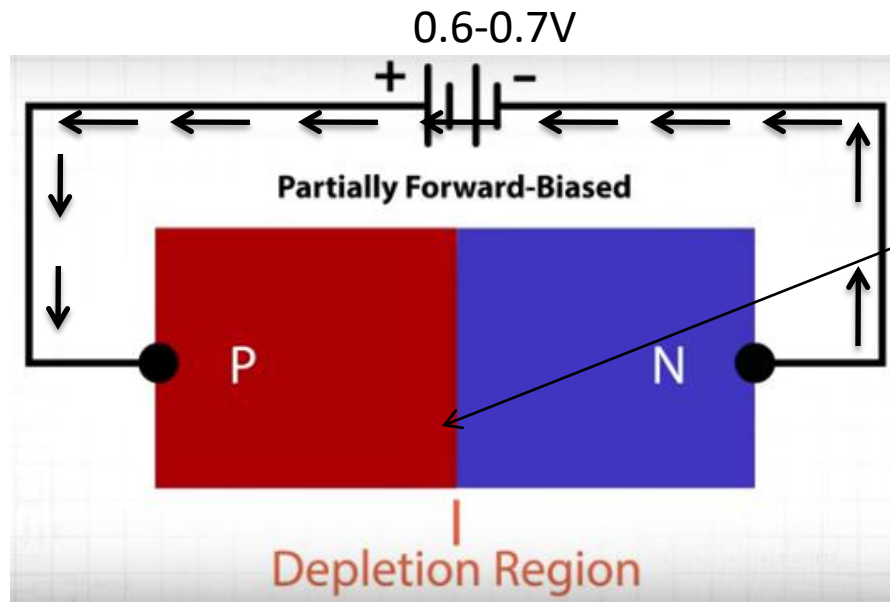- Holes in p-type: Repelled by +ve terminal & Electrons in n-type: Repelled by -ve terminal
- Depletion region decreases
- Barrier voltage reduces
- Diffusion current starts to flow across the junction
- **Amount of current - low**



FORWARD – BIAS (full)

- Fully collapsed depletion region
- **Applied voltage = Barrier voltage**
- **Barrier voltage fully overcome**
- **Enormous diffusion current starts to flow across the junction**
- **Amount of this current – very high!**

“p-n” Junction Diode – *Unique feature!*


REVERSE- BIASED p-n junction diode,

Resists Current flow

FORWARD- BIASED p-n junction diode,


Allows Current flow

Diode → acts like a switch!!!

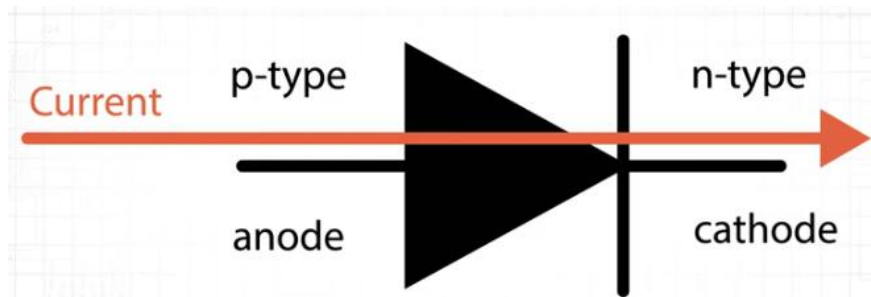

Circuit symbol

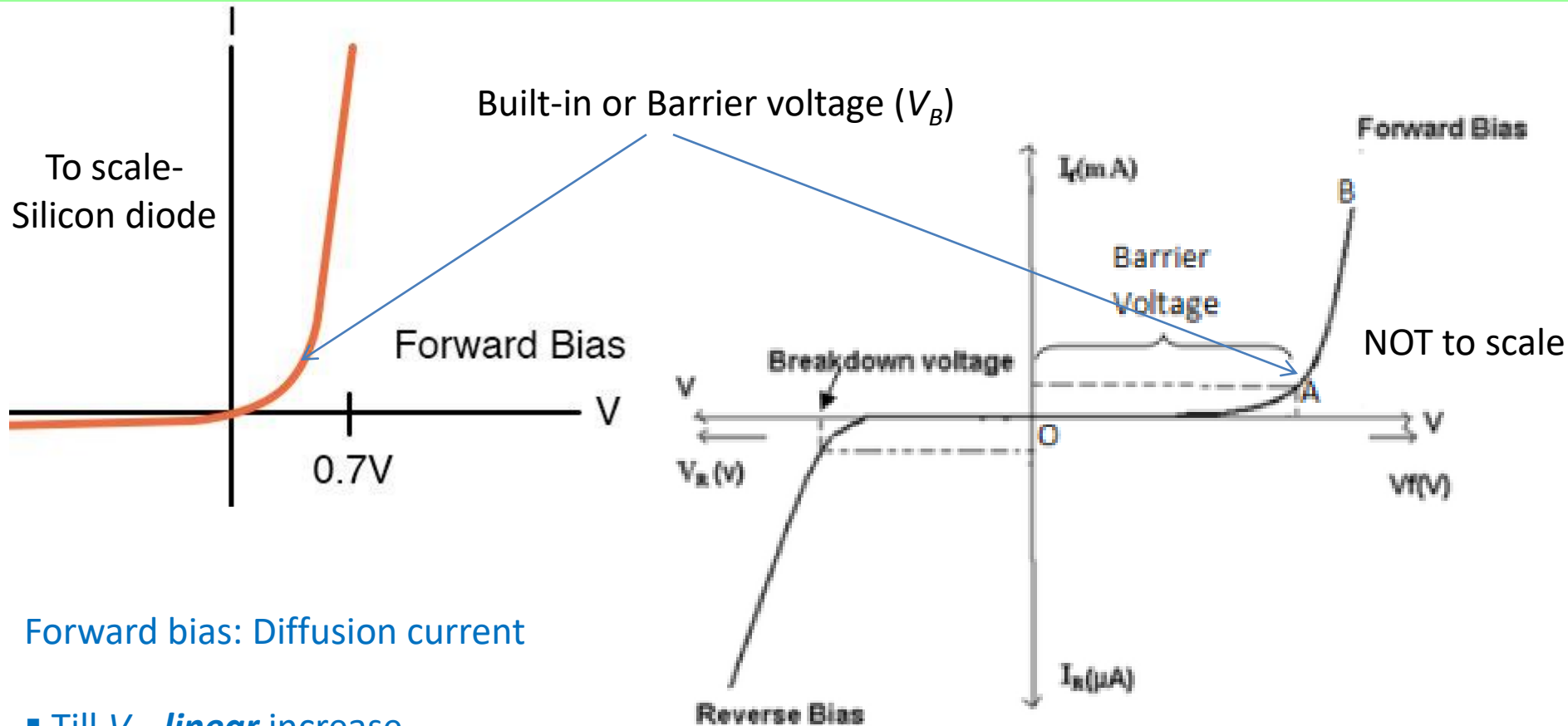“p-n” Junction Diode: *I-V characteristics*




Forward bias: Diffusion current

- Till V_B , **linear** increase
- After V_B , **exponential** increase

Reverse bias: Leakage current

- Very small current flows and is constant till a voltage called **breakdown voltage**

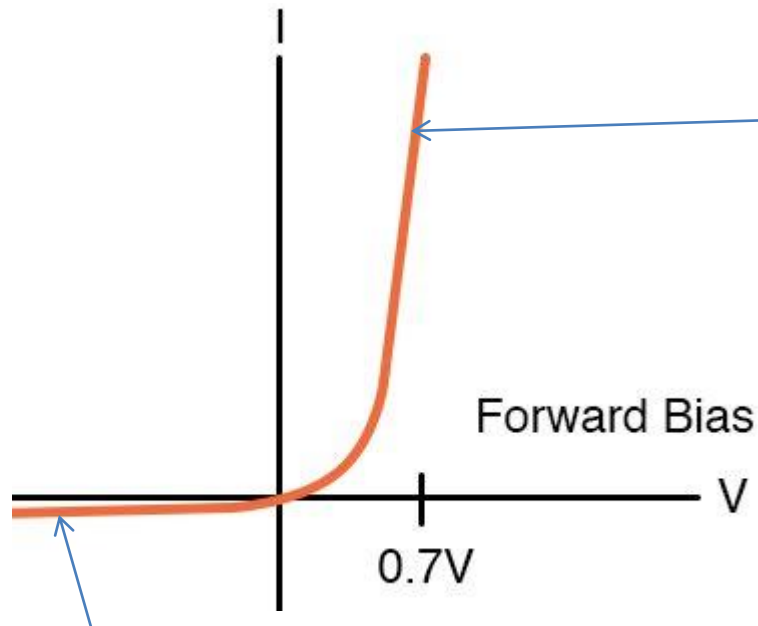“p-n” Junction Diode: *Ideal diode equation*



Ideal diode equation for
Reverse bias

$$I = I_o \left(e^{\frac{qV_A}{kT}} - 1 \right)$$

Ideal diode equation for
Forward bias

$$\frac{kT}{q} = 0.026V$$

Example - $I_o \approx 10^{-15} A$ Find applied
voltage V_A

$$I \approx 39.47 \mu A$$

$$\ln\left(\frac{I}{I_o} + 1\right) = \frac{qV_A}{kT}$$

$$\ln\left(\frac{39.47 \times 10^{-6}}{10^{-15}} + 1\right) = \frac{V_A}{0.026}$$

$$17.49 \times 0.026 = V_A \quad V_A = 0.454V$$

Rectification – *Half wave & Full wave*

Rectification - process of converting an oscillating sinusoidal AC voltage source into a constant current DC voltage supply by means of diodes, thyristors, transistors, or converters.

Types of Rectifiers




- a) Half-wave rectifiers
- b) Full-wave rectifiers
- c) Uncontrolled rectifiers
- d) Fully-controlled rectifiers




Semiconductor Diodes


AC Sinusoidal Waveform

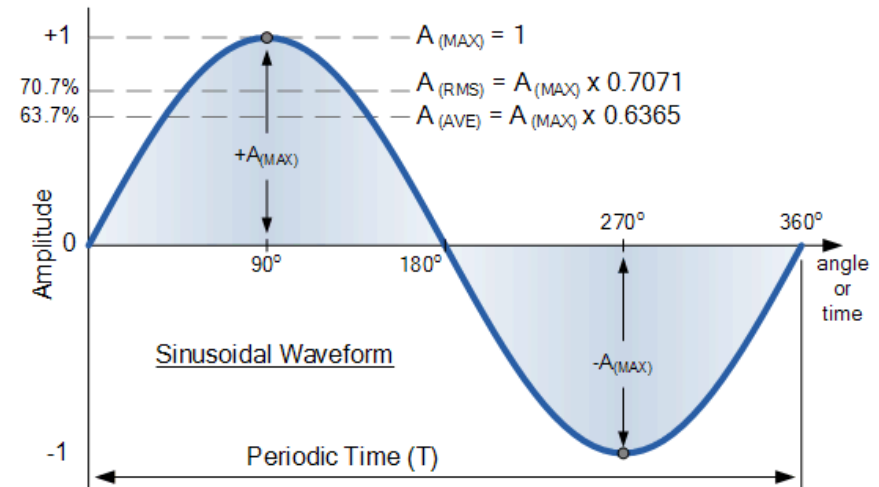

Half wave Rectifier

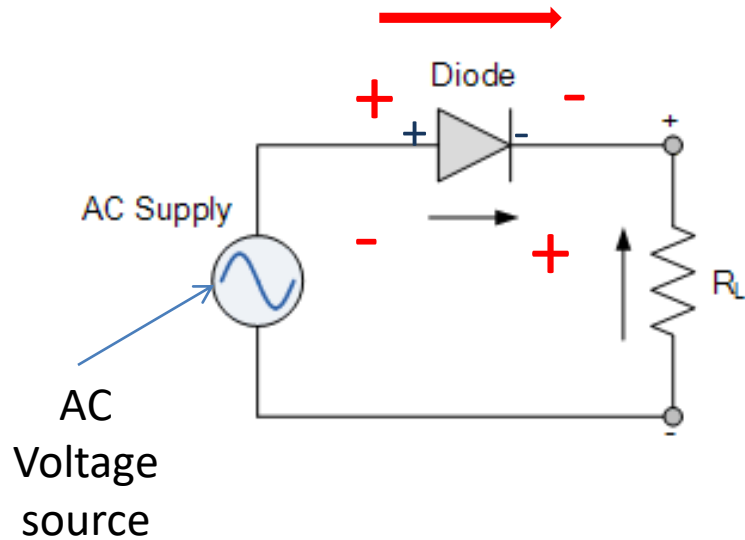

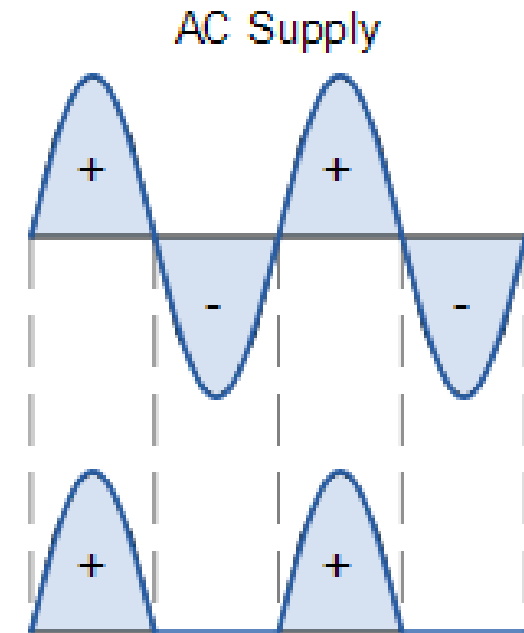
Unique feature of a pn-junction diode utilized to convert the *bi-directional* alternating supply into a *one-way unidirectional* current by eliminating one-half of the supply.




Rectified Output Waveform
No Negative Half-cycle

Half wave Rectifier

AC Sinusoidal Waveform

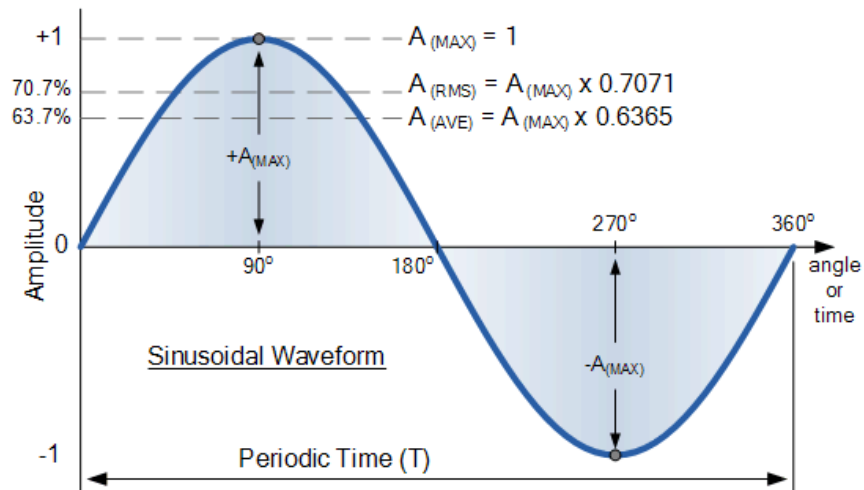
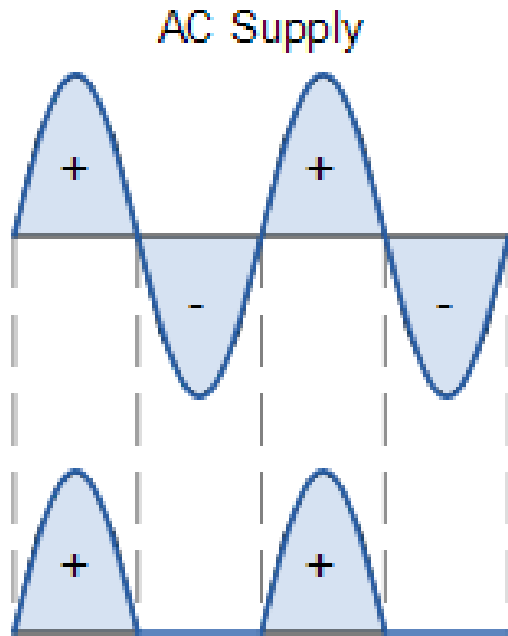
$$A_{AVG} = \frac{0.637}{2} \times A_{MAX} = \frac{A_{MAX}}{\pi} = 0.318 A_{MAX}$$



Rectified Output Waveform
No Negative Half-cycle

$$V_{AVG} = 0.318 * V_{MAX}$$

$$I_{AVG} = 0.318 * I_{MAX}$$


$$\frac{V_{AVG}}{V_{RMS}} = 0.9$$

$$V_{AVG} = 0.45 * V_{RMS}$$

$$I_{AVG} = 0.45 * I_{RMS}$$

Half wave Rectifier

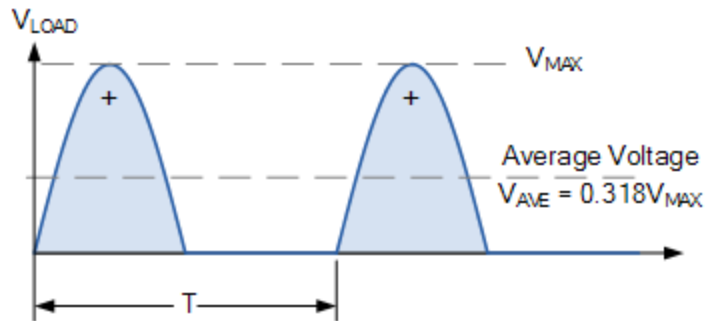Example A single phase half-wave rectifier is connected to a 50V RMS 50Hz AC supply. If the rectifier is used to supply a resistive load of 150 Ohms. Calculate the equivalent DC voltage developed across the load, the load current and power dissipated by the load. Assume ideal diode characteristics.



$$V_m = V_p = V_{PK} = V_{MAX}$$

$$V_{RMS} = 50 \text{ volts} \quad \text{—————} \quad \text{Given}$$

$$V_{max} = V_P = 1.414 \cdot V_{RMS} = 1.414 \cdot 50 = 70.7 \text{ volts}$$

$$V_{RMS} = V_{PK} \times 0.707 \quad \frac{V_{RMS}}{V_P} = 0.707 \quad \frac{V_P}{V_{RMS}} = \frac{1}{0.707} = 1.414$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$


$$\text{Equivalent DC voltage} = 0.318 \cdot V_P = 0.318 \cdot 70.7 = 22.5 \text{ volts}$$

$$\text{Load current} \quad I_L = \frac{V_{DC}}{R_L} = 22.5 / 150 = 0.15 \text{ A or } 150 \text{ mA}$$

$$\text{Power dissipated by load} \quad P_L = V_{DC} \times I \text{ or } I^2 \cdot R_L = 22.5 \cdot 0.15 = 3.375 \text{ W} \approx 3.4 \text{ W}$$

Full wave Rectifier

Full wave BRIDGE Rectifier

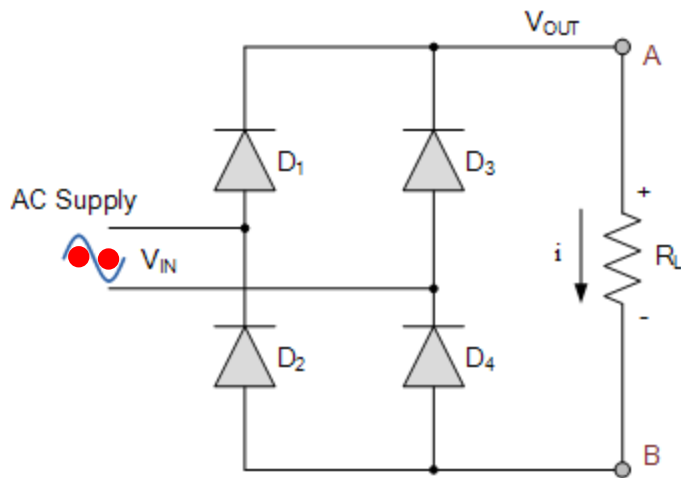

During +ve half cycle of V_{IN} ,

D_1 and D_4 are forward biased, whereas,

D_2 and D_3 are reverse biased

This bridge configuration of diodes provides full-wave rectification because at any time two of the four diodes are forward biased while the other two are reverse biased.



During -ve half cycle of V_{IN} ,

D_2 and D_3 are forward biased, whereas,

D_1 and D_4 are reverse biased

Full wave Rectifier

Full wave BRIDGE Rectifier

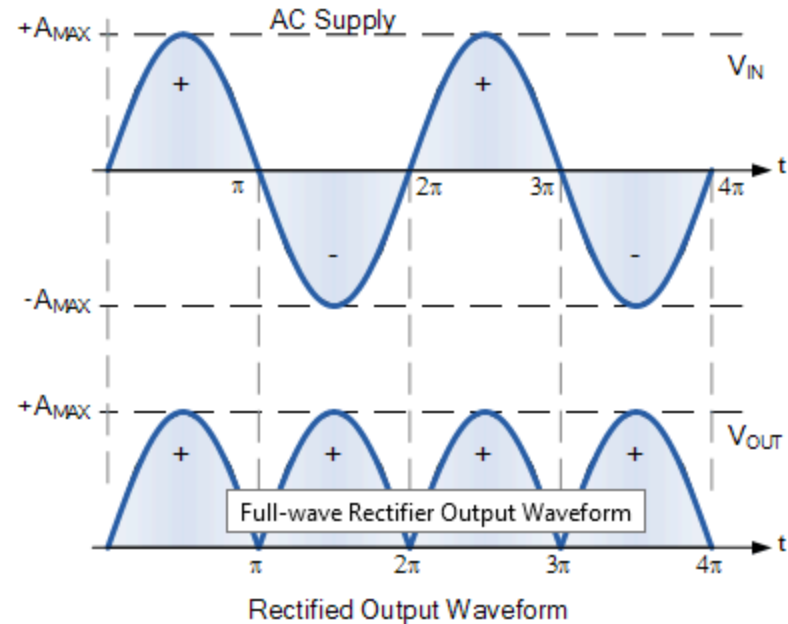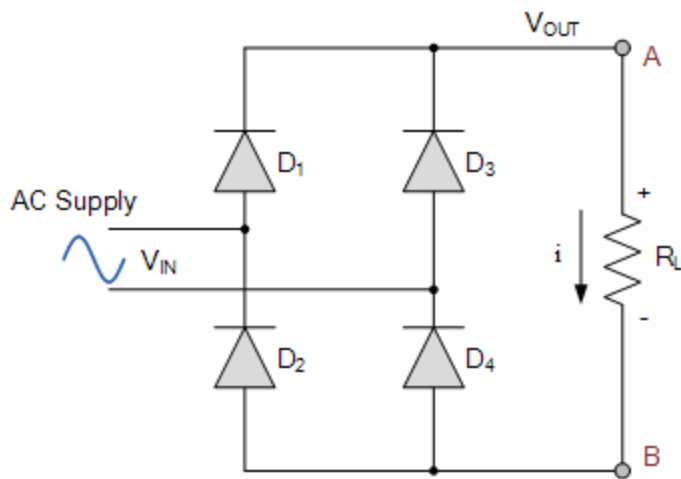

$$V_{AVG} = 0.637 \cdot V_{MAX}$$




$$I_{AVG} = 0.637 \cdot I_{MAX}$$

$$V_{AVG} = 0.9 \cdot V_{RMS}$$

$$I_{AVG} = 0.9 \cdot I_{RMS}$$

Ripple Factor

Half wave Rectifier

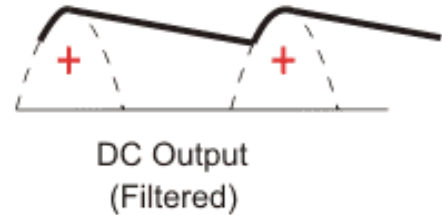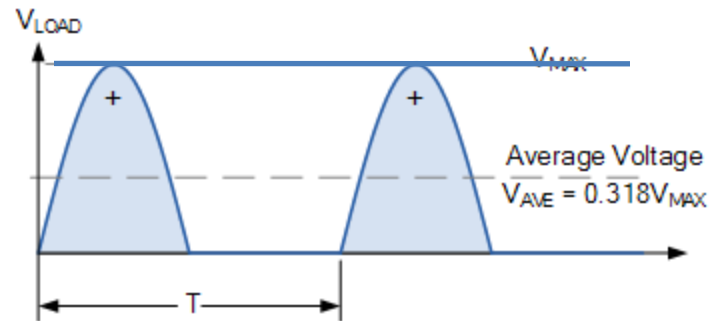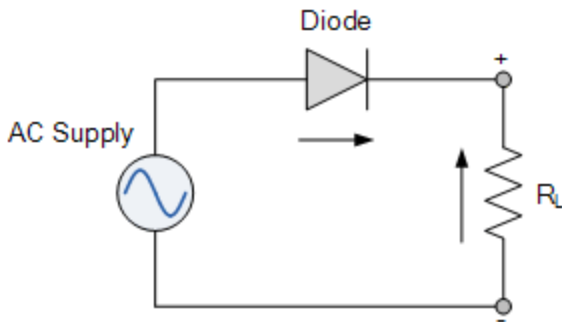

Ripple Factor γ –

Unwanted AC component remaining while converting AC waveform into DC

$$\gamma = \sqrt{\left(\frac{V_{rms}}{V_{DC}}\right)^2 - 1}$$

Acknowledgements

1. <https://www.electronics-tutorials.ws/power/single-phase-rectification.html>
2. <https://www.electrical4u.com/half-wave-rectifiers/>