



EEE1024: Fundamentals of Electrical and Electronics Engineering

Dr. Sanchit Khataavkar

Course Outline

Comm.
Systems

Sensors

**μ processor
&
 μ controller**


**Semiconductor
Devices**

**Digital
Systems**

**AC
Circuits -
Basics**

**DC
Circuits -
Basics**

“Standing on the shoulder of Giants!”

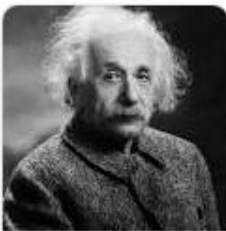

Albert
Einstein
1879–1955




Isaac Newton
1643–1727



Galileo Galilei
1564–1642



Marie Curie
1867–1934

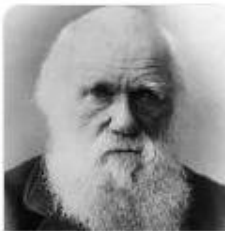


Charles
Darwin
1809–1882



Nikola Tesla
1856–1943



Stephen
Hawking
1942–2018

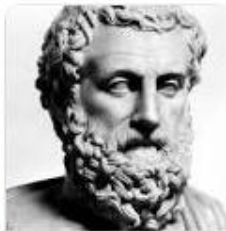

Aristotle
385 BC–32...



Louis Pasteur
1822–1895



Michael
Faraday
1791–1867



Nicolaus
Copernicus
1473–1543



Leonardo da
Vinci
1452–1519



Archimedes
288 BC–21...



Francis Crick
1916–2004



Thomas
Edison
1847–1931



James
Watson



Richard
Feynman
1918–1988



Richard
Feynman
1918–1988



Rosalind
Franklin
1920–1958



Niels Bohr
1885–1962



James Clerk
Maxwell
1831–1879



Carl Sagan
1934–1996



Gottfried
Wilhelm Lei...
1646–1716



Robert Hooke
1635–1703



Alexander
Fleming
1881–1955




Carl Linnaeus
1707–1778

Basic concepts

Electric Circuit – A closed interconnection of electrical elements like sources and loads through wires (or cables) and through which current flows

Simple Electric Circuit

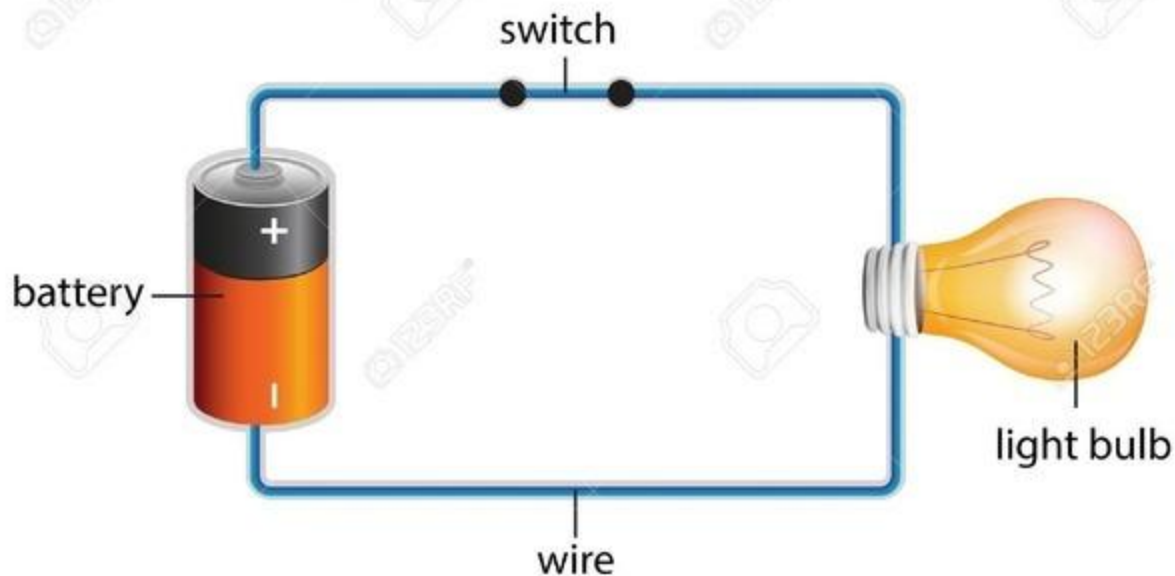

➤ **CHARGE**

➤ **CURRENT**

➤ **VOLTAGE**

➤ **POWER**

CHARGE -
q

- Most fundamental concept in electric circuits.
- Unit – coulomb (C): Charles-Augustin de Coulomb
- From basic physics, charge of 2 types
- 1 electron has $-1.6 \times 10^{-19} \text{ C}$
- 1 proton has $1.6 \times 10^{-19} \text{ C}$

CURRENT -
I

- Time rate of change of charge. $i = \frac{dq}{dt}$
- Unit – ampere (A): A. M. Ampère
- Direct Current (DC) and Alternating Current (AC)

VOLTAGE -
V

- Amount of energy needed to push charge through an element.
- Unit – volts (V): Alessandro Volta
- *Voltage can exist between a pair of terminals regardless of whether current flows through them or not!*

POWER -
P

- Time rate of expending or absorbing energy
- Unit – watts (W): James Watt


Direct Current Vs Alternating Current

Thomas Elva Edison

Current remains constant with time

Unidirectional

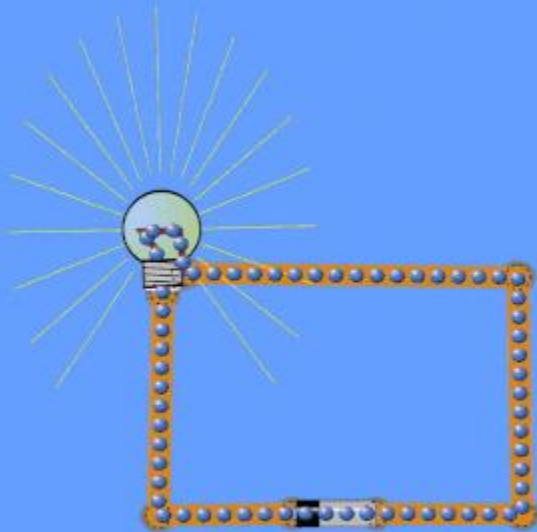DC: Constant flow of electrons from an area of high electron density to an area of low electron density.



Nikola Tesla

Current varies sinusoidally with time

Bi-directional

AC: Current will flip the direction of charge flow (60 times a second in USA (60 Hz) and 50 times a second in Europe (50 Hz) and also in ?



Elements and Sources - Types

Active element:


Capable of generating energy

Generators, Batteries, Operational Amplifiers
– Active elements

Passive element:

Not Capable of generating energy


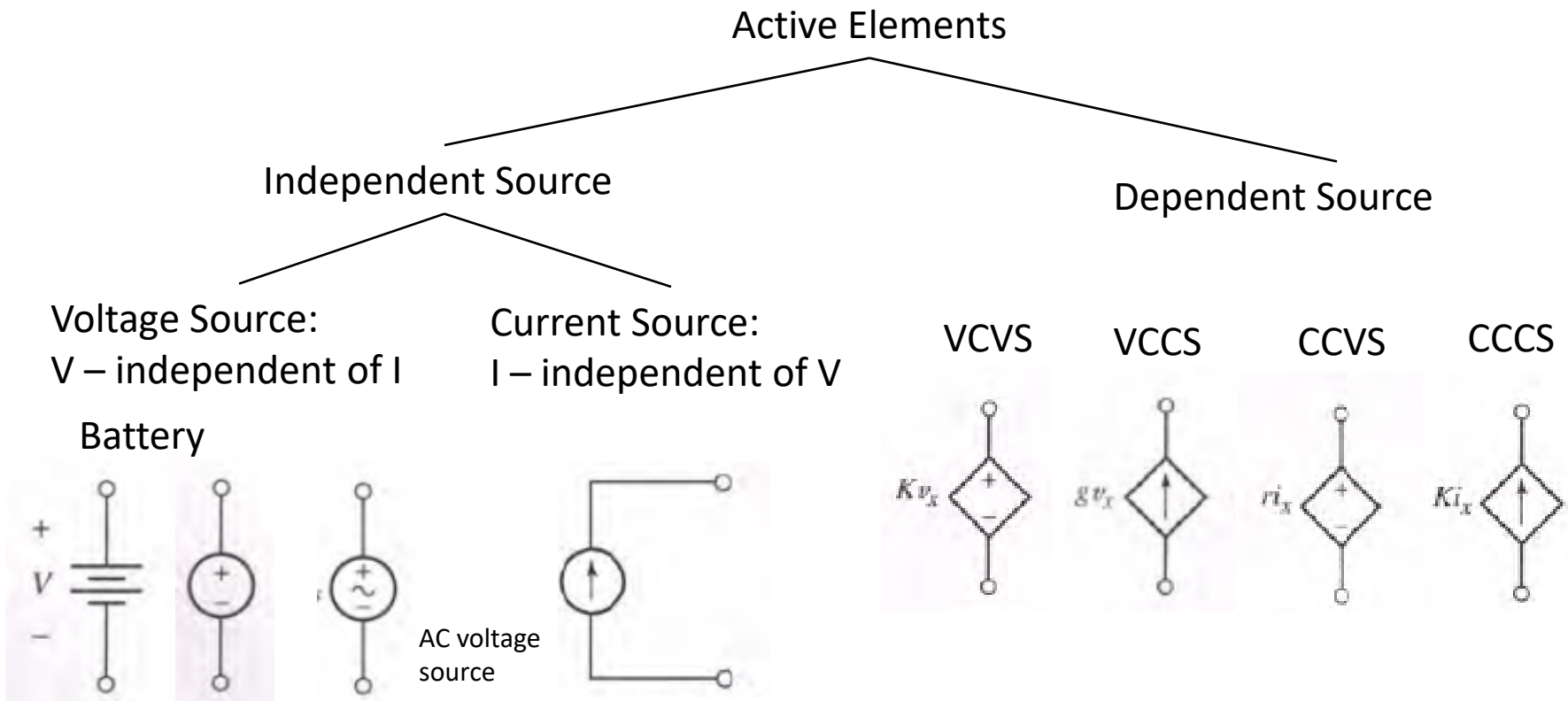
Resistors, Capacitors and Inductors
– Passive elements



Ideal Vs Practical Sources

Independent Voltage source – Voltage completely independent of the current flowing through it.

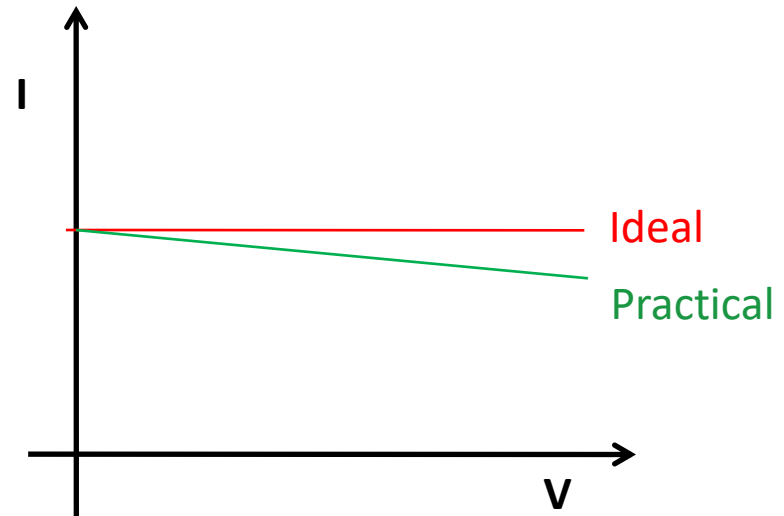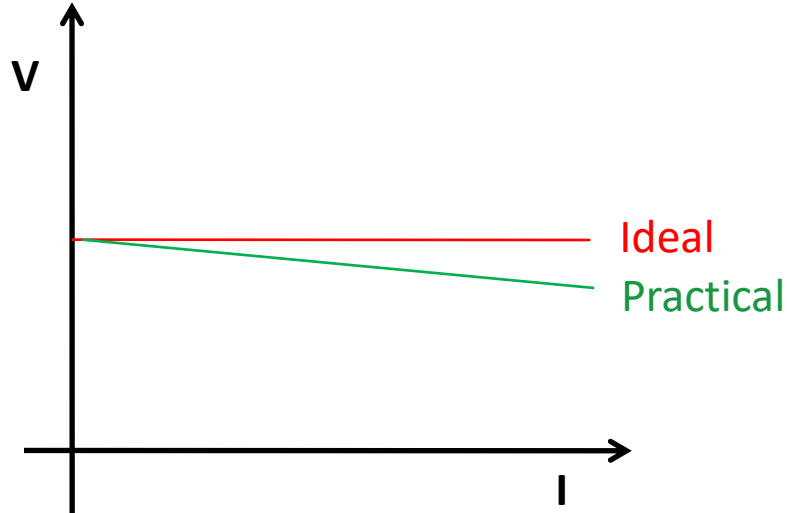Independent Current source – Current completely independent of the voltage flowing through it.



Passive Elements

Linear Resistor: 1827 – G. S. Ohm and later Henry Cavendish


“Voltage across conducting materials is proportional to the current flowing through it”

$$V \propto I \quad V = IR \quad \text{or} \quad R = \frac{V}{I} \quad \text{where } R \text{ is constant of proportionality - resistance}$$

Unit of resistance – ohm “ Ω ”

$$1\Omega = \frac{1V}{1A}$$
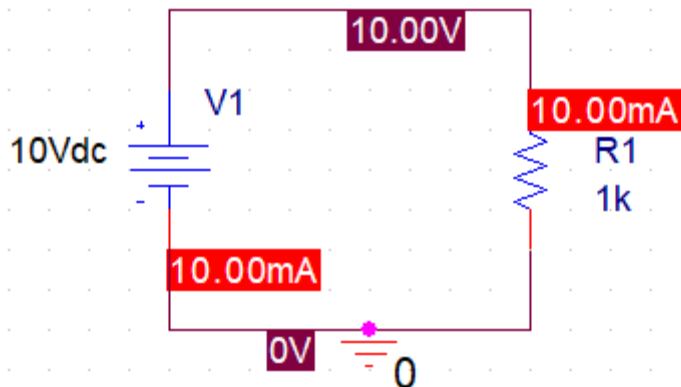
$$\frac{1A}{1V} = 1S \quad \text{where } S \text{ is unit of Conductance 'G'} \quad G = \frac{I}{V} = \frac{1}{R}$$



$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{10}{1 \times 10^3}$$

$$I = 10^{-2} \text{ A}$$

$$I = 10 \text{ mA}$$

