



EEE1024: Fundamentals of Electrical and Electronics Engineering


Dr. Sanchit Khataavkar

Assessments and Other Guidelines

Assessment Type	Date	Max. marks	Weightage	Remarks
Assignment I	Before CAT I	30	10%	Questions and Rubrics will be given later
Assignment II	After CAT II	30	10%	Questions and Rubrics will be given later
Quizes	Throughout the course	50	10%	During class
CAT-I	As per University announcement		15%	Schedule to be announced by University in due course.
CAT-II			15%	
FAT			40%	

ATTENDANCE: 75% !!!

Kirchhoff's Current law (KCL)

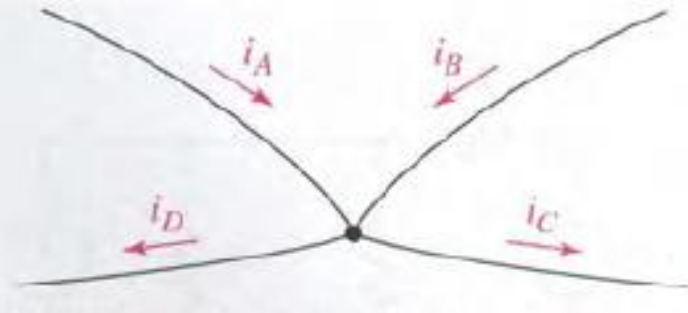

$$i_A + i_B = i_C + i_D$$


Algebraic sum of currents entering any node is zero

Entering the node $i_A + i_B + (-i_C) + (-i_D) = 0$

Leaving the node $(-i_A) + (-i_B) + i_C + i_D = 0$

$$\sum_{n=1}^N i_n = 0$$

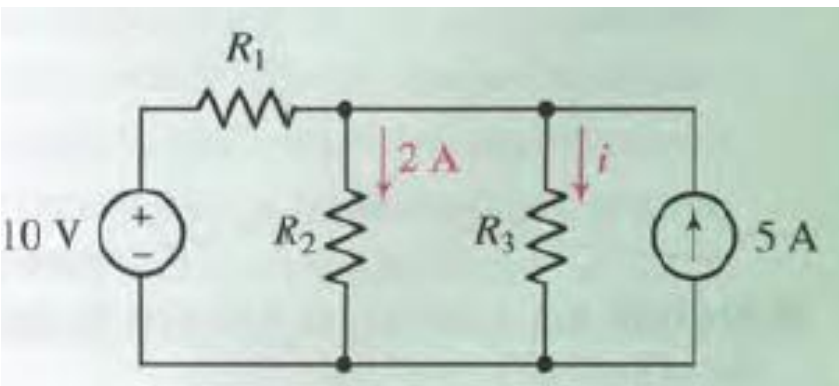Example: If the voltage source supplies 3A of current, compute the current through resistor R_3





Strategy for such questions

- 1) Identify goal of the problem
- 2) Collect known info
- 3) Devise a plan
- 4) Construct proper set of equations.

Kirchhoff's Current law (KCL)

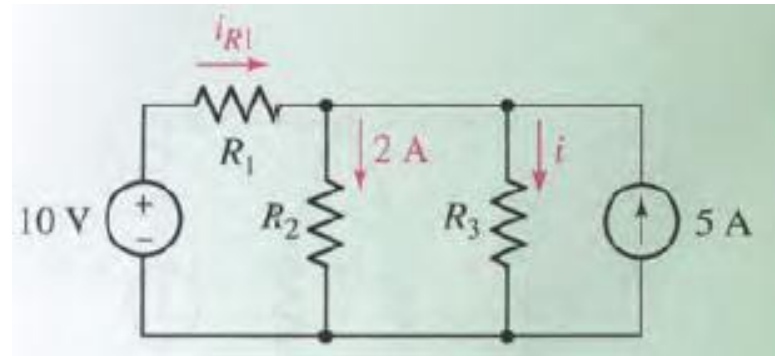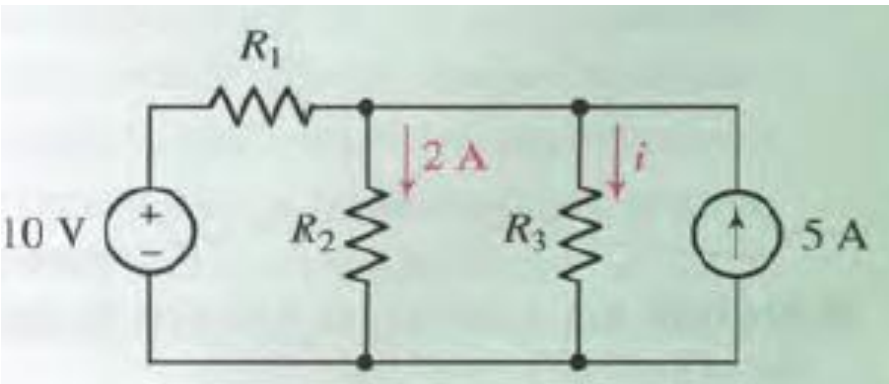Example: If the voltage source supplies 3A of current, compute the current through resistor R_3



- 1) Identify goal of the problem:

Labelled 'i' on the figure

- 2) Collect known info:


Top node of R_3 connected to 3 branches.
Current flowing into this node will have currents from these 3 branches.

- 3) Devise a plan:

Label current thr' R_1 and write KCL at the top node of R_3

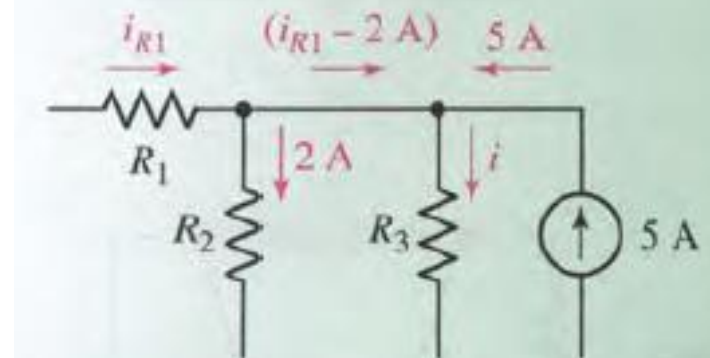- 4) Construct proper set of equations:

Summing up the currents flowing into the node -





$$i_{R1} - 2 - i + 5 = 0$$

$$3 - 2 + 5 = i$$

$$i = 6A$$

Which node to choose?

Kirchhoff's Current law (KCL)

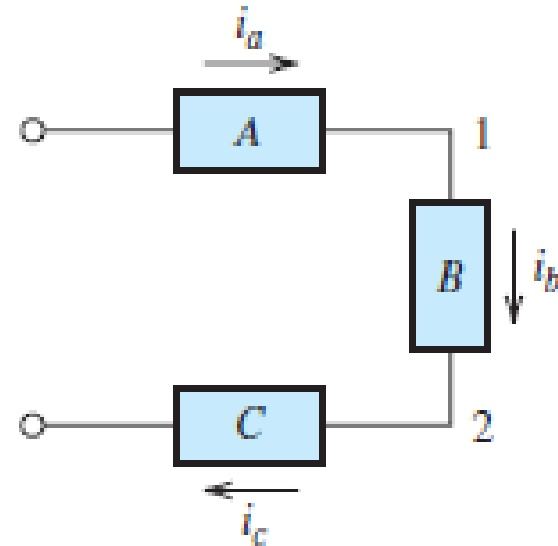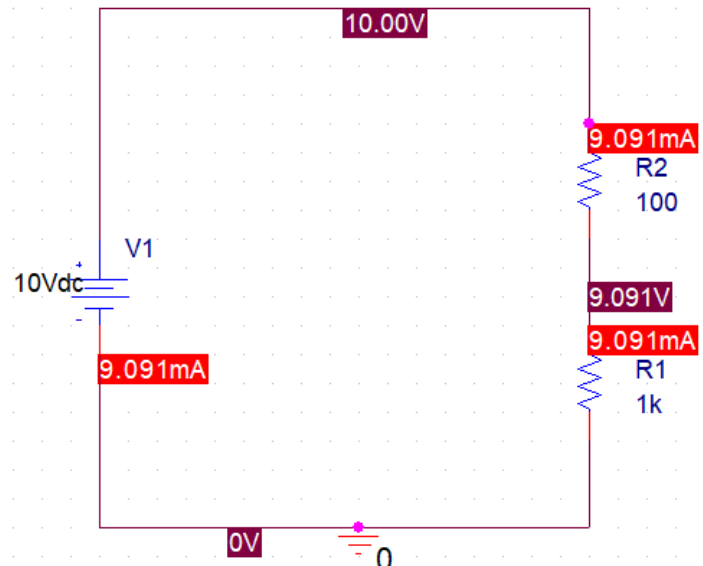

Elements connected from end to end ——— Series circuit

CURRENT in a **SERIES** circuit – remains same!

Apply KCL to check this!


@ Node 1, $i_a = i_b$

@ Node 2, $i_b = i_c$

Thus, $i_a = i_b = i_c$

Kirchhoff's Voltage law (KVL)

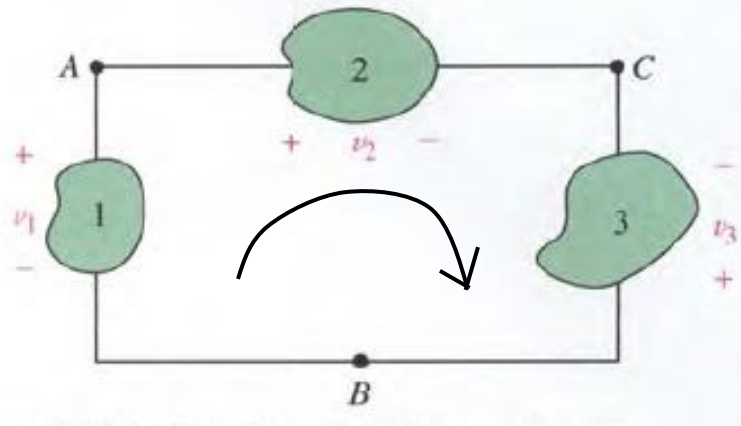Algebraic sum of voltages around any closed path is zero




$$v_1 + v_2 + v_3 + \dots + v_N = 0$$

$$\sum_{n=1}^N v_n = 0$$

Move mentally in a clockwise direction, write voltage of each element in such a way that if a +ve terminal is encountered then +ve, and if -ve terminal, then -ve

$$-v_1 + v_2 - v_3 = 0$$

Example: Find v_x and i_x

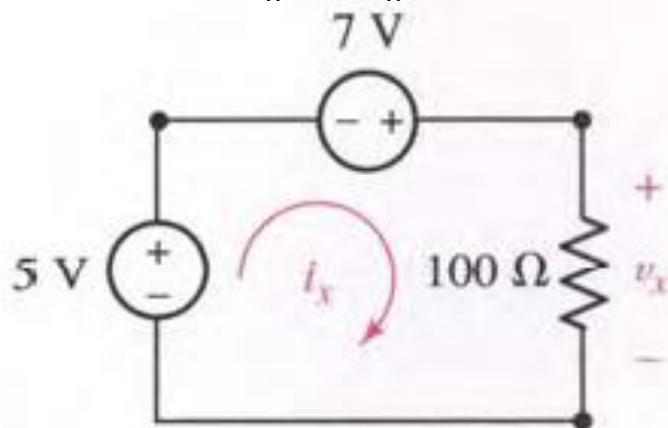


Applying KVL,

$$-5 - 7 + v_x = 0$$

$$i_x = \frac{v_x}{100} = \frac{12}{100} \text{ A} = 120 \text{ mA}$$

Kirchhoff's Voltage law (KVL)

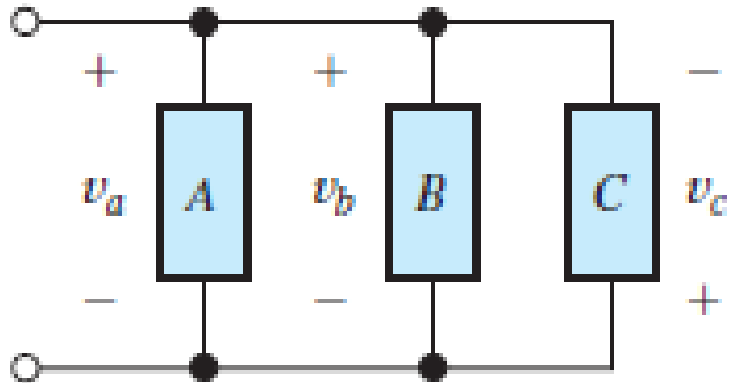

Both ends of an element to the _____ Parallel circuit
corresponding ends of the other

VOLTAGE in a **PARALLEL** circuit – remains same!

Apply KVL to check this!


@ Loop 1, $-v_a + v_b = 0$

@ Loop 2, $-v_a - v_c = 0$


Thus, $v_a = v_b = -v_c$

Practice

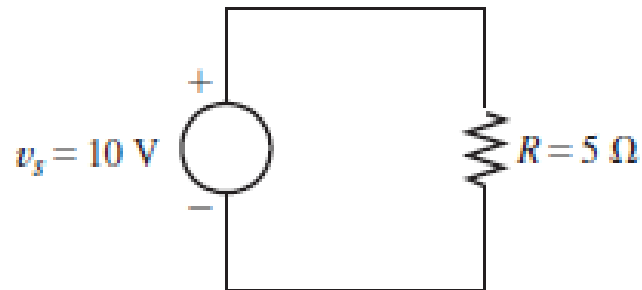Q) Find voltages, current and power in this simple circuit




1) Apply KVL to the loop -

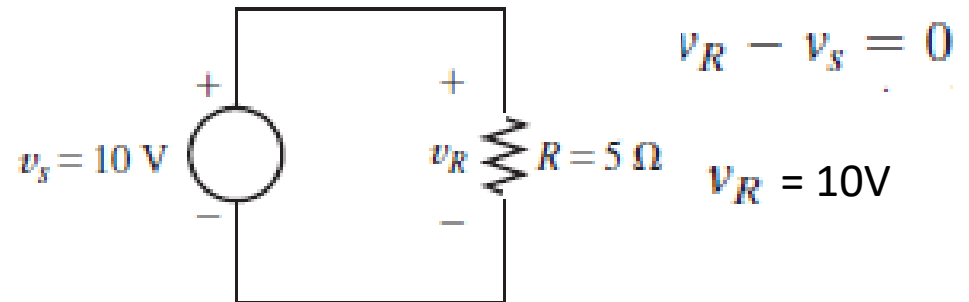


2) Source and R in parallel –
V has to be same!

4) Apply KCL to 2 nodes

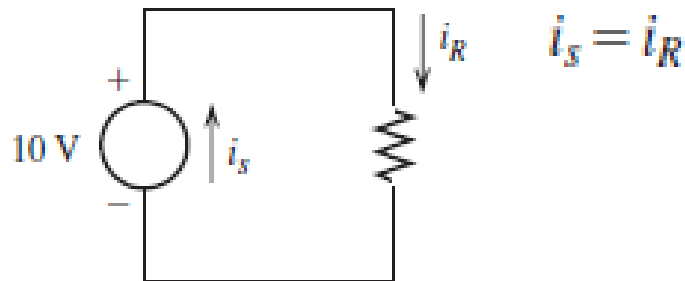


3) Use Ohm's law -

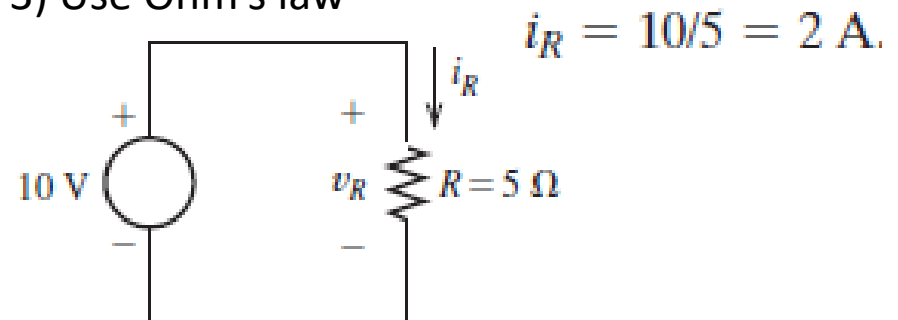

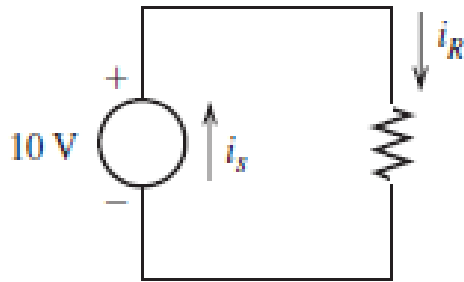5) Source and resistance in series – I has to same!

Practice

Q) Find voltages, current and power in this simple circuit



Case where source and R were in series and parallel!

Happens only in a 2 element circuit

Power delivered to resistor

$$p_R = v_R i_R = 10 \times 2 = 20 \text{ W}$$

$$p_R = i_R^2 R = 2^2 \times 5 = 20 \text{ W}$$

$$p_R = \frac{v_R^2}{R} = \frac{10^2}{5} = 20 \text{ W}$$

Power supplied by the source

$$p_s = -v_s i_s = -10 \times 2 = -20 \text{ W}$$

Law of conservation of energy!